
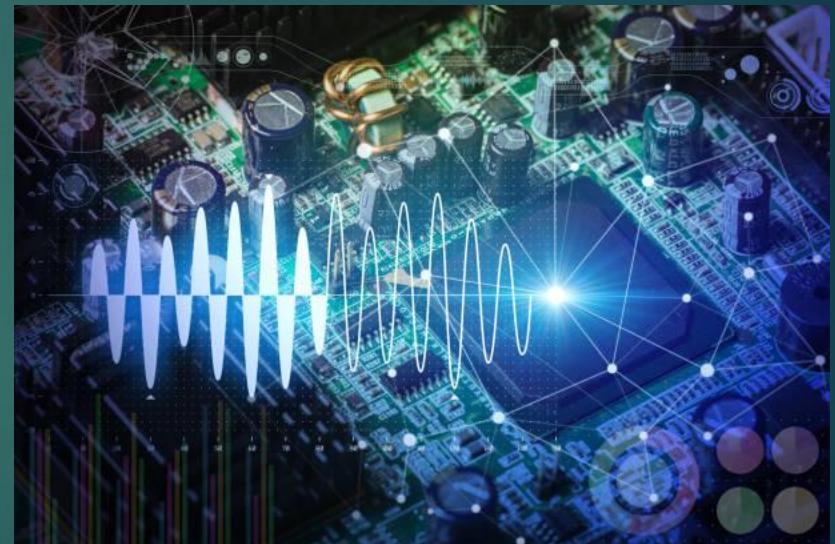


# EE3301 Analog Electronics

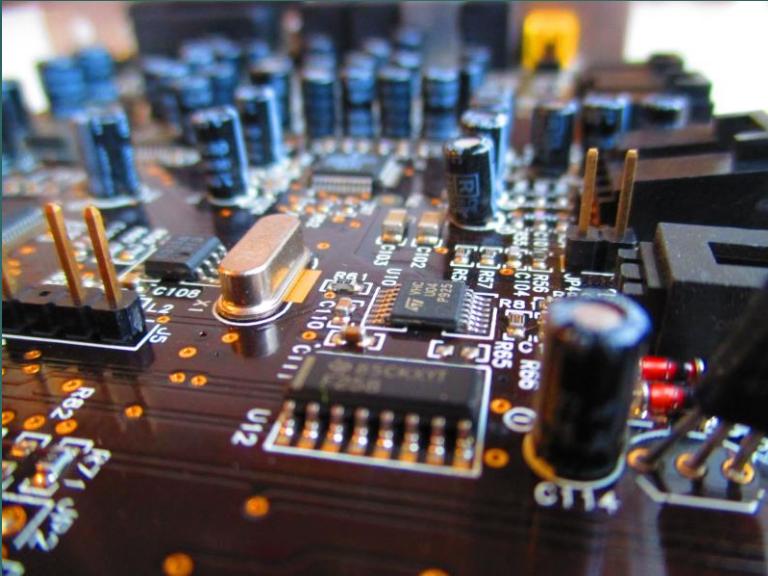

Neel Karunasena

Department of Electrical & Information Engineering

Faculty of Engineering University of Ruhuna

# DC POWER SUPPLIES AND REGULATION CIRCUITS

1. Diodes
2. Half Wave Rectification and Full wave Rectification
3. Clamping and Clipping
4. Filtering and Regulation

# Diodes

## Types of materials

### 1. Conductor

is defined as materials that allow electricity to flow through them easily.

Eg:- Copper, Gold, Iron, Aluminum



## 2. Insulator

is a material that does not conduct electrical current

Eg:- Plastic, Wood, Glass



Dry wood




Glass




Rubber
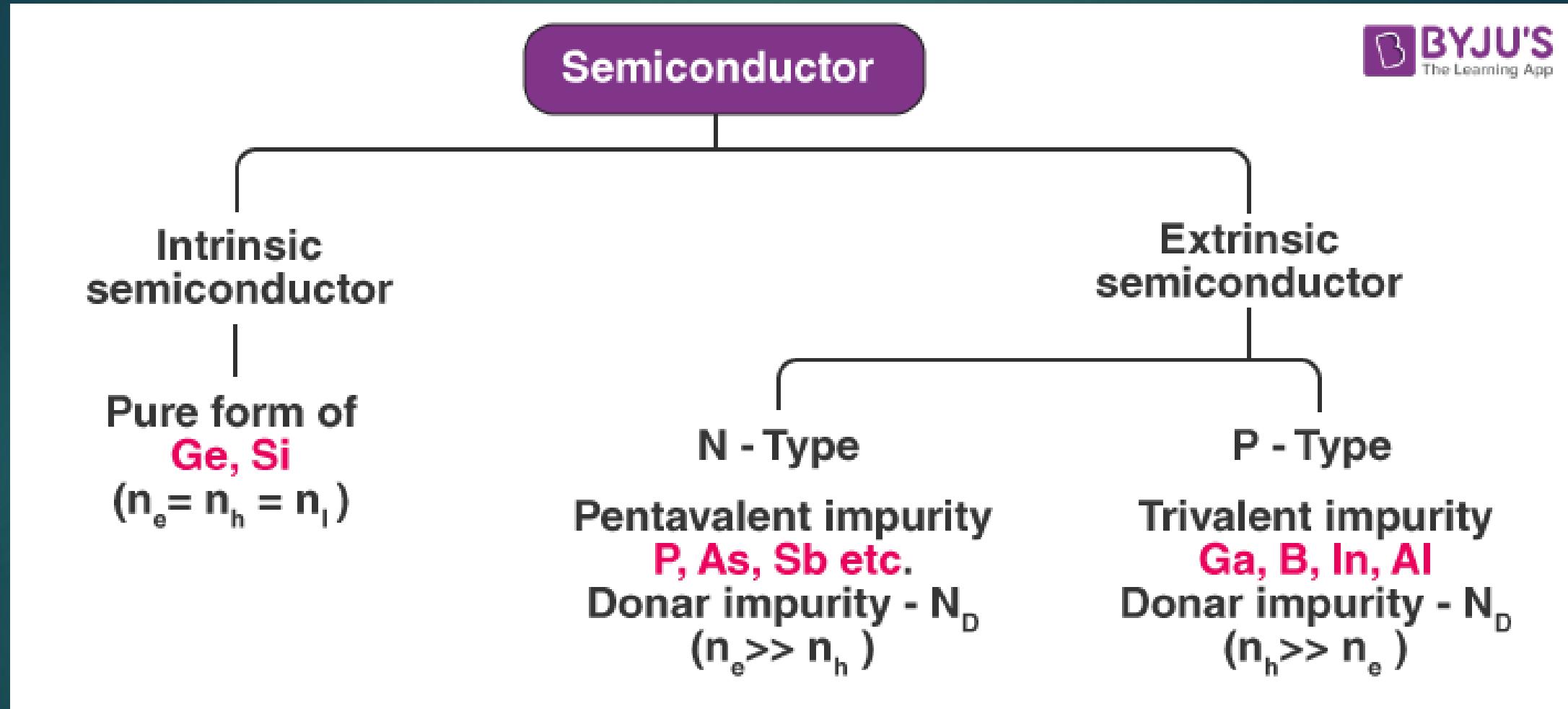
## 3. Semiconductor


is a material that has a conductivity between conductors and insulators



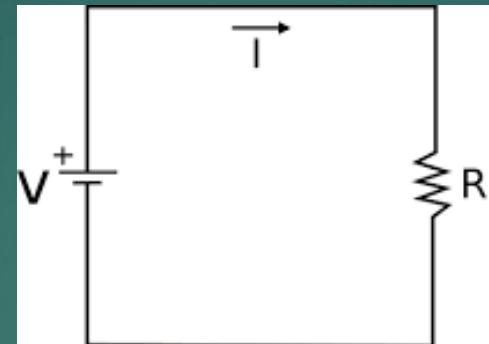Q1) When  $V= 8.8 \text{ V}$  and  $R= 2.2 \text{ k}\Omega$ , Calculate the current through the resistor.



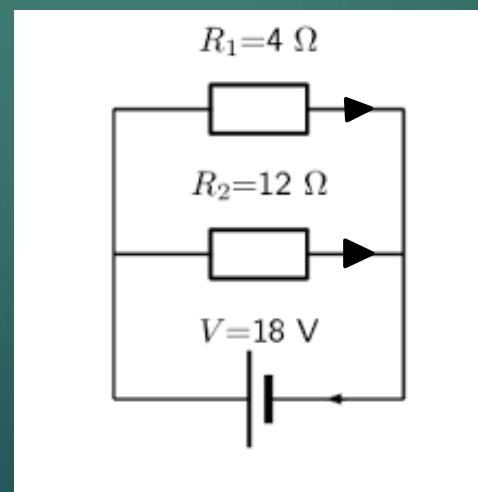Q2) Calculate the total current drawn from the battery.




$$Q_1. \quad V = IR.$$

$$8.8 = I \times 2.2 \times 10^3$$

$$I = 4 \times 10^{-3}$$

$$\underline{\underline{I = 4 \text{ mA}}}$$

$Q_2$

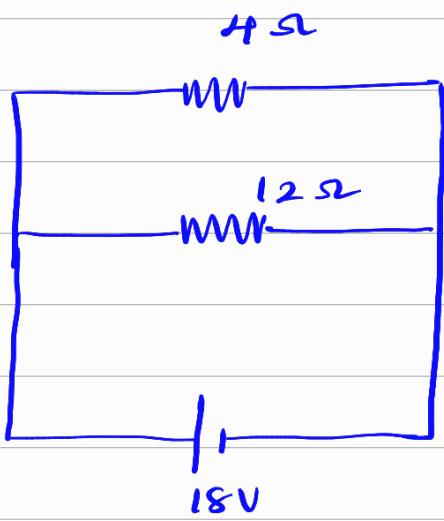

$$R_{eq} = \frac{4 \times 12}{16}$$

$$R_{eq} = 3 \Omega$$


$$V = IR.$$

$$18 = I \times 3$$

$$\underline{\underline{I = 6 \text{ A}}}$$

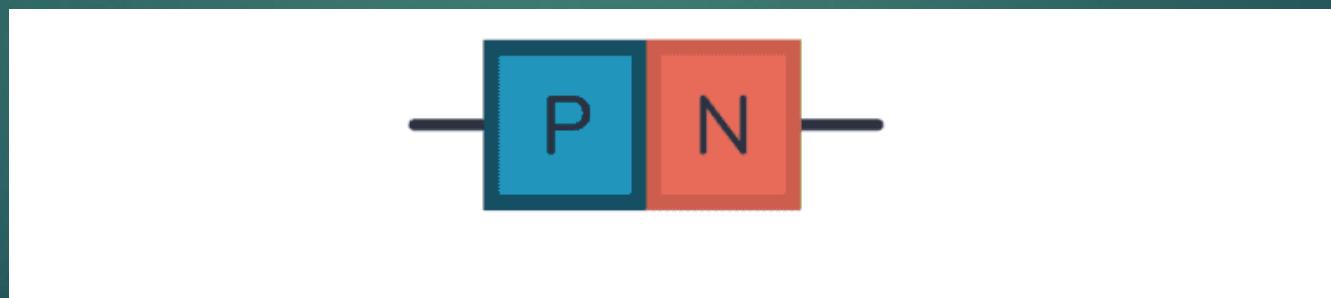
# What is a Diode?

- A diode is a component that lets current flow in one direction and blocks it from flowing in the other direction.
- The diode is created from a PN junction. Can get a PN junction by taking a negatively doped and positively doped semiconductor material and putting it together.


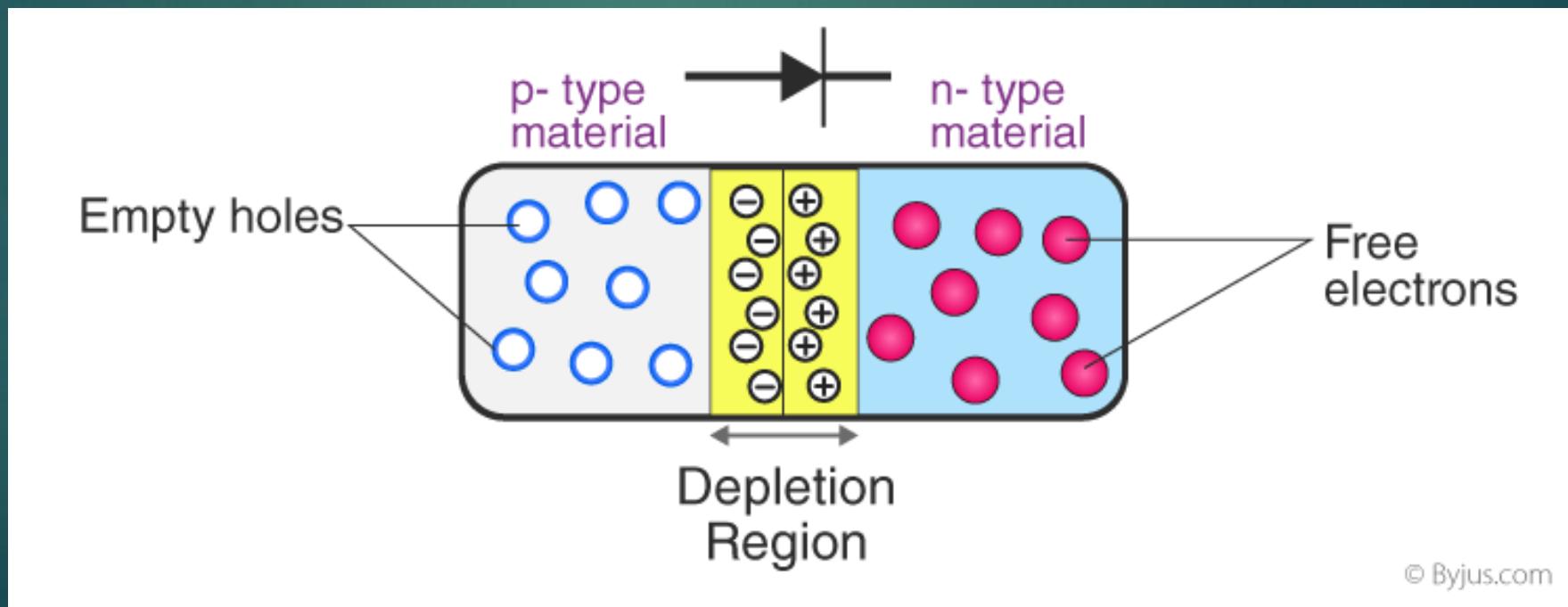
# What is P-N Junction?

A P-N junction is an interface or a boundary between two semiconductor material types, namely the p-type and the n-type, inside a semiconductor.



# Types of Diodes



## Types of Diode



Junction  
Diode



Zener  
Diode




Tunnel  
Diode




Schottky  
Diode



Varactor  
Diode

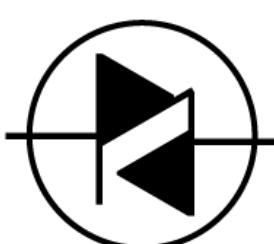


Diac

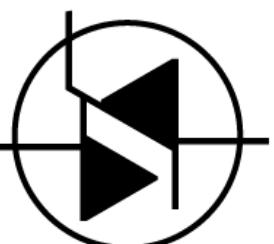


Triac



SCR

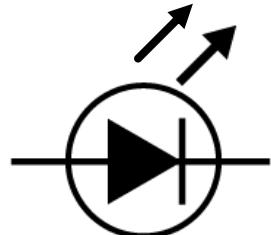


Light Emitting  
Diode (LED)

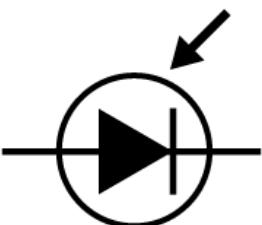



Photodiode

# Rectifier Diode


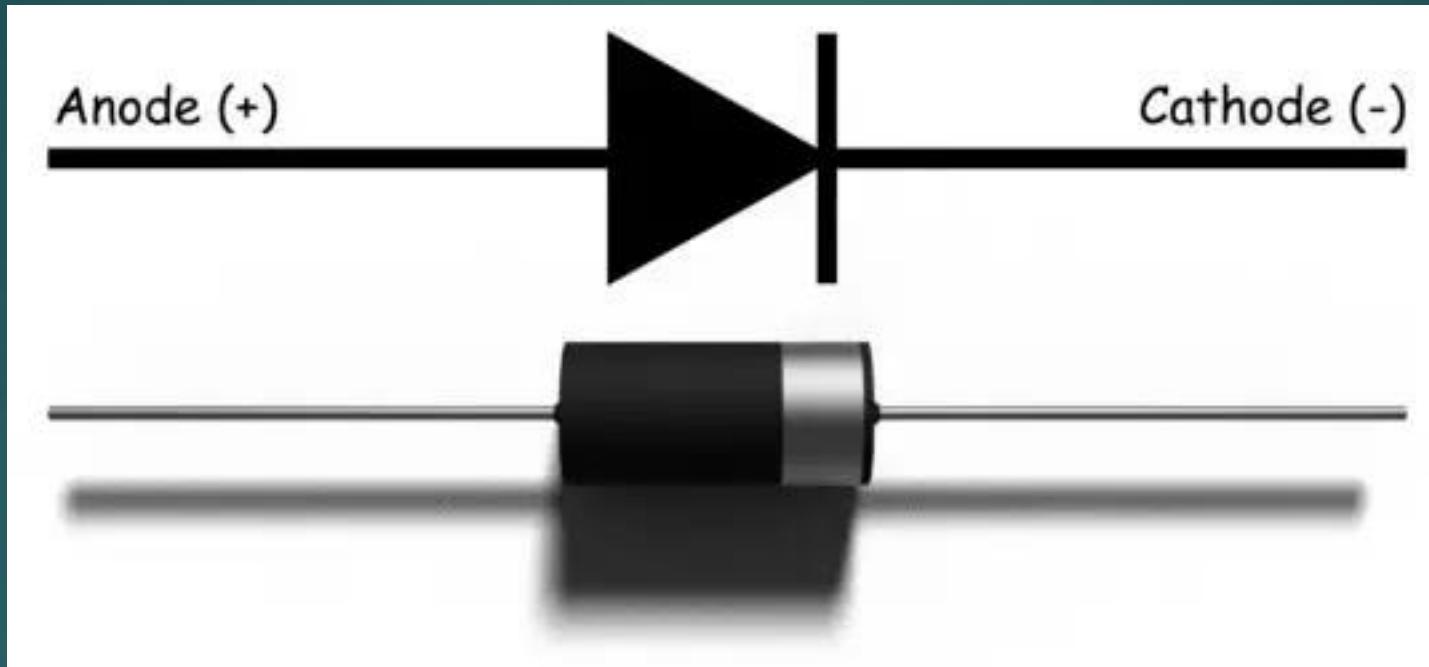


# Diode modes

## 1. Forward Bias

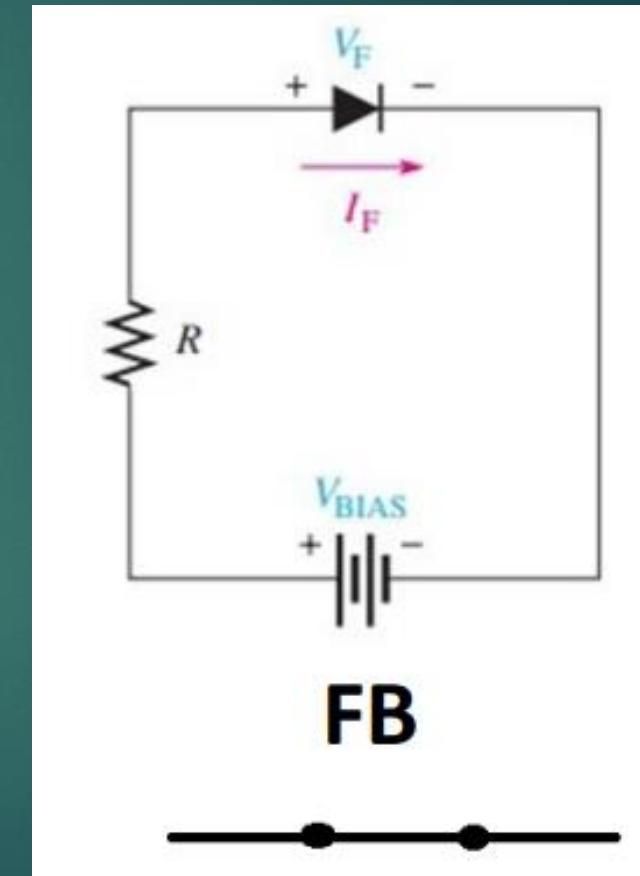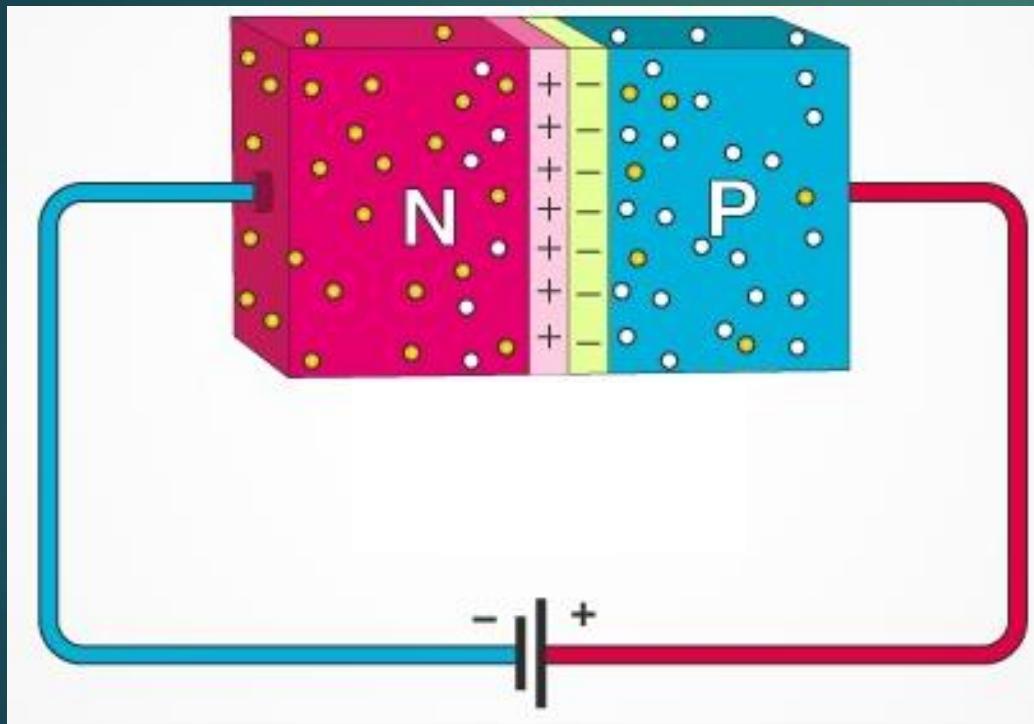


## 2. Reverse Bias

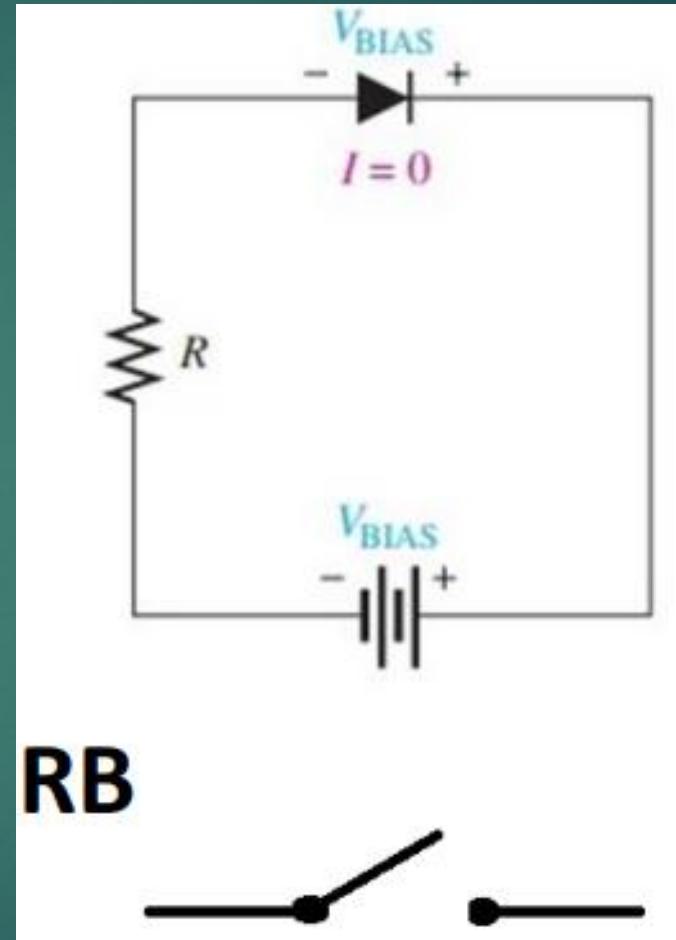
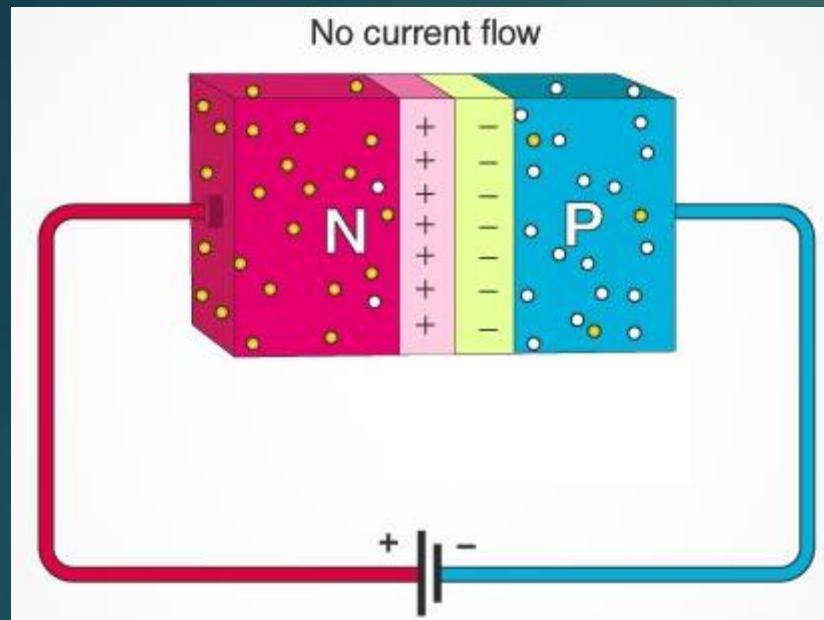


**RB**

# Resistor I-V Characteristics

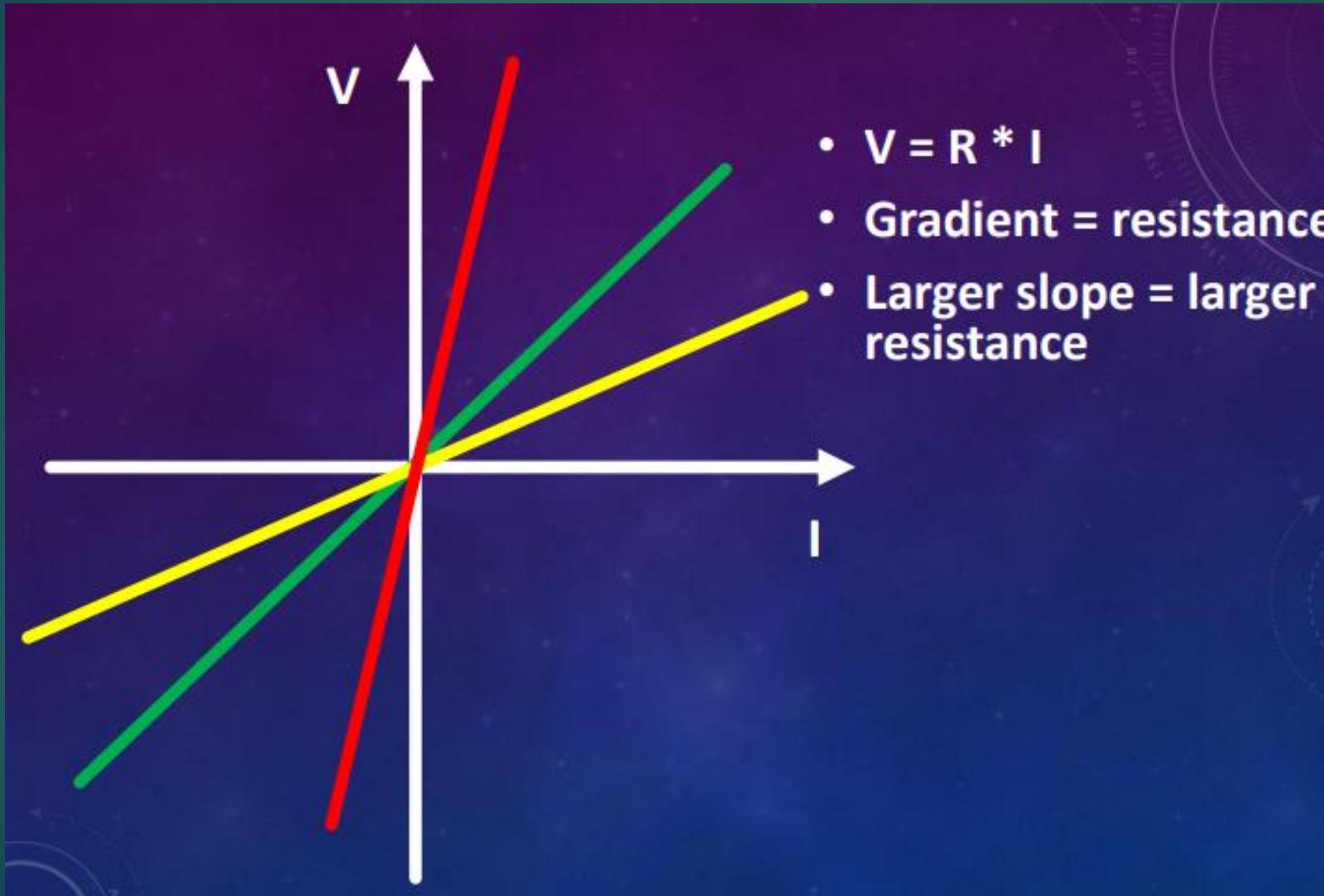


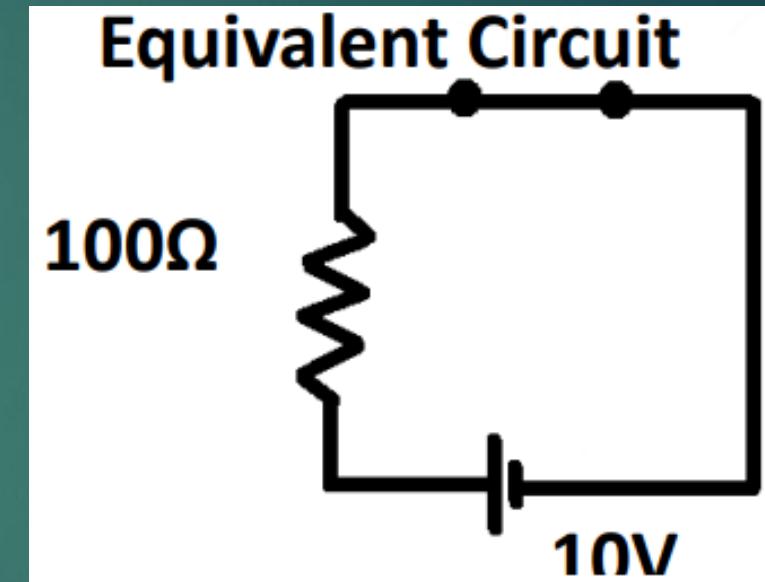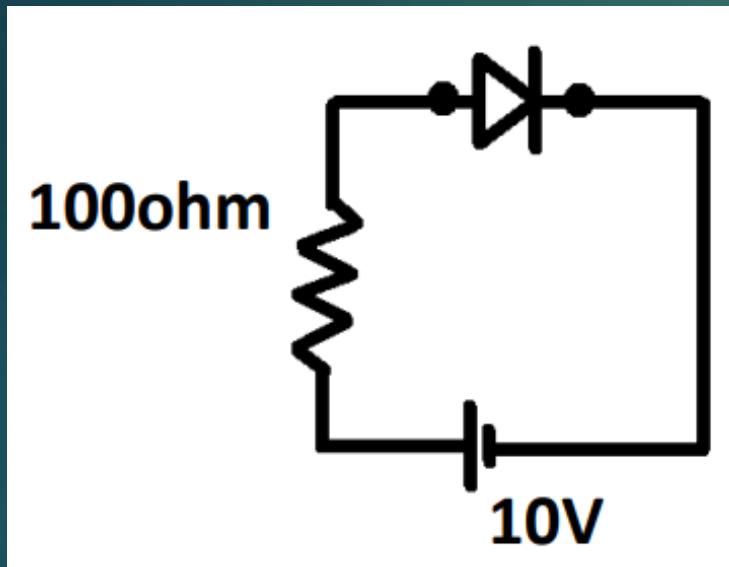Q3) Considering the diode is a ideal one, calculate the current through the diode. Then draw an equivalent circuit and graph.




$$\begin{aligned}I &= V/R \\&= 10/100 \\&= 0.1A\end{aligned}$$

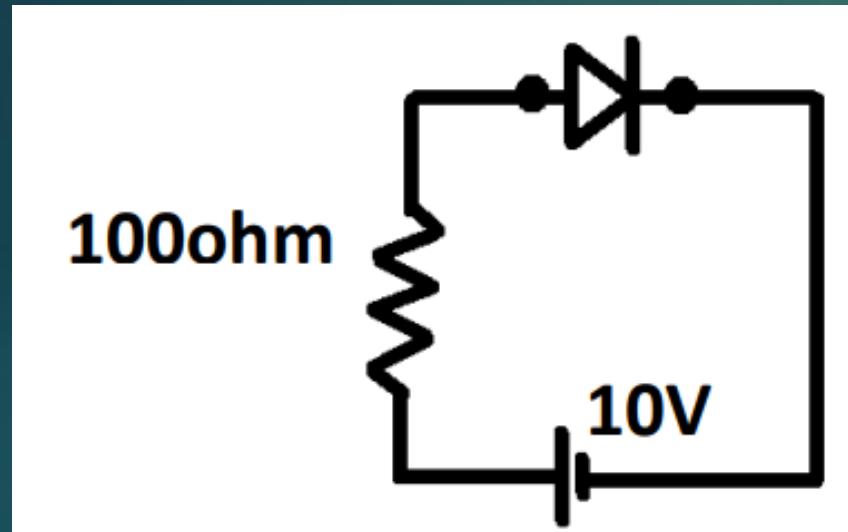
Q4) Calculate the current through the Si diode. Then draw an equivalent circuit and graph. (0.7 V Silicon)




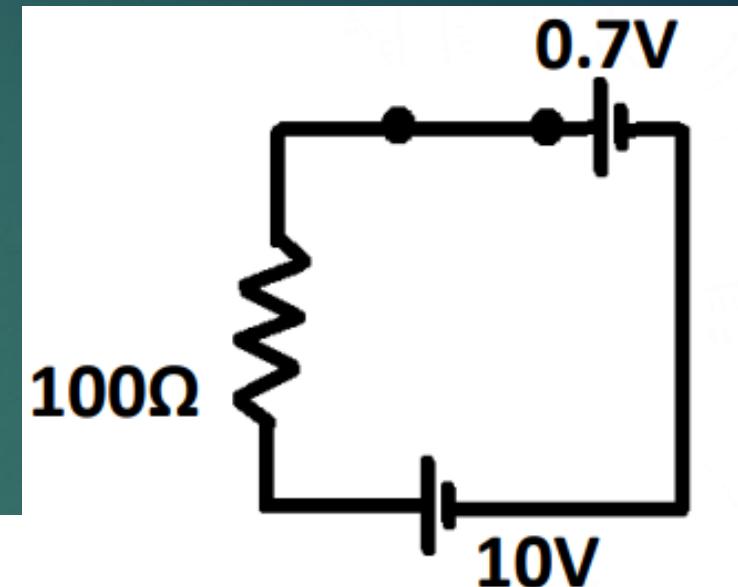
$$\begin{aligned}I &= V/R \\&= (10-0.7)/100 \\&= 0.093A\end{aligned}$$



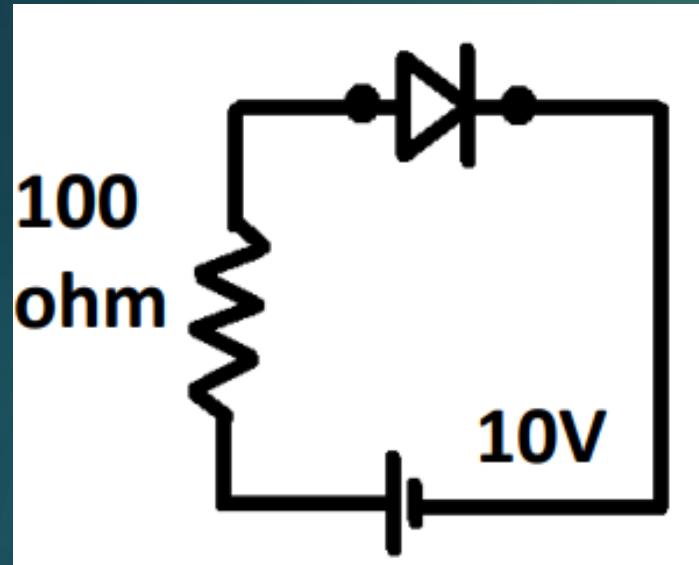
Q5) Calculate the current through the Si diode when the diode has a resistance of 25 ohm. Then draw an equivalent circuit and graph.


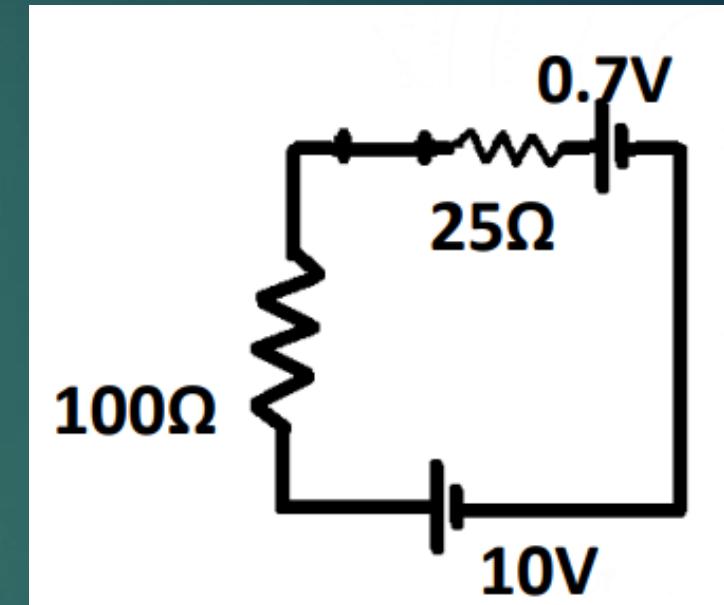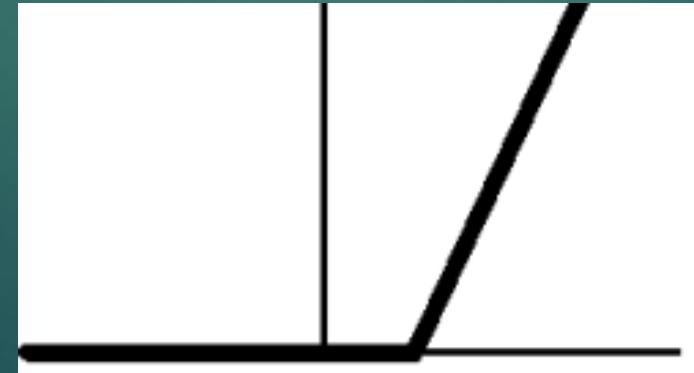
$$\begin{aligned}I &= V/R \\&= (10-0.7)/(100+25) \\&= 0.074A\end{aligned}$$



# Diode I-V Characteristics

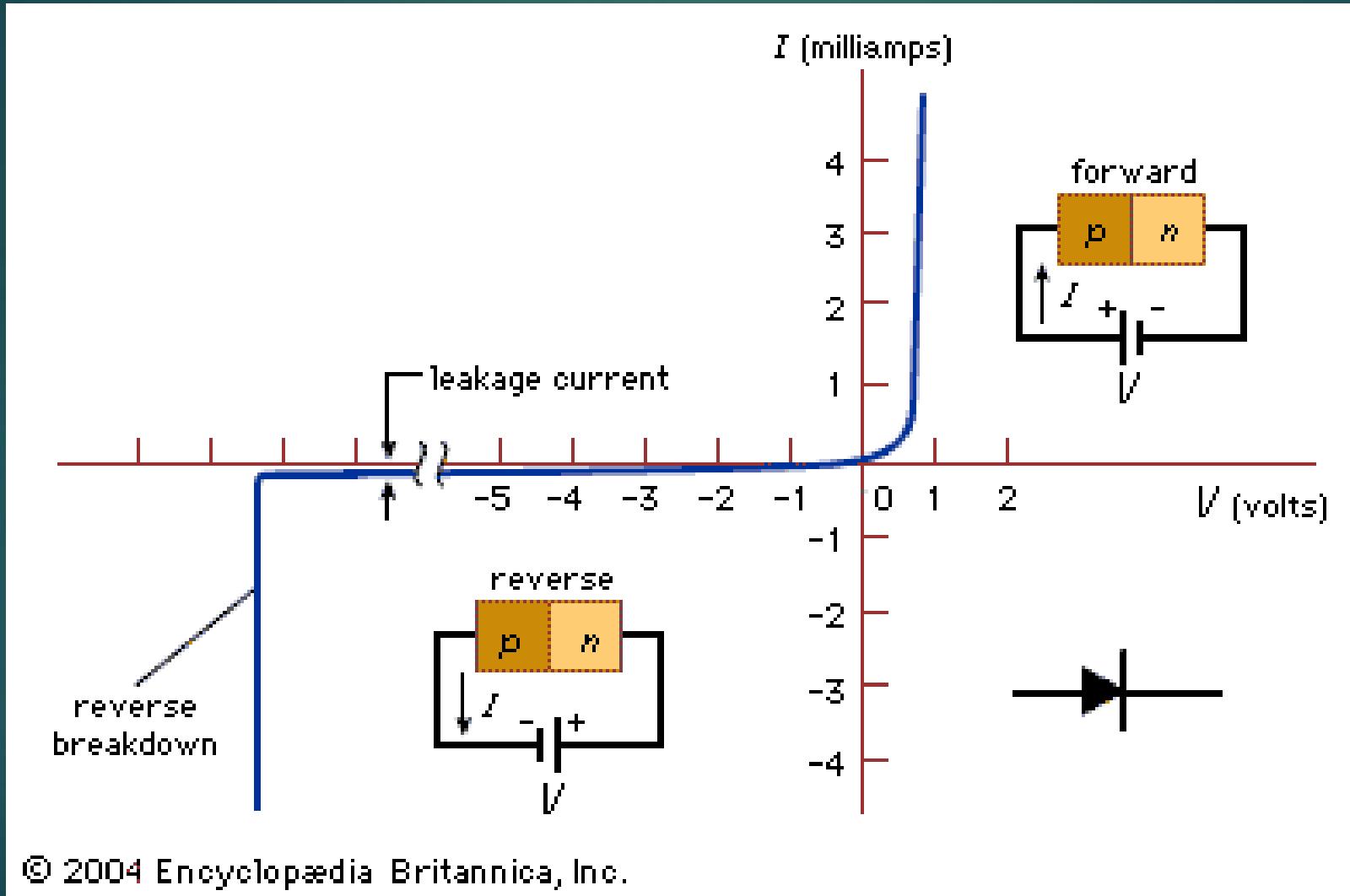

# Applications

1. **Rectifier Diode:** A rectifier diode is a kind of diode that is used for the rectification of current (A.C.).
2. **LED:** LEDs are diodes used for providing light.
3. **Zener Diode:** Zener diode is used for the stabilization of current and voltage in electronic systems.
4. **Photodiode:** Photodiodes are used to detect light.
5. **Switching Diode:** Switching diodes are used for providing fast switching in circuits.
6. **Tunnel Diode:** A tunnel diode is a special type used in the negative resistance region.

# Common Diodes

## 1N4001-7 silicon power diode

Characteristic	Symbol	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Unit
Peak Repetitive Reverse Voltage	$V_{P(VM)}$								
Working Peak Reverse Voltage	$V_{R(VM)}$	50	100	200	400	600	800	1000	V
DC Blocking Voltage	$V_R$								
RMS Reverse Voltage	$V_{R(RMS)}$	50	70	140	280	420	560	700	V
Average Rectified Output Current (Note 1) @ $T_A = +75^\circ\text{C}$	$I_O$				1.0				A
Non-Repetitive Peak Forward Surge Current 8.3ms Single Half Sine-Wave Superimposed on Rated Load	$I_{FSM}$				30				A
Forward Voltage @ $I_F = 1.0\text{A}$	$V_{FM}$				1.0				V
Peak Reverse Current @ $T_A = +25^\circ\text{C}$ at Rated DC Blocking Voltage @ $T_A = +100^\circ\text{C}$	$I_{RM}$				5.0				$\mu\text{A}$
					50				
Typical Junction Capacitance (Note 2)	$C_J$		15			8			pF
Typical Thermal Resistance Junction to Ambient	$R_{\theta JA}$			100					K/W
Maximum DC Blocking Voltage Temperature	$T_A$			+150					$^\circ\text{C}$
Operating and Storage Temperature Range	$T_J, T_{STG}$			-65 to +150					$^\circ\text{C}$

Notes:

1. Leads maintained at ambient temperature at a distance of 9.5mm from the case.
2. Measured at 1.0 MHz and applied reverse voltage of 4.0V DC.
3. EU Directive 2002/95/EC (RoHS). All applicable RoHS exemptions applied, see EU Directive 2002/95/EC Annex Notes.

# Common Diodes

- 1N4001-7 silicon power diode
- 1N34, 1N34A Detector Diodes
- 1N4448 silicon signal diode
- MPN3404 (or BA479) PIN diode
- KV1360NT variable capacitance diode (varicap)

# Replacement and Equivalent

You can replace the 1N4004 with the

RL207, RL206, RL205, RL204, HER208, HER207, HER206, HER205, HER158, HER157,  
HER156, HER155, HER108, HER107, HER106, HER105, FR207, FR206, FR205, FR204, FR157,  
FR156, FR155, FR154, FR107, FR106, FR105, FR104, EM520, EM516, EM513, BY133, 1U8, 1U7,  
1U6, 1U5, 1N5399, 1N5398, 1N5397, 1N5395, 1N4937, 1N4936, 1N4007, 1N4006, 1N4005, 1A7,  
1A6, 1A5, 1A4, SF16, SF18, SF26, SF28, UF4004, UF4005, UF4006, UF4007, 1N4004G,  
1N4005G, 1N4006G, 1N4007G, 1N4936G, 1N4937G

# **EE3301 Analog Electronics**

## **DC power Supplies and Regulation Circuits**

**Neel Karunasena**

**[neelk@eie.ruh.ac.lk](mailto:neelk@eie.ruh.ac.lk)**

**Department of Electrical & Information Engineering**

**Faculty of Engineering University of Ruhuna**

# 2.0 Rectifiers

- ▶ “Rectify”
  - ❖ To set right, make one directional
- ▶ “Rectifier”
  - ❖ It rectifies
  - ❖ Permits current to flow through it in one direction only
- ▶ Peak Inverse Voltage (PIV)
  - ❖ Maximum permissible reverse biased voltage that the diode can withstand without a breakdown
  - ❖  $PIV \geq V_p$

# Frequency

- ▶  $f = 1 / T$
- ▶ Angular velocity


$$\omega = 2\pi f$$



# Rectifiers

Half - Wave  
Rectifiers

Full - Wave  
Rectifiers

## 2.1 Half- Wave Rectifiers

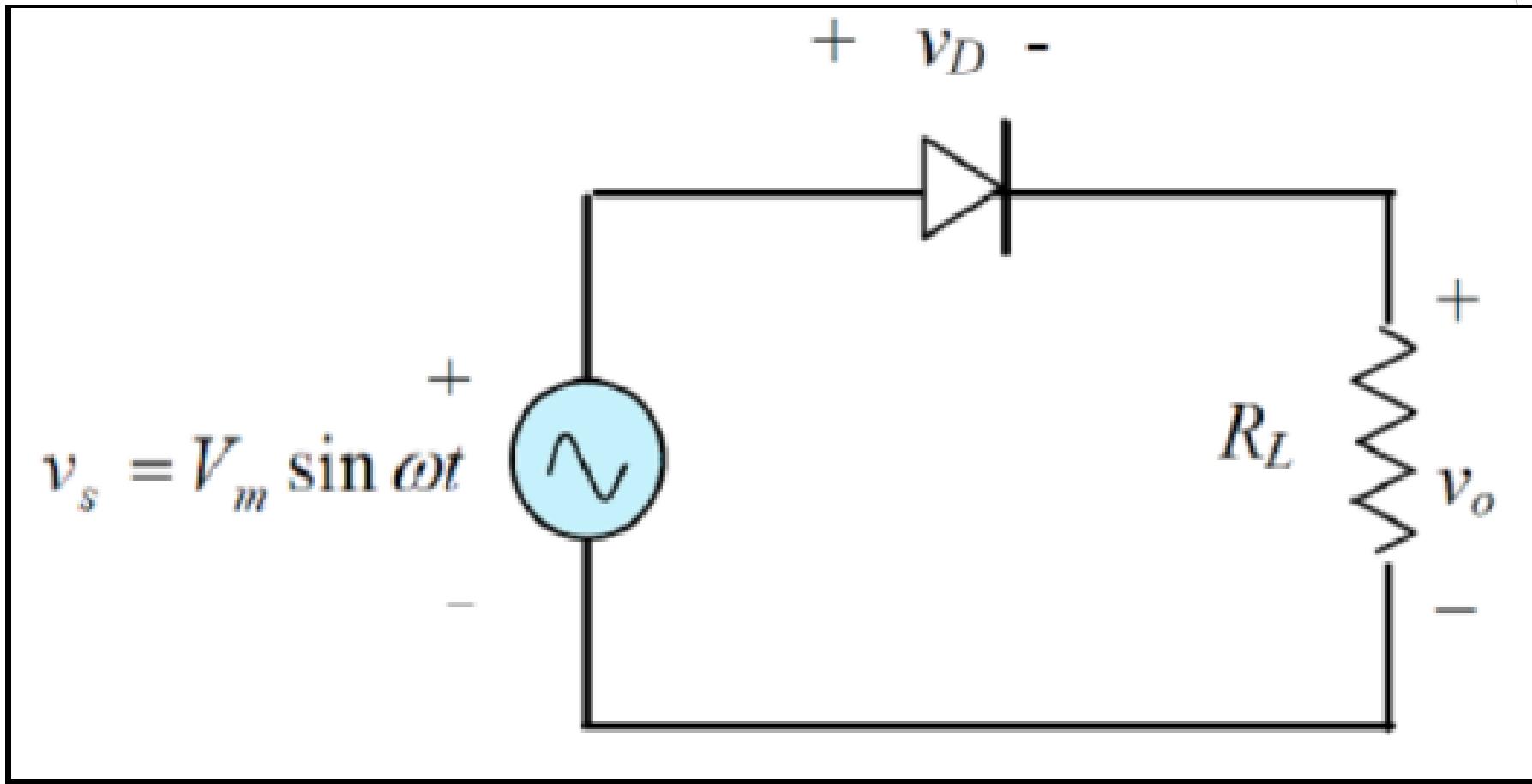


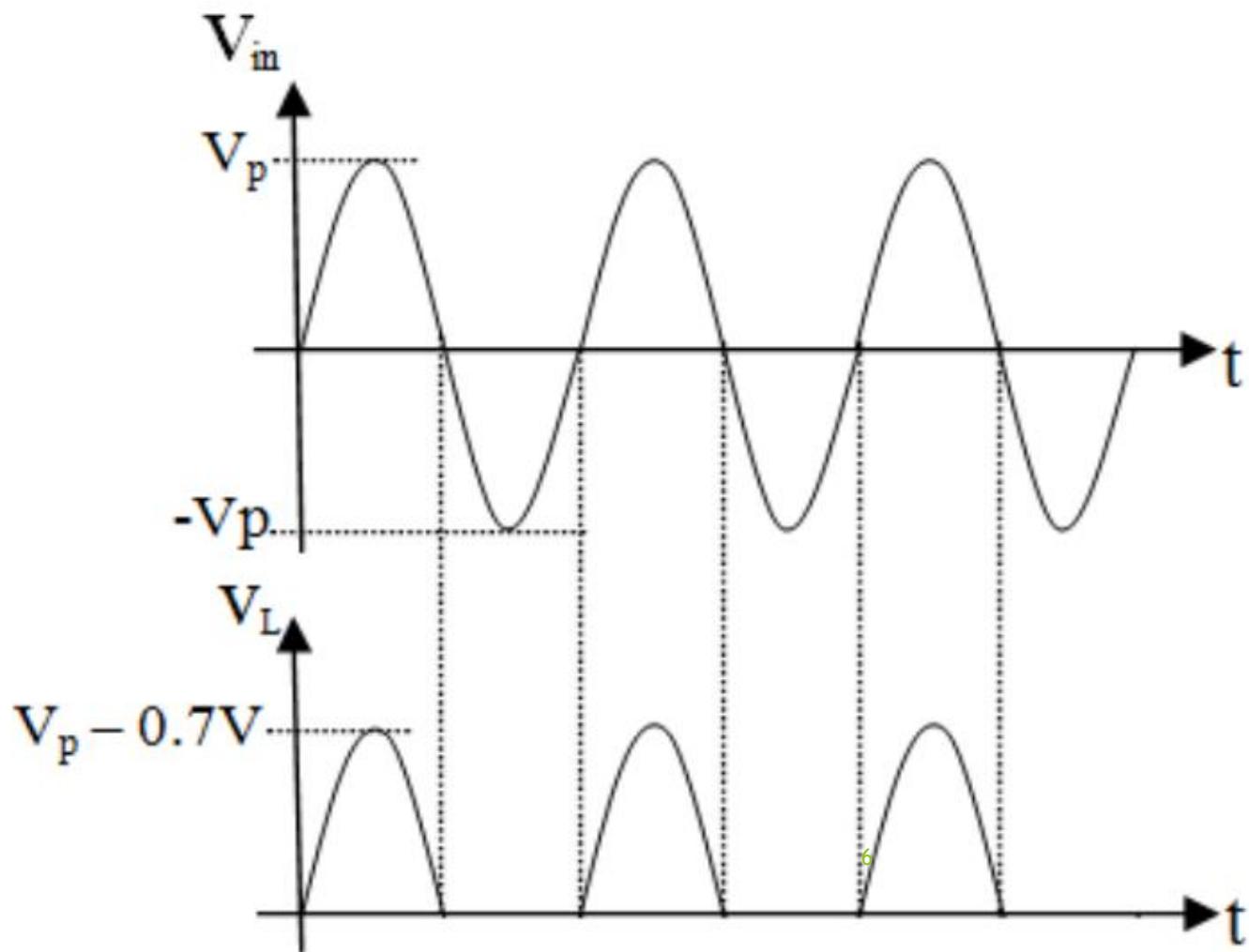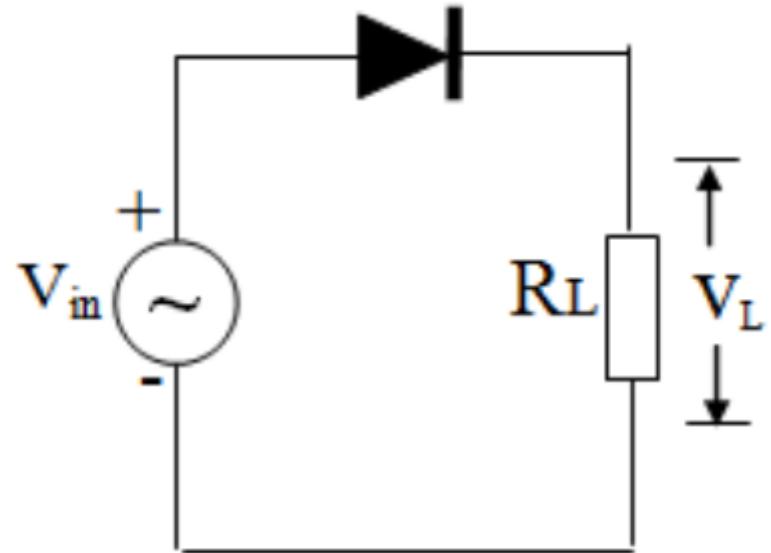

- ▶ AC waveform, One diode
- ▶ During the positive half cycle
  - ▶ Diode is forward biased
- ▶ Conduct all instantaneous voltages greater than the cutting voltage
- ▶  $V_{PR} = V_p - 0.7$ 

Where;  $V_{PR}$  = peak value of rectified voltage
- ▶ During the negative half cycle
  - ▶ Diode is reverse biased
  - ▶ No voltage output
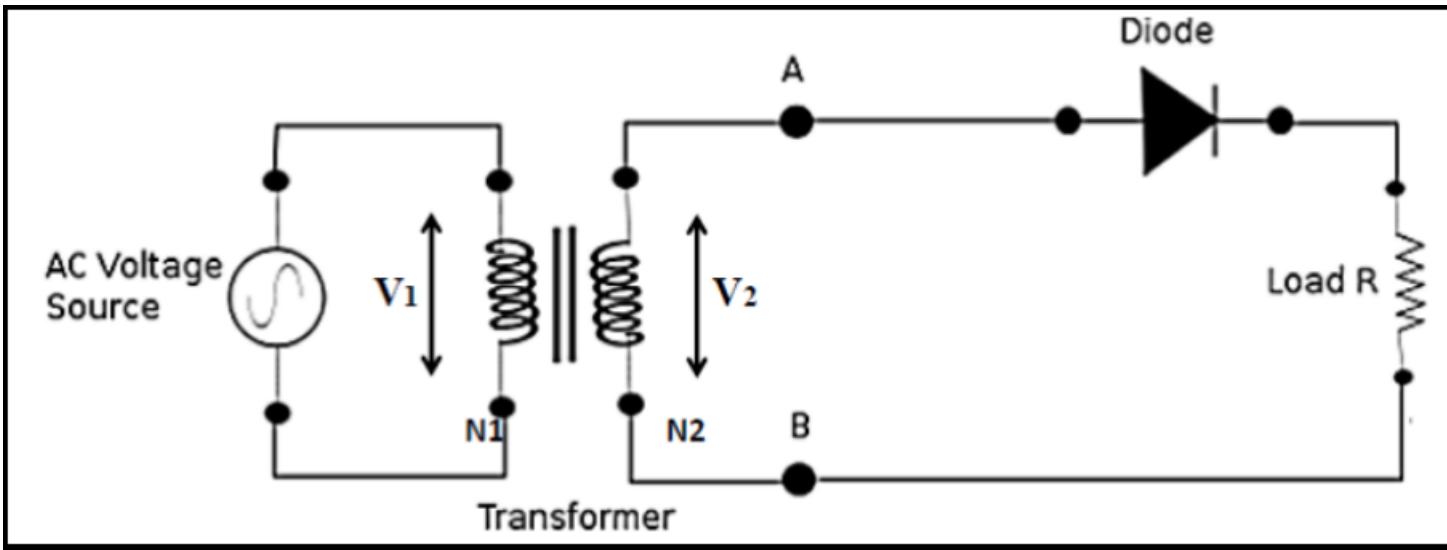
## 2.2 HWR with Transformer coupled input



- ▶  $V_2 / V_1 = ?$
- ▶  $V_1$  - rms value of primary voltage
- ▶  $V_2$  - rms value of secondary voltage
- ▶  $N_1$  - No. of turns in the primary winding
- ▶  $N_2$  - No. of turns in the secondary winding


- ▶ Advantages....

- ▶ AC source is electrically isolated from the load
- ▶ Allows source voltage step up or step down

# Average and RMS values

- ▶ RMS – Root mean square
- ▶ RMS gives you the equivalent DC voltage for the same power
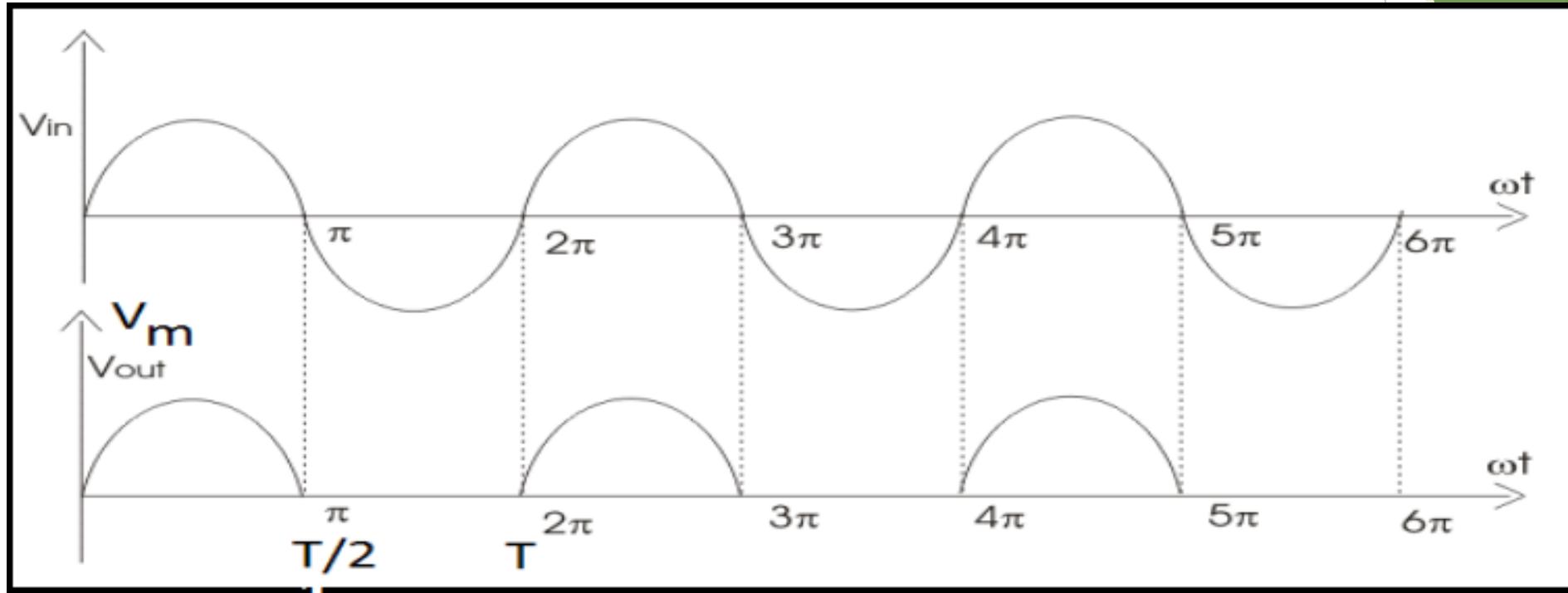
## 2.3 Calculate the Average and RMS of HWR



◆ Period  $T = 2\pi$ ,  $f = 1/2\pi$


◆  $f_{out} = f_{in}$

$$\diamond V_{avg} = \frac{1}{T} \int_0^T v(t) dt \longrightarrow V_{avg} = \frac{V_m}{\pi}$$


$$\diamond V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt} \longrightarrow V_{rms} = \frac{V_m}{2}$$
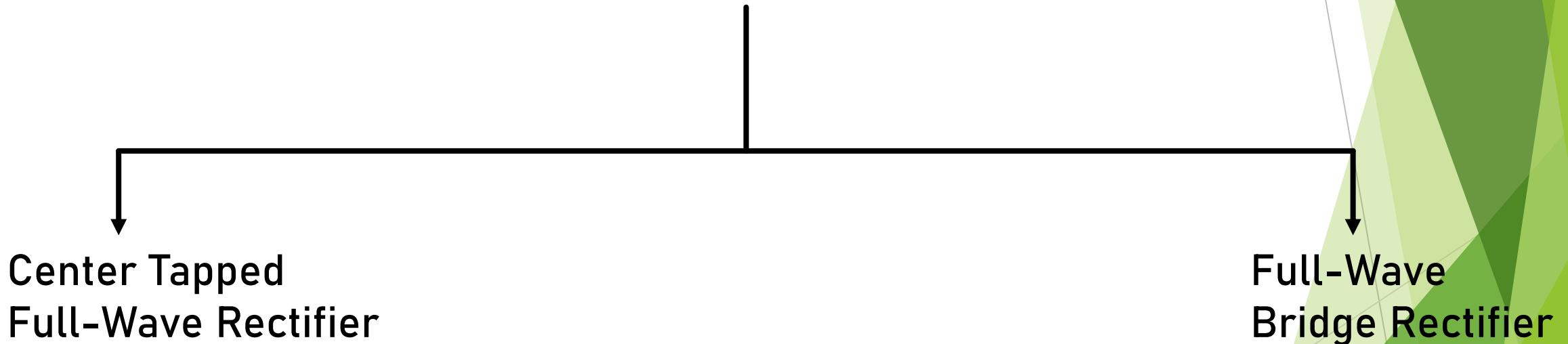
## 2.4 Full Wave Rectifiers


- ▶ A full-wave rectifier is a circuit that allows a unidirectional current to flow through the load during the ENTIRE input cycle.


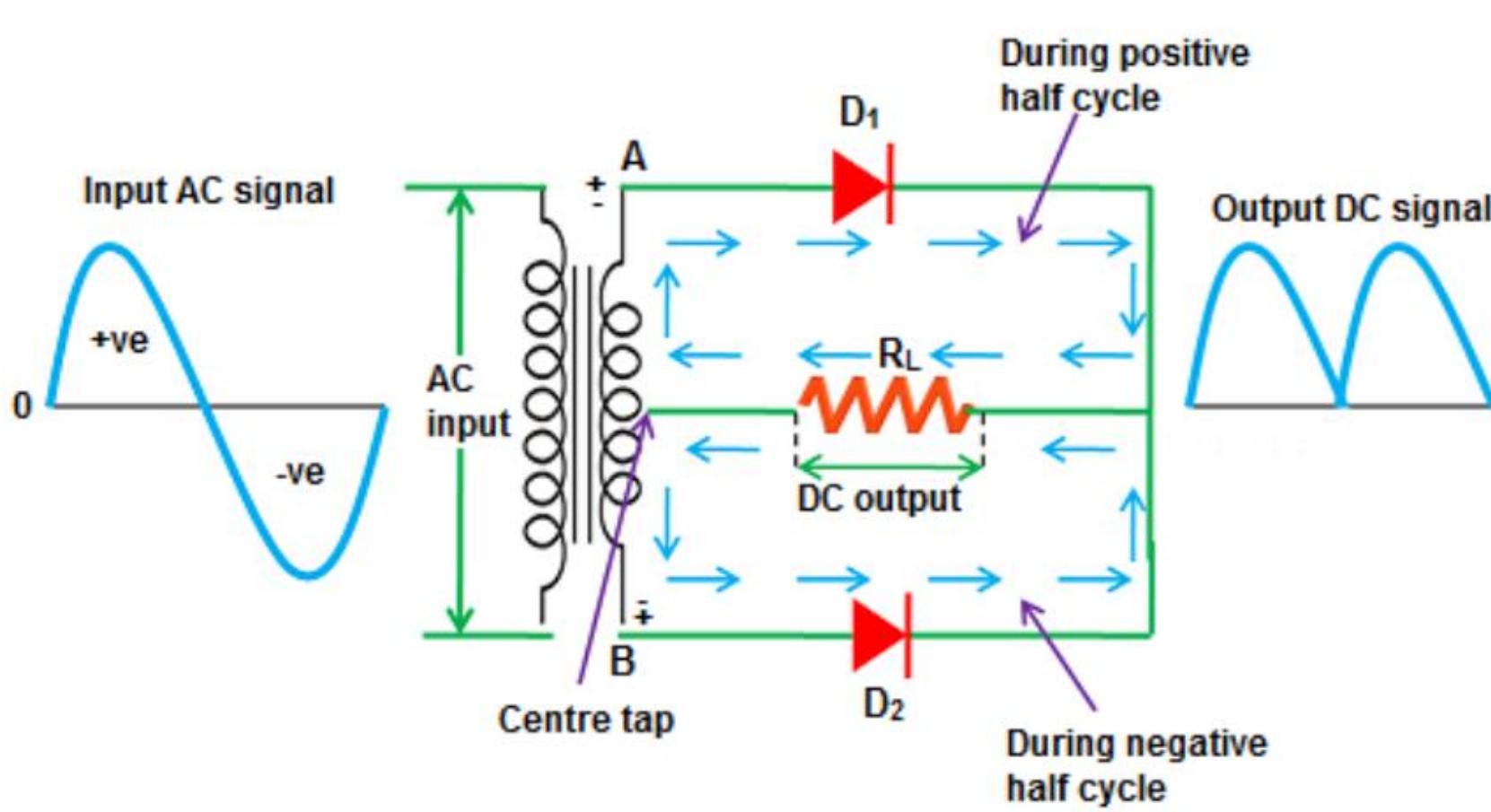
## 2.4.1 Center Tapped Full-Wave Rectifier



## 2.4.2 Full-Wave Bridge Rectifier

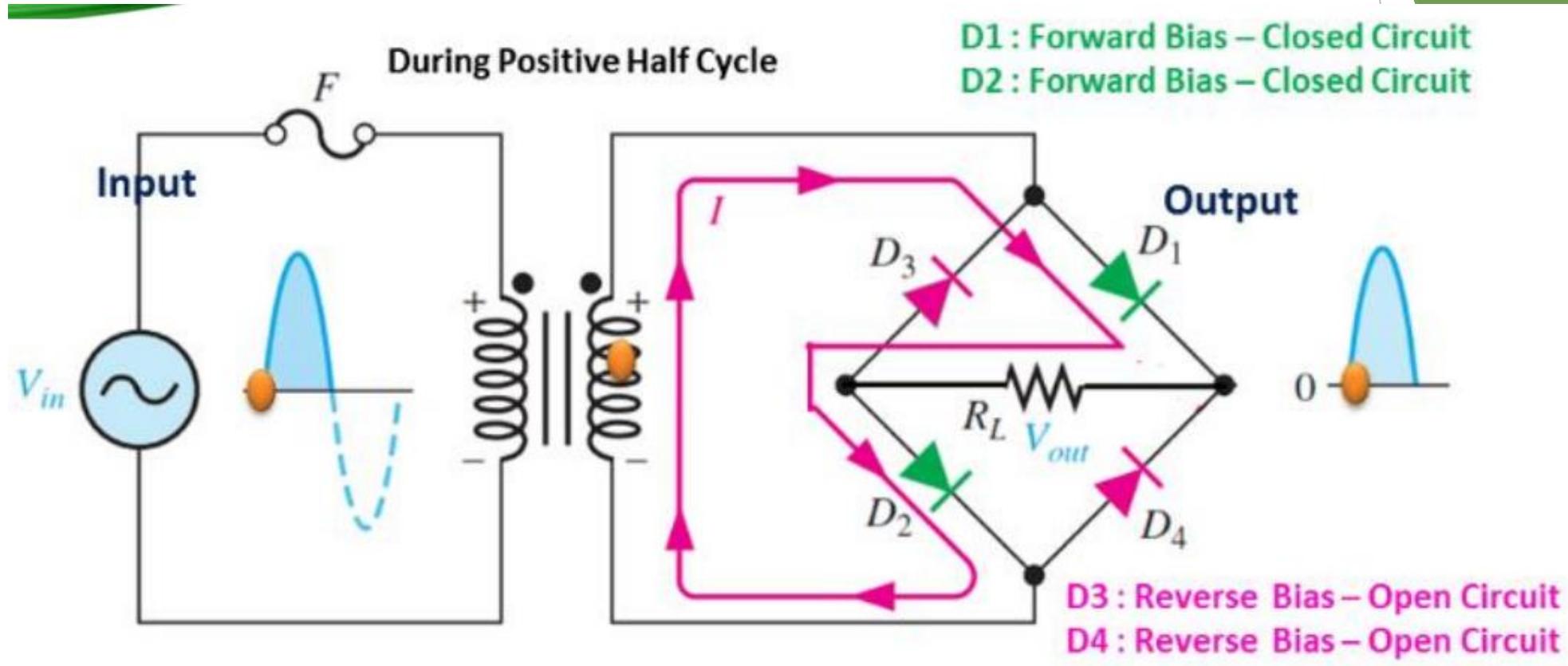

$$V_{PR} = V_p - 1.4$$

## 2.5 Calculate the Average and RMS of FWR


$$\diamond V_{avg} = \frac{1}{T} \int_0^T v(t) dt \longrightarrow V_{avg} = \frac{2V_m}{\pi}$$

$$\diamond V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt} \longrightarrow V_{rms} = \frac{V_m}{\sqrt{2}}$$



For a pure sinusoidal waveform ONLY, both the average voltage and the RMS voltage (or currents) can be easily calculated as:

**Average value** =  $0.637 \times$  maximum or peak value,  $V_{pk}$

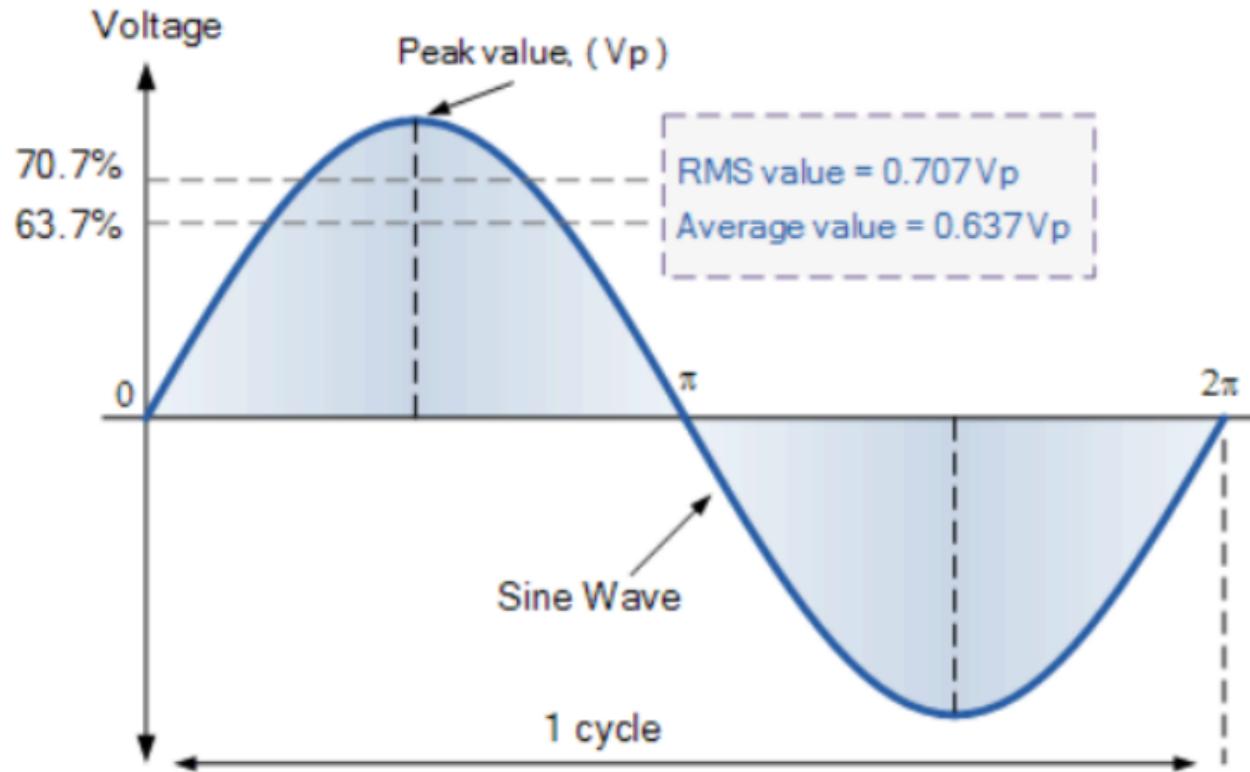
**RMS value** =  $0.707 \times$  maximum or peak value,  $V_{pk}$




# 3. Clipping and Clamping

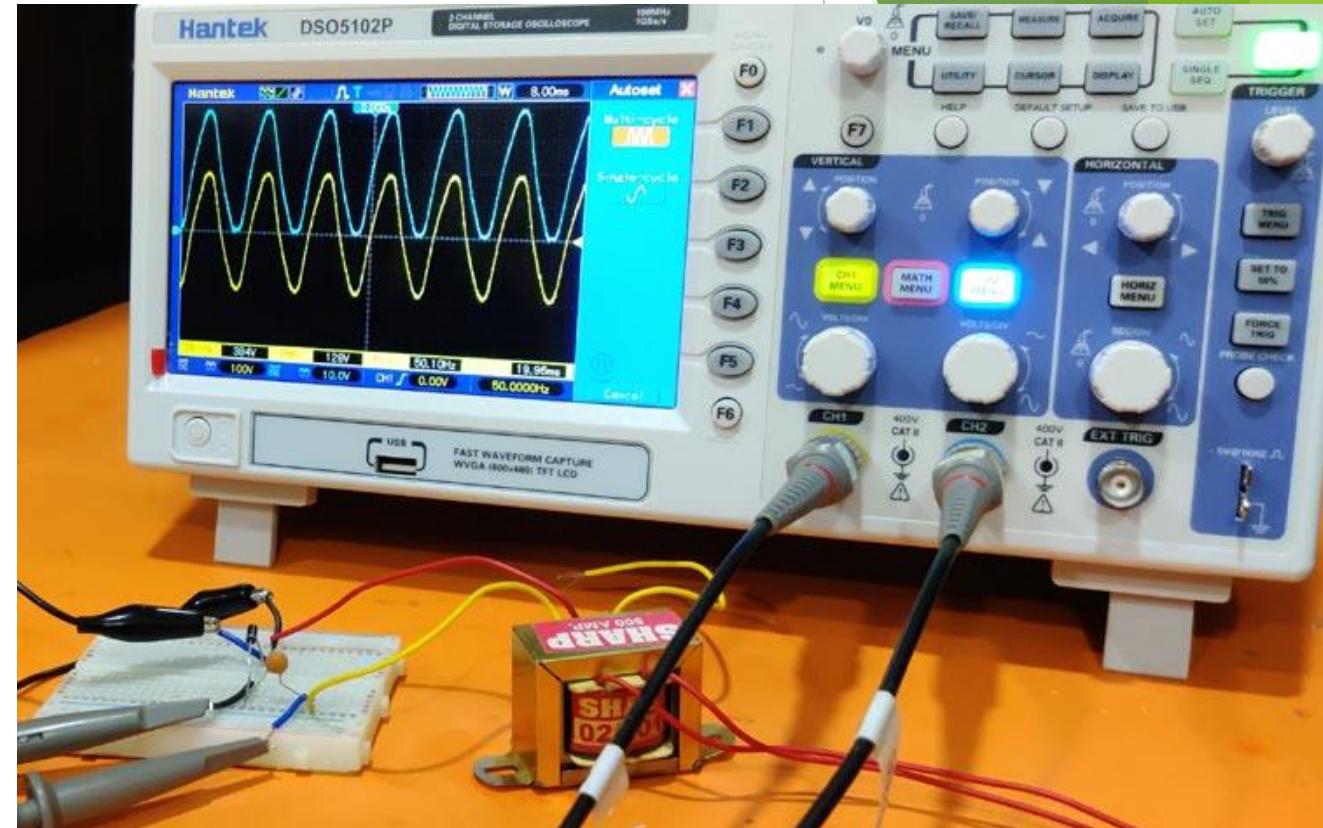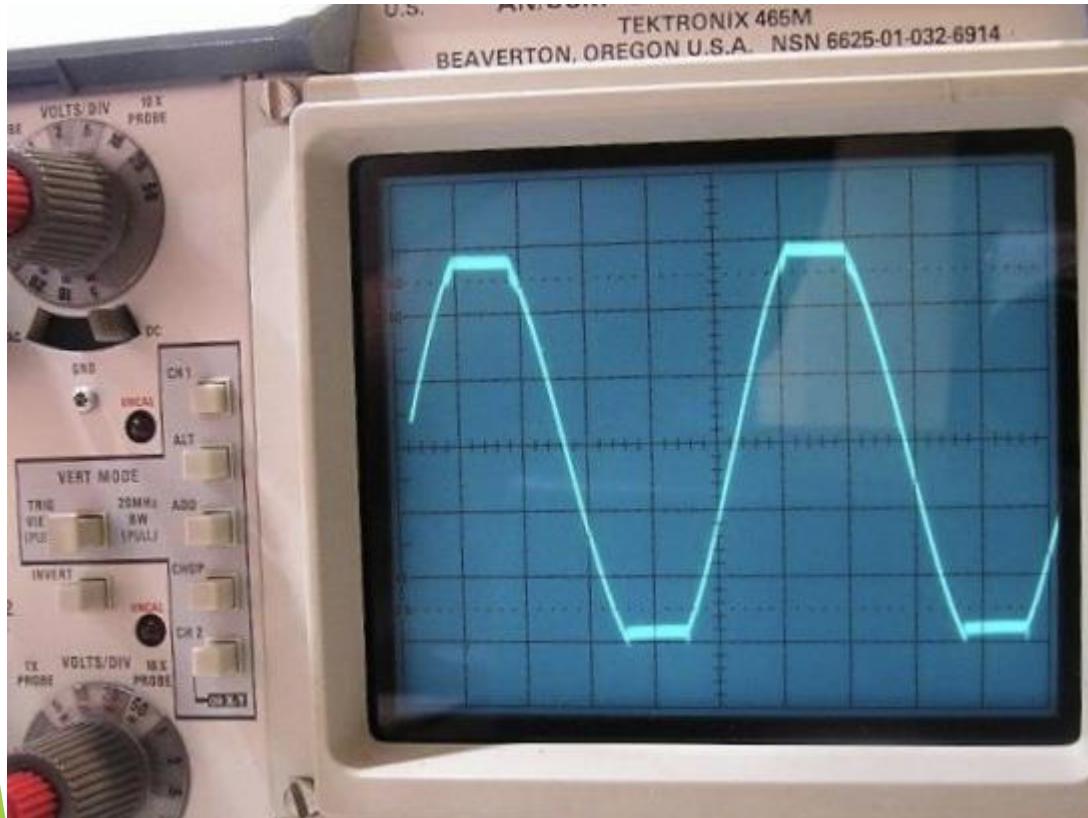


# 3.1 Clipping

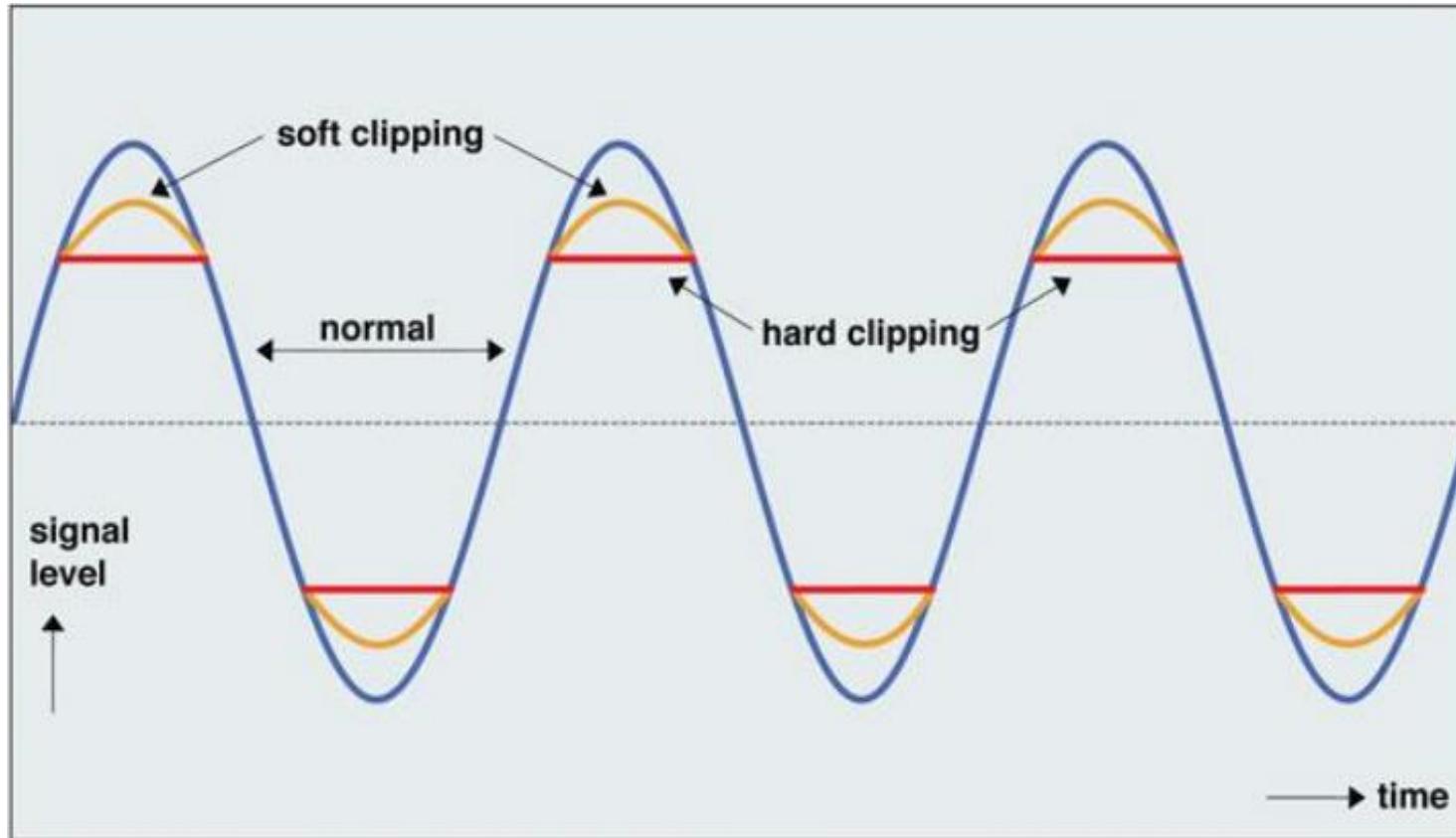

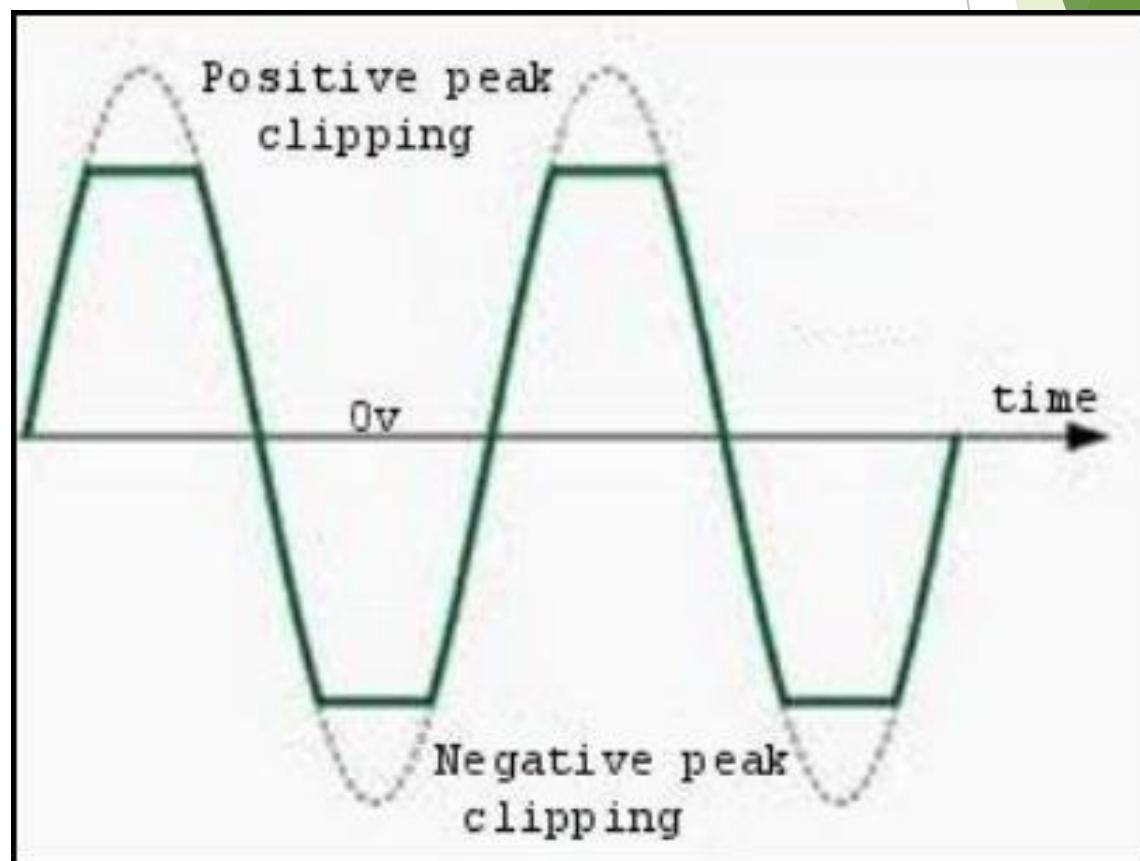- ▶ If the output voltage exceeds a certain level, it limits the tops/ bottoms of a waveform.
- ▶ But does not distort the remaining part of the waveform.
- ▶ Limit the voltage in circuits




## 3.1.2 Clipping Circuits

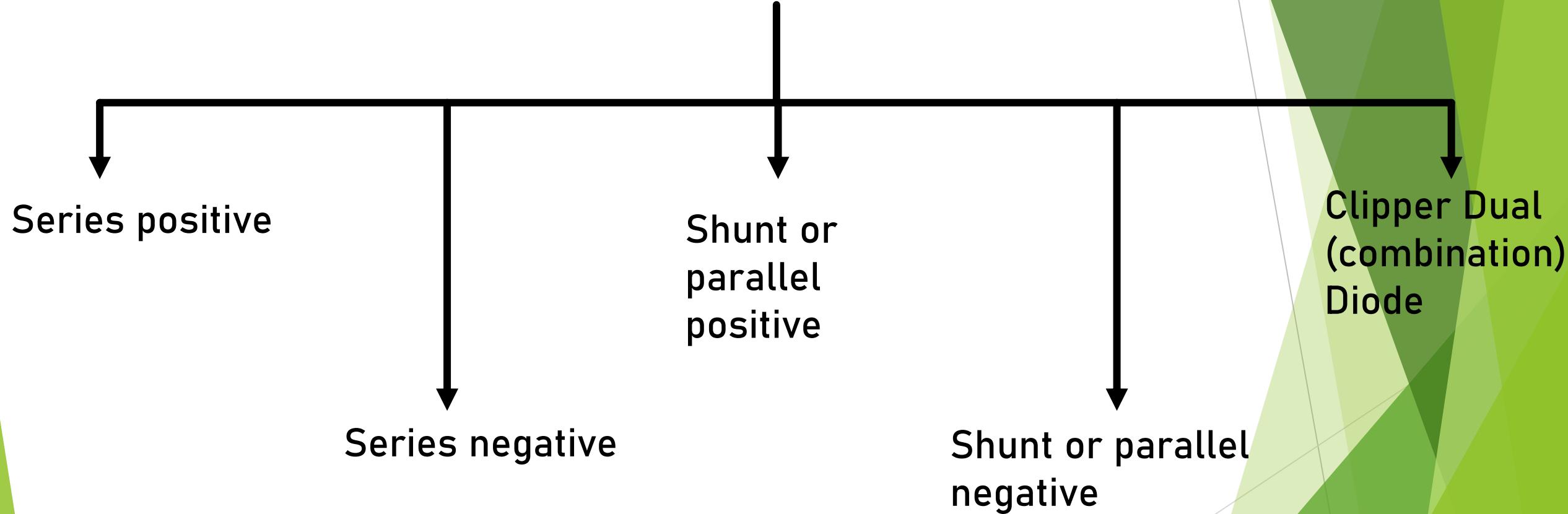
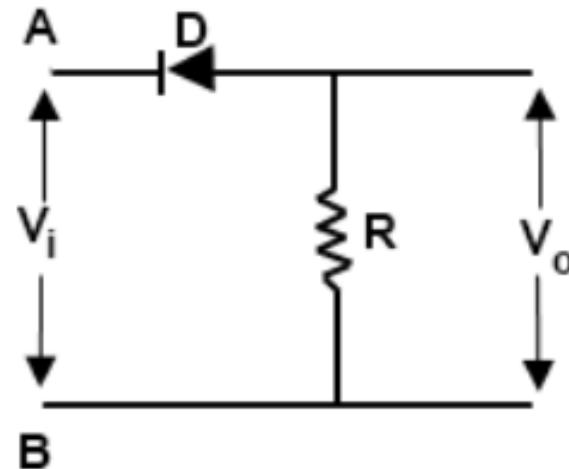
# Series positive Clipper



- In a series positive clipper, a diode is connected in series with the output




(a) Positive Clipper
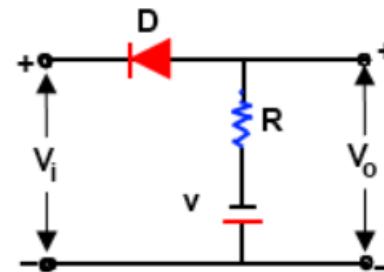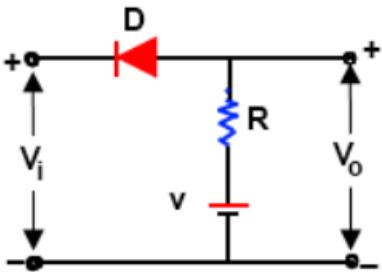
# Series-positive Clipper With Bias



- The clipping takes place during the positive cycle only when the input voltage is greater than the battery voltage (i.e.  $V_i > V$ ). The clipping level can be shifted up or down by varying the bias voltage ( $V$ )



# Series Negative Clipper

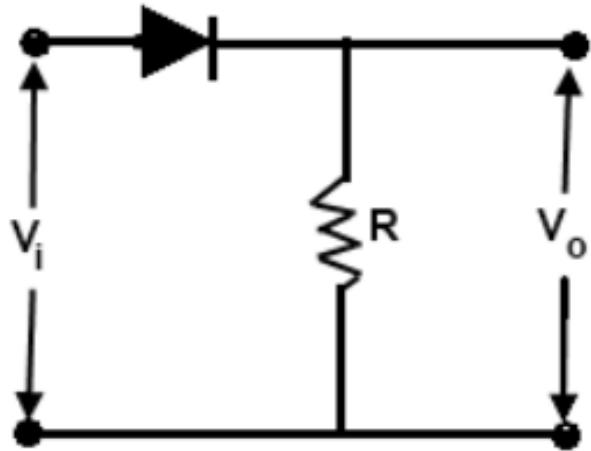


# Series-negative Clipper With Bias

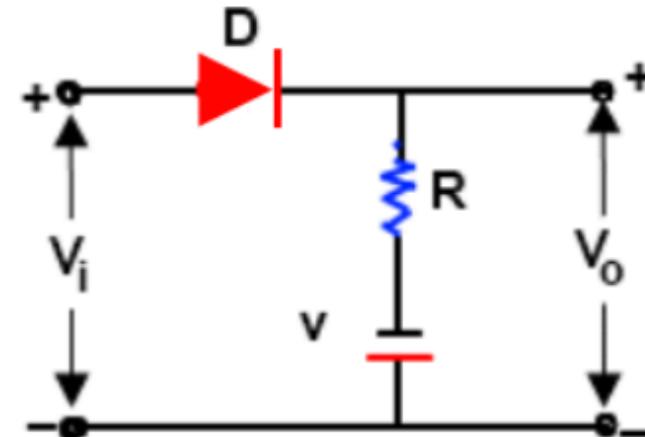
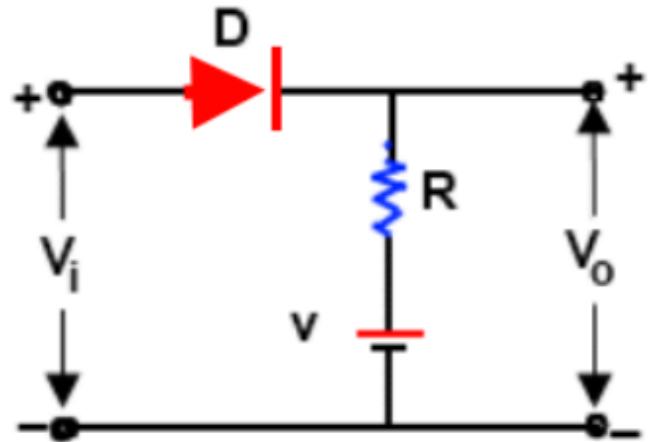

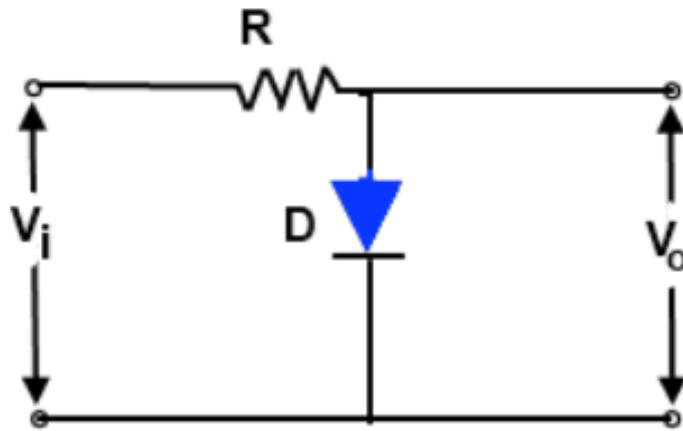
# Shunt Or Parallel Positive Clipper


In shunt clipper, the diode is connected in parallel with the output load.



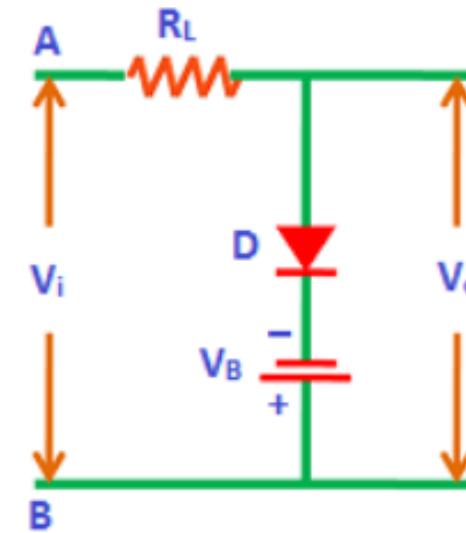
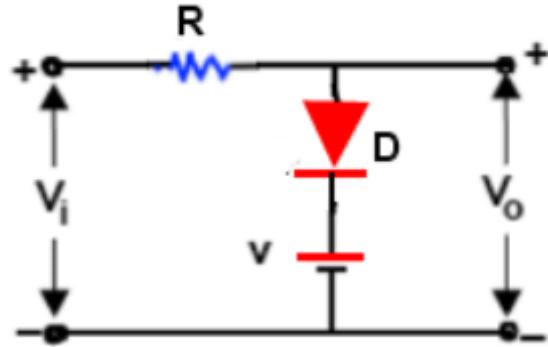
# Shunt Or Parallel Positive Clipper With Bias




# Shunt Or Parallel Negative Clipper

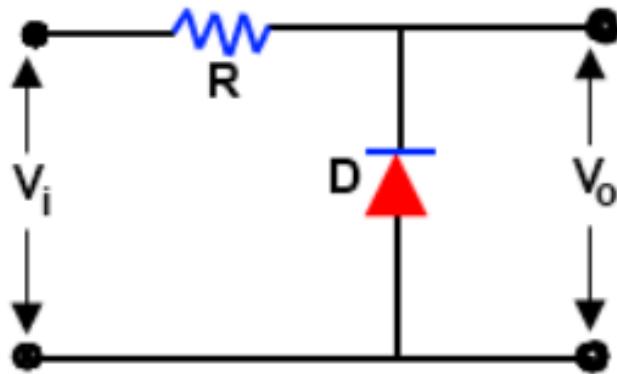
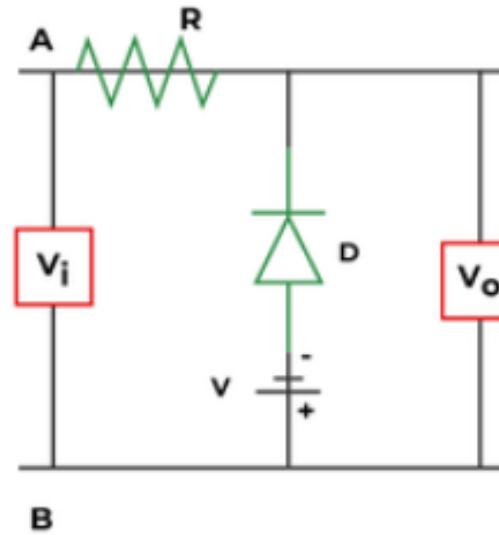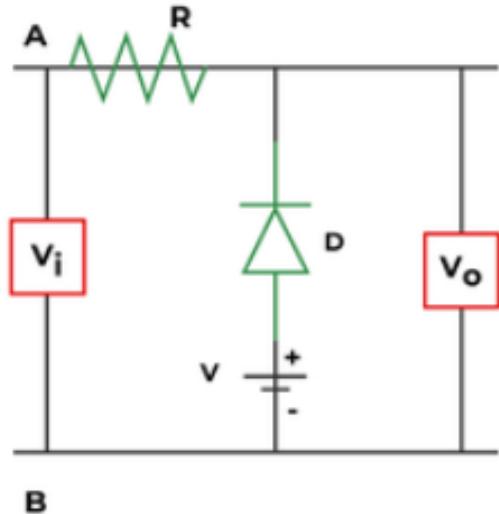
# Shunt Or Parallel Negative Clipper With Bias



# Dual (Combination) Diode Clipper

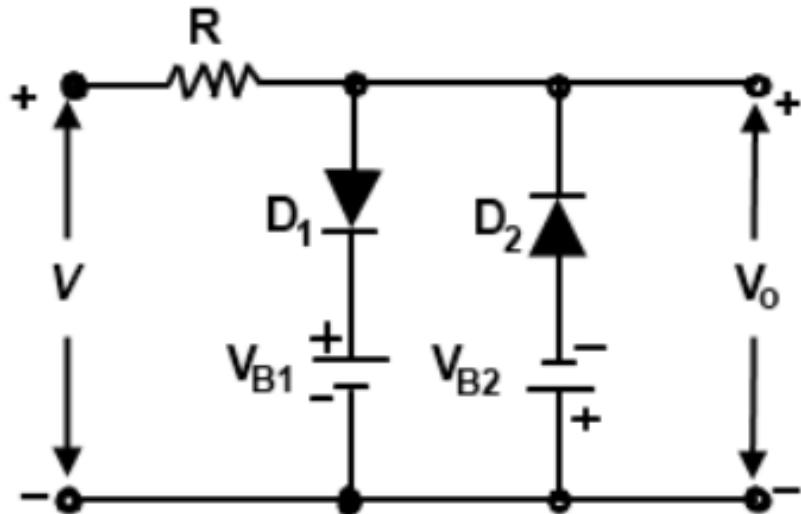

# EE3301 Analog Electronics

## DC power Supplies and Regulation Circuits

Neel Karunasena

[neelk@eie.ruh.ac.lk](mailto:neelk@eie.ruh.ac.lk)

Department of Electrical & Information Engineering

Faculty of Engineering University of Ruhuna

## 4. Filtering and Regulation

- ▶ Device/process to remove unwanted components/features from a signal.
- ▶ Removes the ripples from the rectified output
- ▶ Most common: c-filter (capacitor) – allows AC and blocks DC
  - ▶ Charge: when input voltage is higher than  $V_c$
  - ▶ Discharge: when input voltage is lower than  $V_c$

# Ripple Factor

3

- A measure of the purity of the DC output
- Want it to be as small as possible

$$r = \frac{\text{rms of AC component of output}}{\text{Avg value of output}}$$

$$r = \frac{V_{AC\text{rms}}}{V_{DC}}$$

$$r = \frac{\sqrt{V_{rms}^2 - V_{DC}^2}}{V_{DC}} = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$$

Can also be given as  $r = \frac{I_{AC}}{I_{DC}}$

# Ripple Factor of Half Wave Rectifier

- HWR

$$r = \sqrt{\left(\frac{V_m/2}{V_m/\pi}\right)^2 - 1}$$

$$r = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1}$$

$$r = 1.211$$

Percentage Ripple =  
121.1%

# Ripple Factor of Full Wave Rectifier

- FWR

$$r = \sqrt{\left(\frac{V_m/\sqrt{2}}{2V_m/\pi}\right)^2 - 1}$$


$$r = \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1}$$

$$r = 0.483$$

- Percentage Ripple = 48.3%

# HWR with Smoothing Capacitor

6

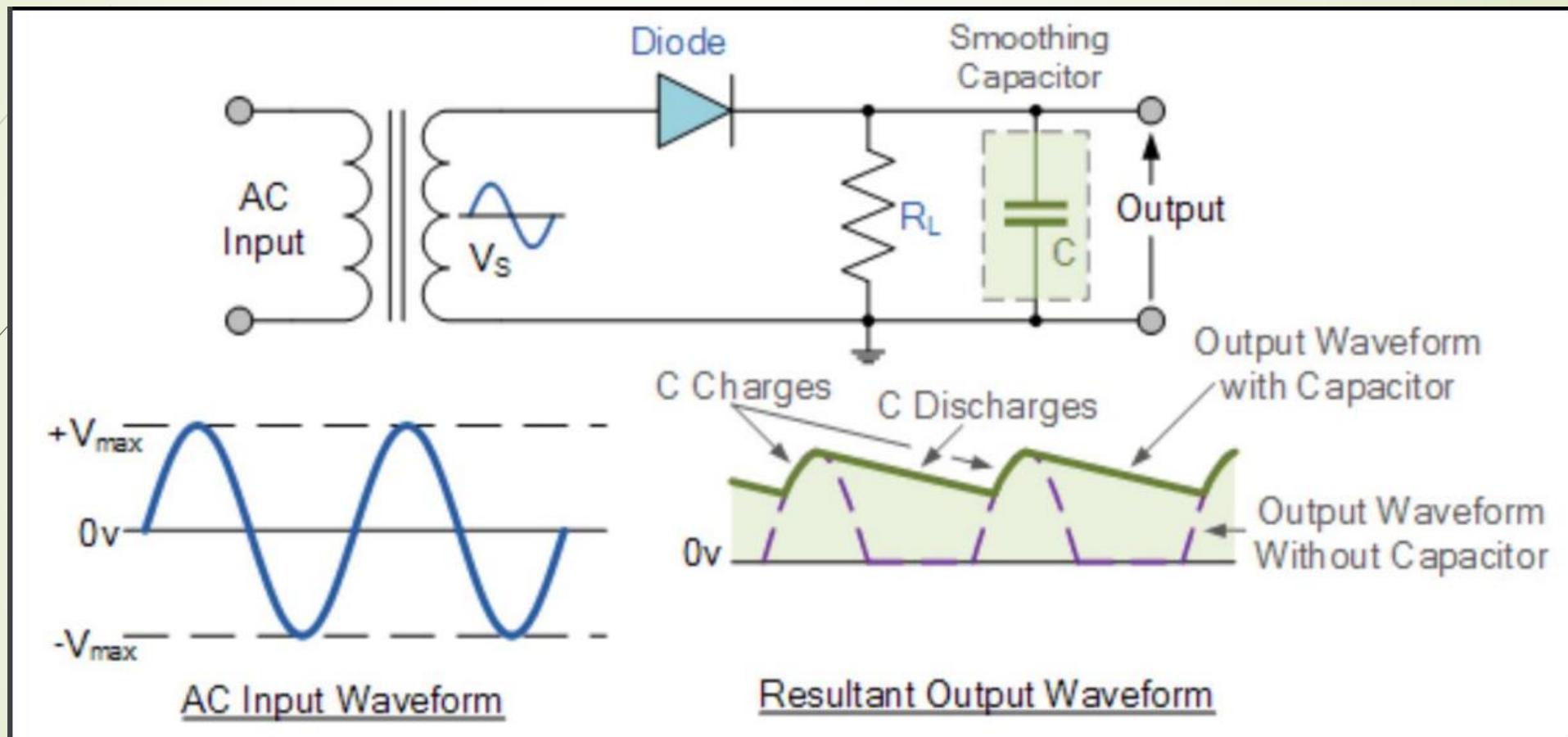

# Rectifiers with RC filters


7

## Assumptions

- ▶ Ripple voltage is small as compared to the dc component
- ▶ Capacitor voltage does not decay significantly from its peak value between the rectified pulses that recharge the capacitor
- ▶ Saw tooth waveform ( $V_{pp}$ )
  - Capacitor charges instantly
  - Voltage decays linearly

**Note:**  
**Circuit Design:  $f$  and  $R$  fixed. Select  $C$  such that ripple is minimized**

# FWR with Smoothing Capacitor

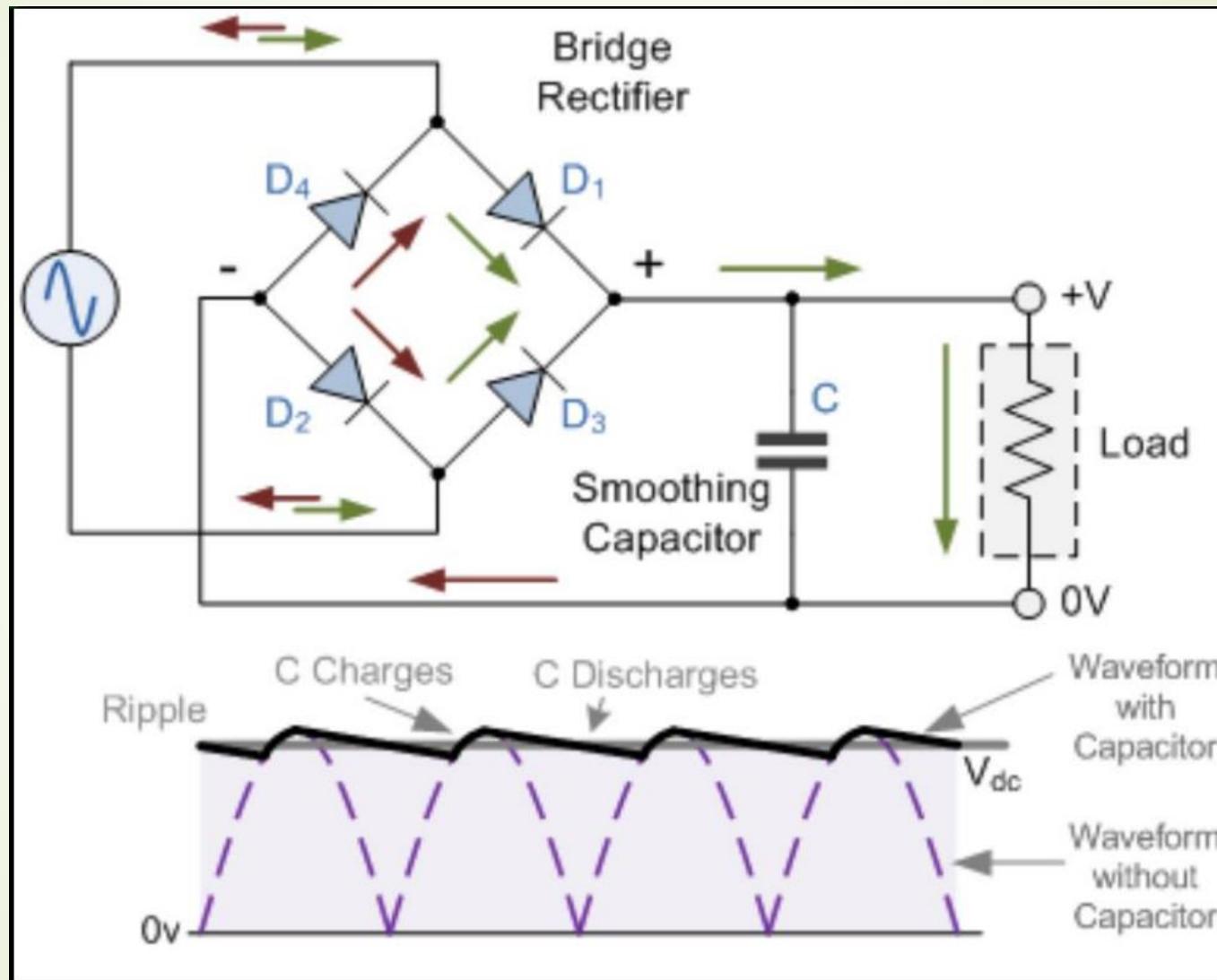

# EE3301 Analog Electronics

## DC power Supplies and Regulation Circuits

Neel Karunasena



[neelk@eie.ruh.ac.lk](mailto:neelk@eie.ruh.ac.lk)

Department of Electrical & Information Engineering

Faculty of Engineering University of Ruhuna

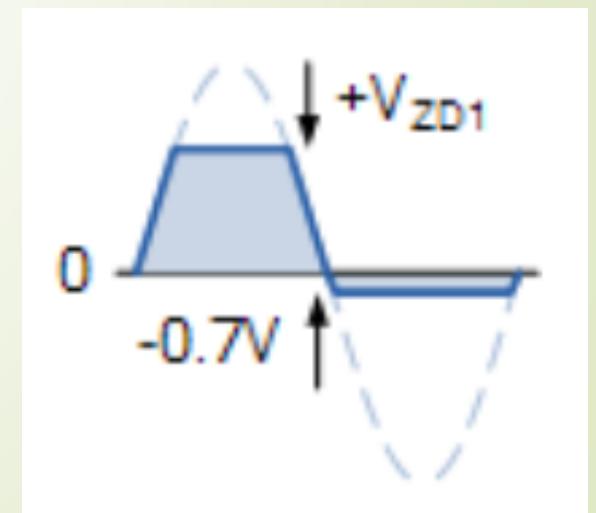
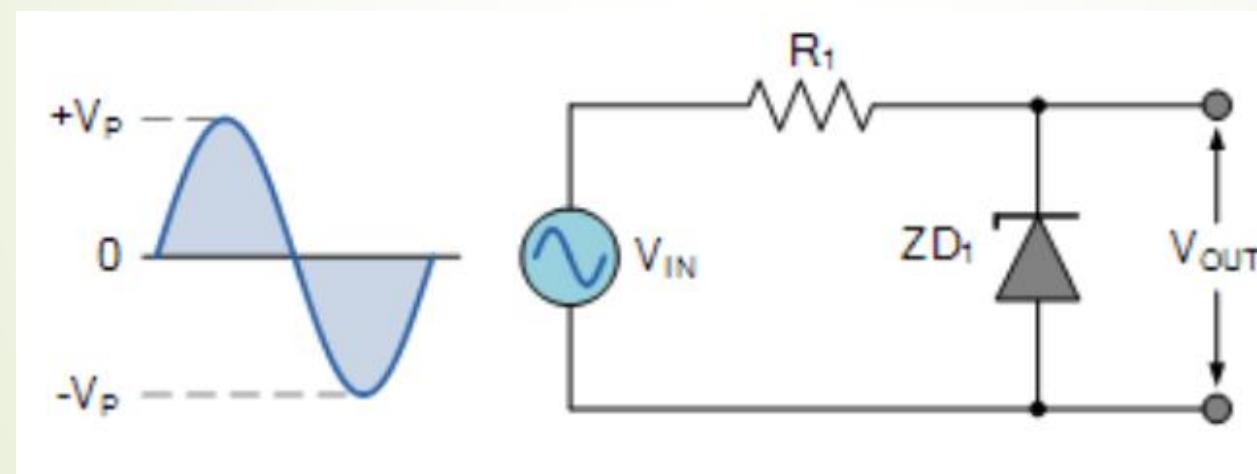
# Zener Diode Clipping

The Zener diode acts like a biased diode clipping circuit with the bias voltage being equal to the Zener breakdown voltage.


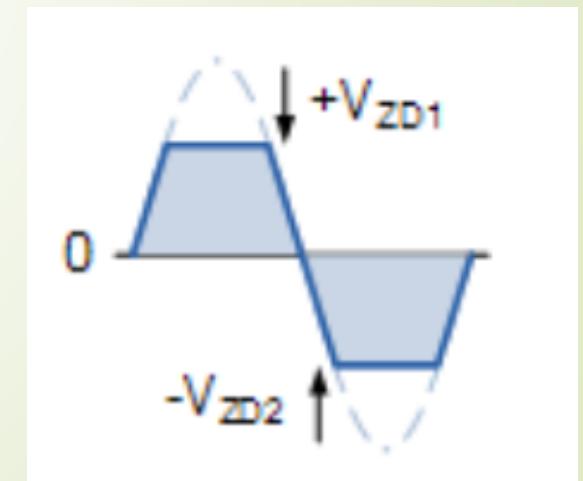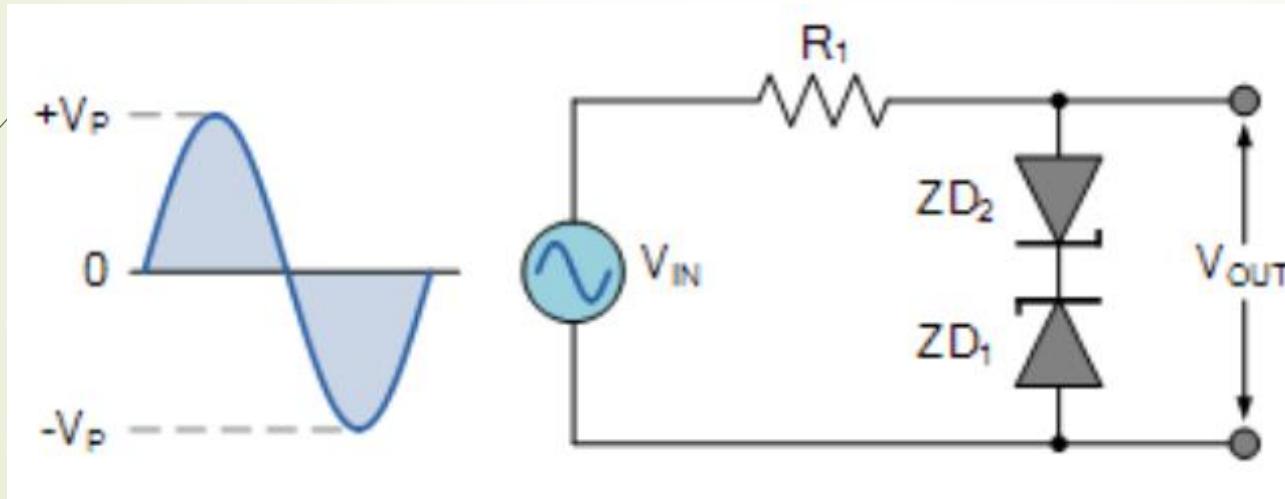
# Full-wave Zener Diode Clipping

The output waveform will be clipped at the Zener voltage plus the 0.7V forward volt drop of the other diode.



# Clamping

4


► Clamping circuits are used to shift an AC waveform up or down by adding a DC level equal to the positive or negative peak value of AC input.

## Types of Clampers


1. Positive Clamper
2. Positive clamper with positive  $V_r$
3. Positive clamper with negative  $V_r$
4. Negative Clamper
5. Negative clamper with positive  $V_r$
6. Negative clamper with negative  $V_r$
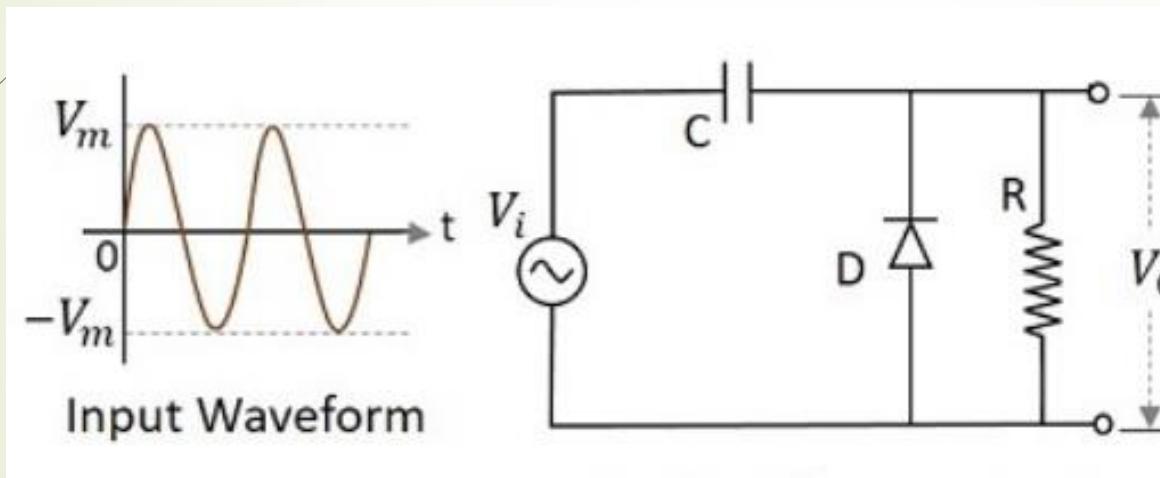
# 1. Positive Clamper Circuit

► A Clamping circuit restores the DC level. When a negative peak of the signal is raised above to the zero level, then the signal is said to be **positively clamped**.





$$V_0 = V_i + V_m$$

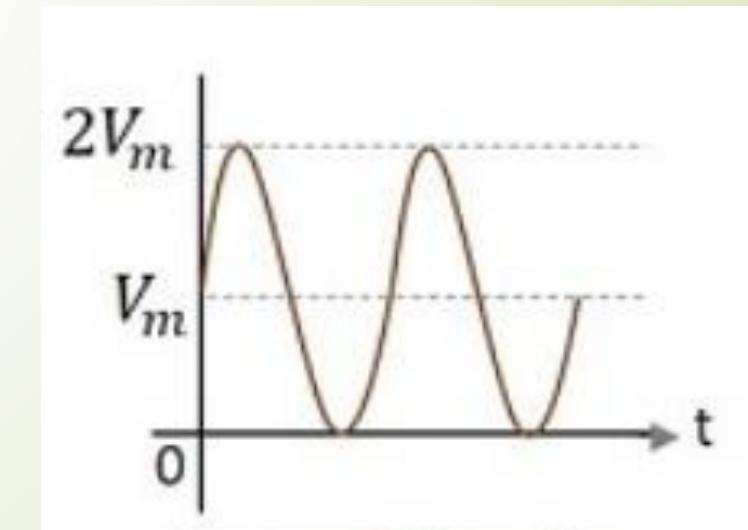

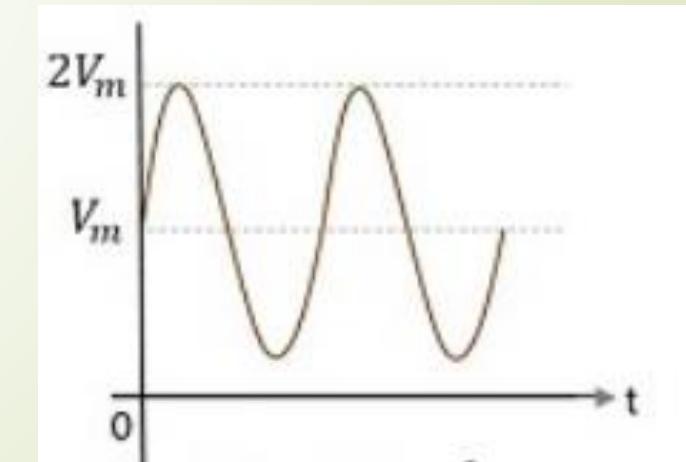
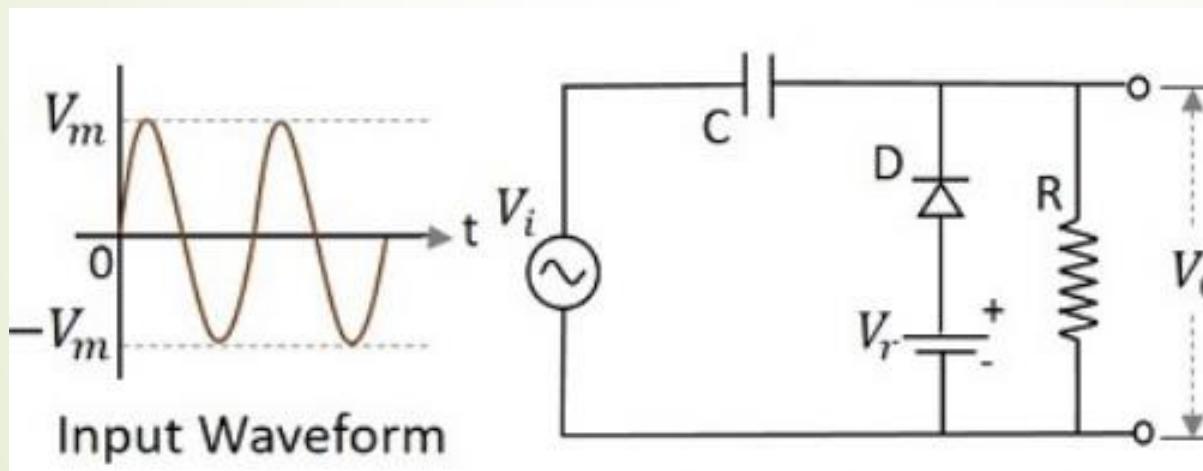
## 2. Positive Clamper with Positive $V_r$

- When a Positive clamper circuit is provided with a positive reference voltage and biased accordingly, the circuit incorporates this voltage into its output, elevating the clamped level in the process.





### 3. Positive Clamper with Negative $V_r$

7

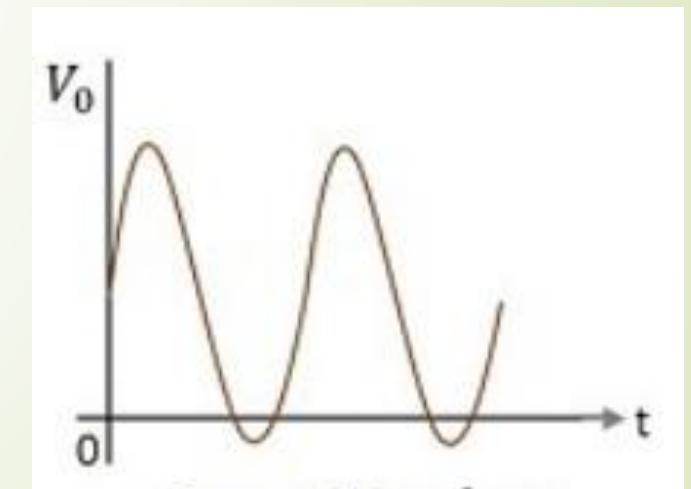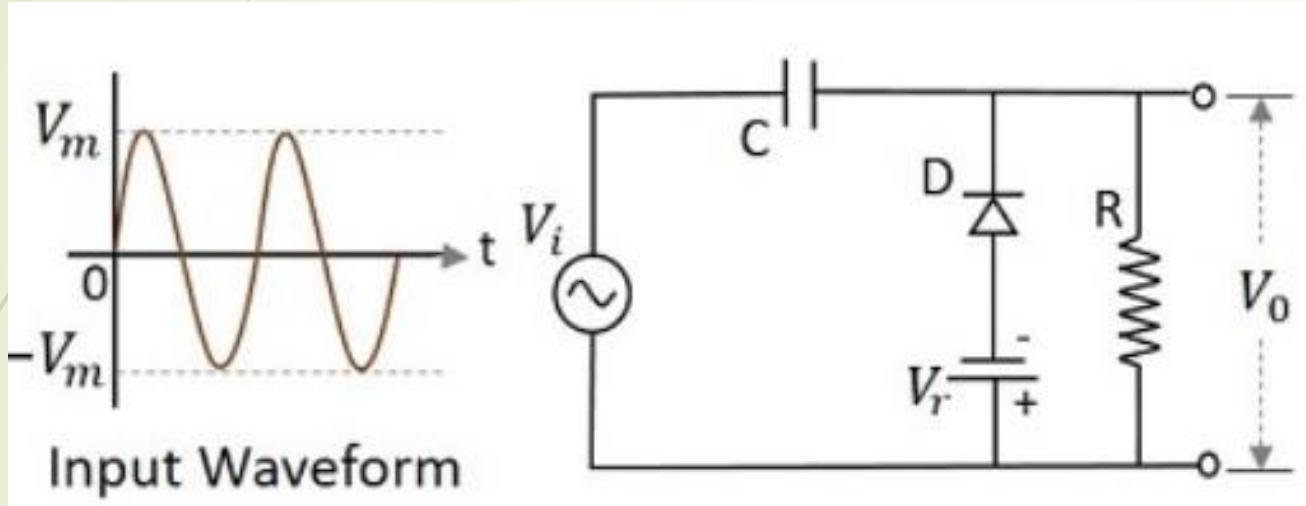

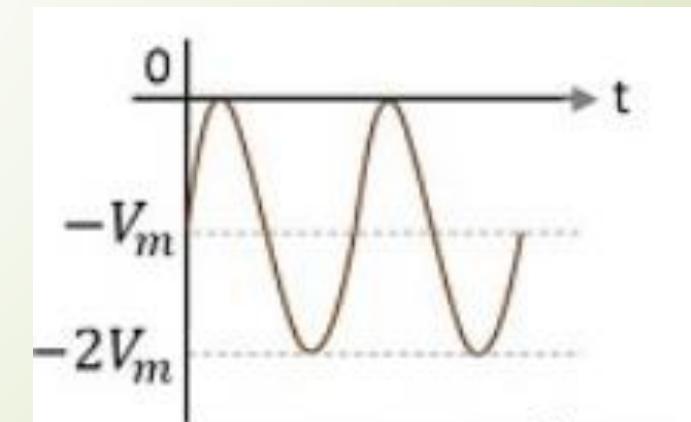
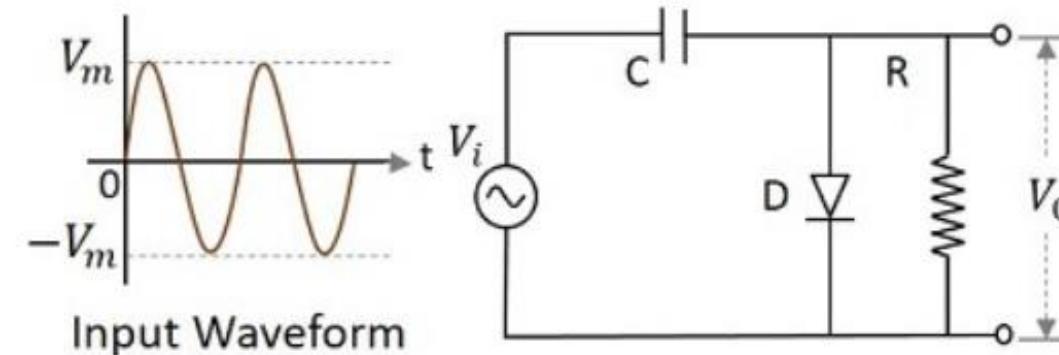
## 4. Negative Clamper

- A Negative Clamper circuit is one that consists of a diode, a resistor, and a capacitor and that shifts the output signal to the negative portion of the input signal.




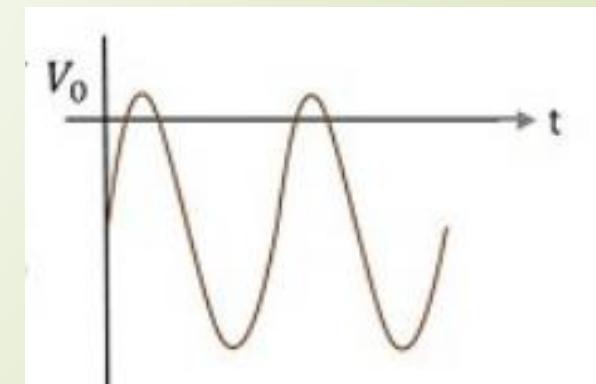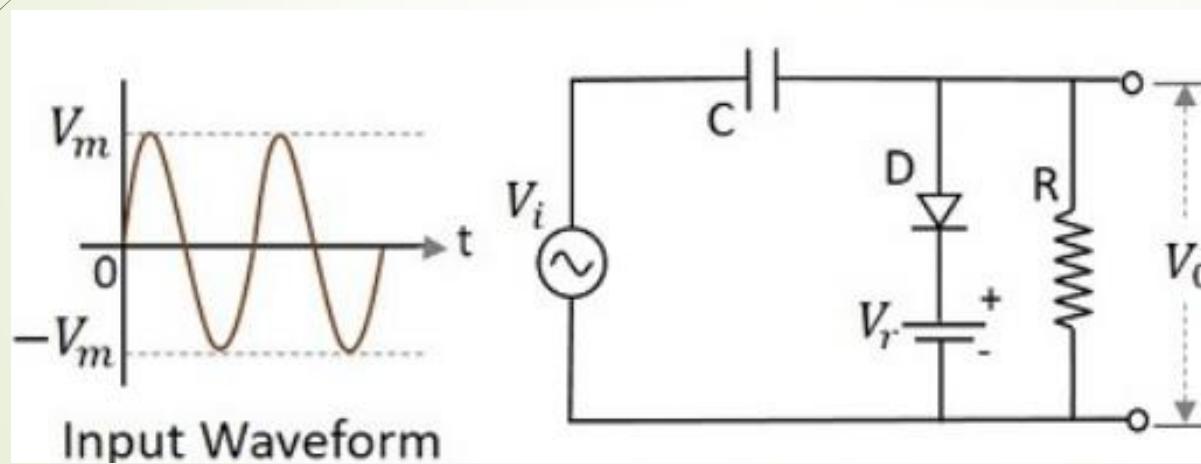
# 5. Negative clamper with positive $V_r$

- A Negative clamper circuit if biased with some positive reference voltage, that voltage will be added to the output to raise the clamped level.


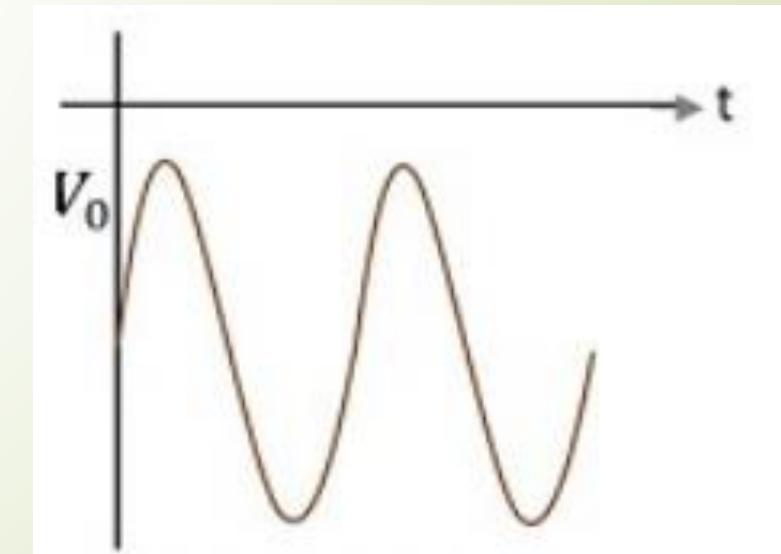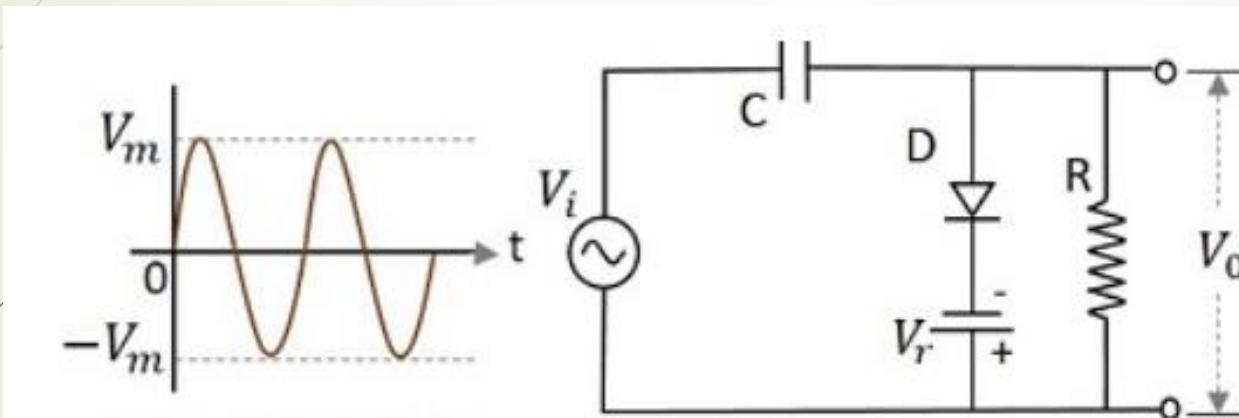
## 6. Negative Clamper with Negative $V_r$



EE/EC 3301

# ANALOG ELECTRONICS

◦ Neel Karunasena


Department of Electrical and Information Engineering.

Email: neelk@eie.ruh.ac.lk
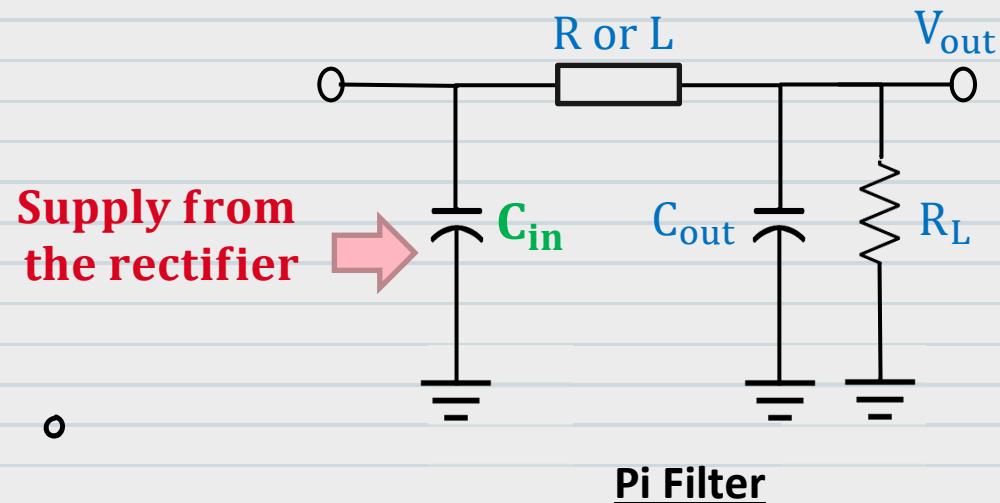
# $\pi$ Filter

Consists of a **shunt capacitor** at the input side, and it is followed by an L-section filter.

The capacitor is present at the input side. Called as *capacitor input filter*.



# $\pi$ Filter

Consists of a **shunt capacitor** at the input side, and it is followed by an L-section filter.


The capacitor is present at the input side. Called as *capacitor input filter*.

The construction arrangement of all the components resembles the shape of Greek letter **Pi ( $\pi$ )**. Called as *Pi filter*.

- o

Supply from  
the rectifier

- o

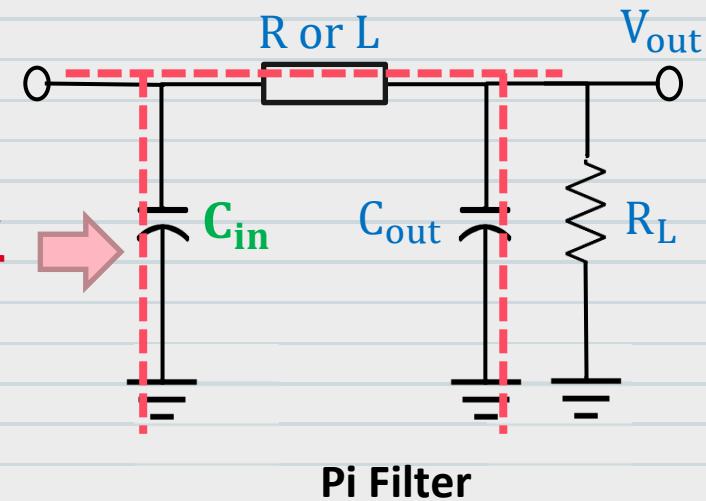


The output from the rectifier is directly given across capacitor.

The pulsating DC output voltage is filtered first by the capacitor connected at the input side and then by resistor or coil and then by another shunt capacitor.

$C_{in}$  – Low reactance to the AC component  
and high (infinite) resistance to the DC component.  
(by passes AC comp to the GND, provides  
DC comp to the R or L.)

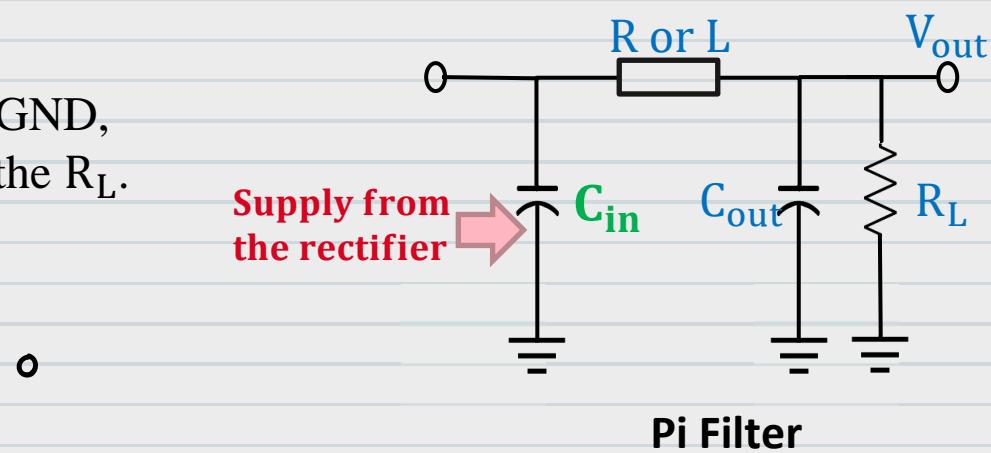
- $C_{out}$  – Bypasses AC comp to the GND,  
provides DC comp across the  $R_L$ .




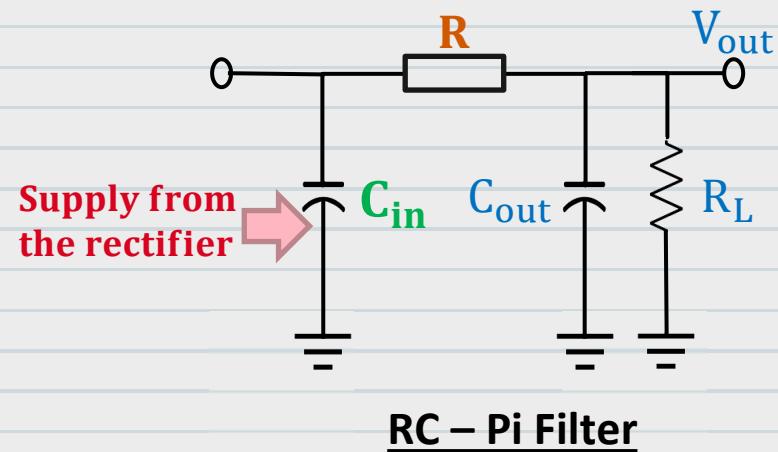
# Rectifier with RC – $\pi$ Filter


Low pass RC filter section added to get greater reduction in ripple.

The capacitor – resistor – capacitor combination is called as ***RC –  $\pi$  filter***.




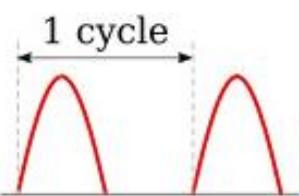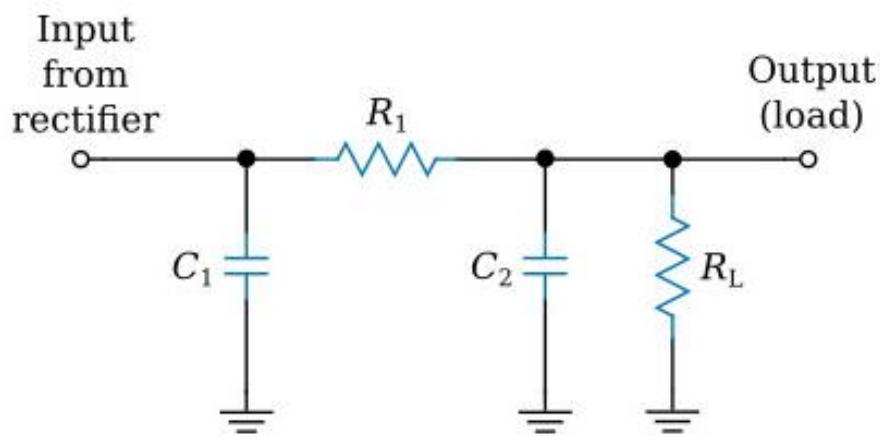

Half-wave rectifier

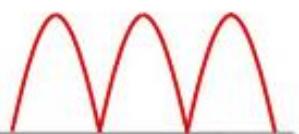

Full-wave rectifier

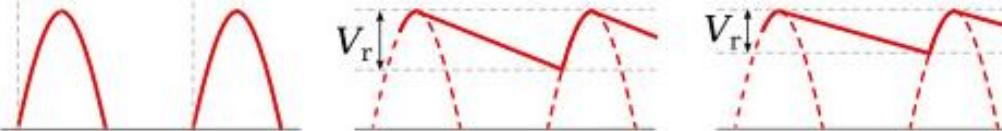


(A) Unfiltered output from rectifier

(B) Voltage across capacitor  $C_1$

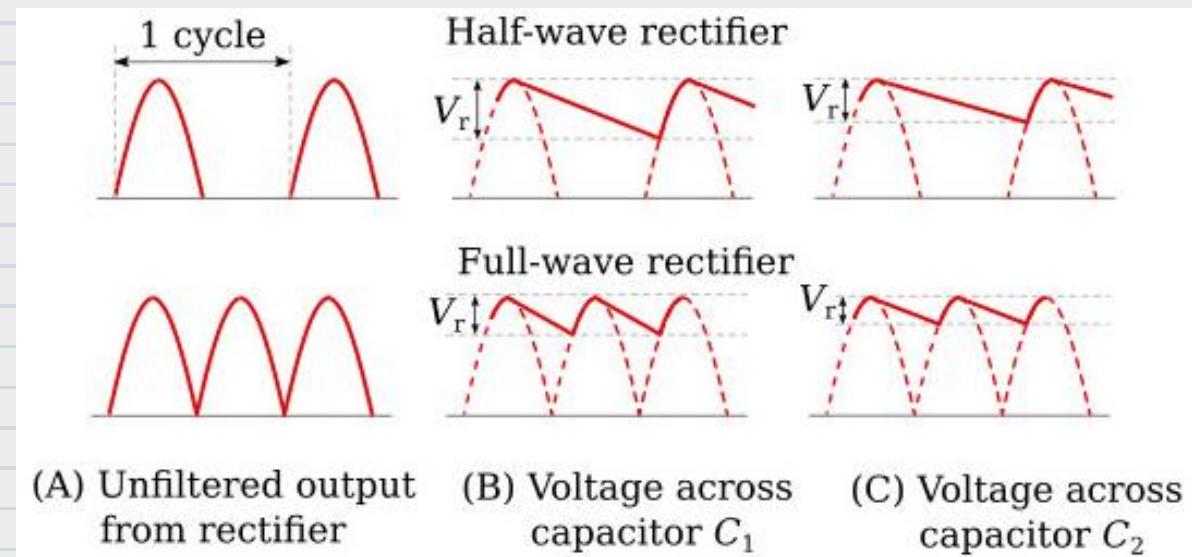(C) Voltage across capacitor  $C_2$

$C_1$  is used to reduce the percentage of ripple to a relatively low value (view B). This voltage is passed on to the  $R_1 - C_2$  network, which reduces the ripple even further.


$C_2$  offers an infinite impedance to the DC component of the output voltage. Thus, the DC voltage is passed to the load.



$\therefore$  Most of the ripple voltage is dropped across  $R_1$ . Only a trace of the ripple voltage can be seen across  $C_2$  and the  $R_L$  (view C).


The RC filter is extremely popular because smaller capacitors can be used with good results.



- 

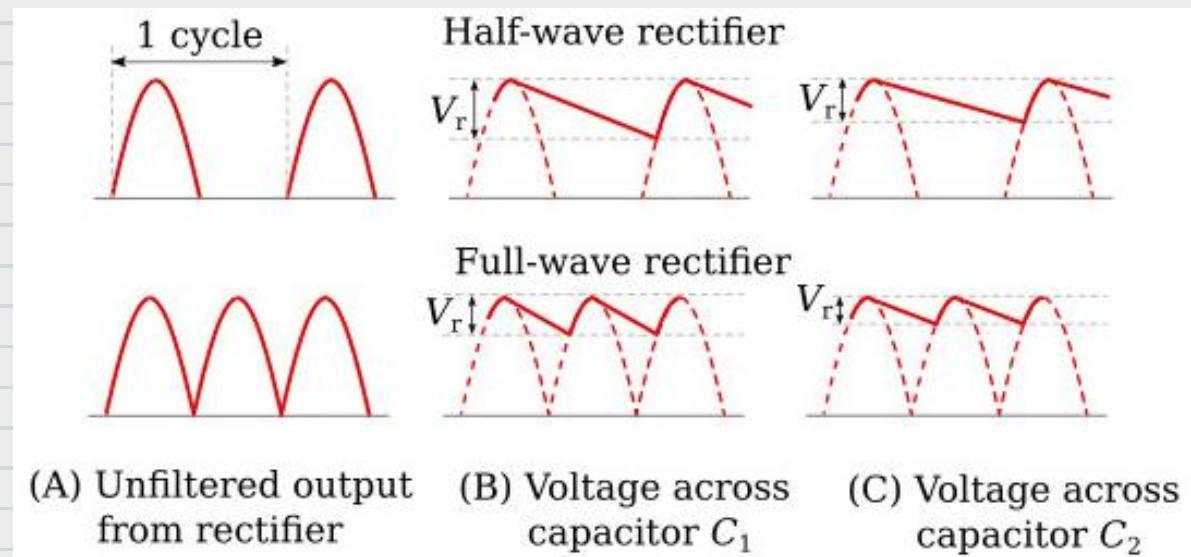


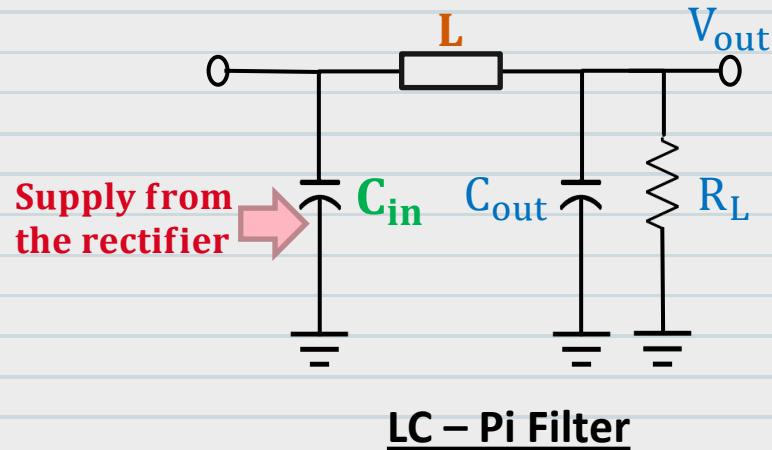
# Rectifier with LC – $\pi$ Filter

R replaced by an **L (Inductor)** and one of the most commonly used filters.



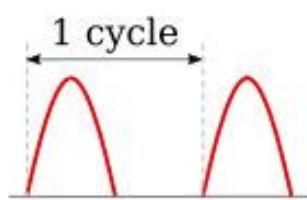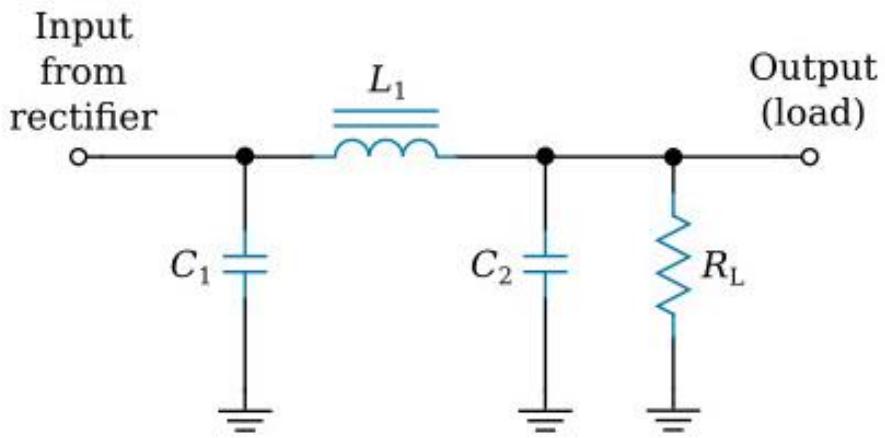

Half-wave rectifier

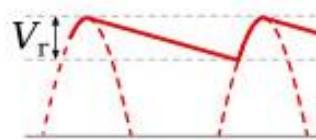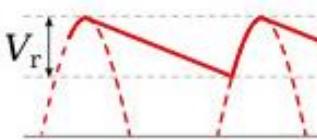


(A) Unfiltered output from rectifier



(B) Voltage across capacitor  $C_1$



(C) Voltage across capacitor  $C_2$

# **DC Power Supplies and Regulation**

# DC Power Supply

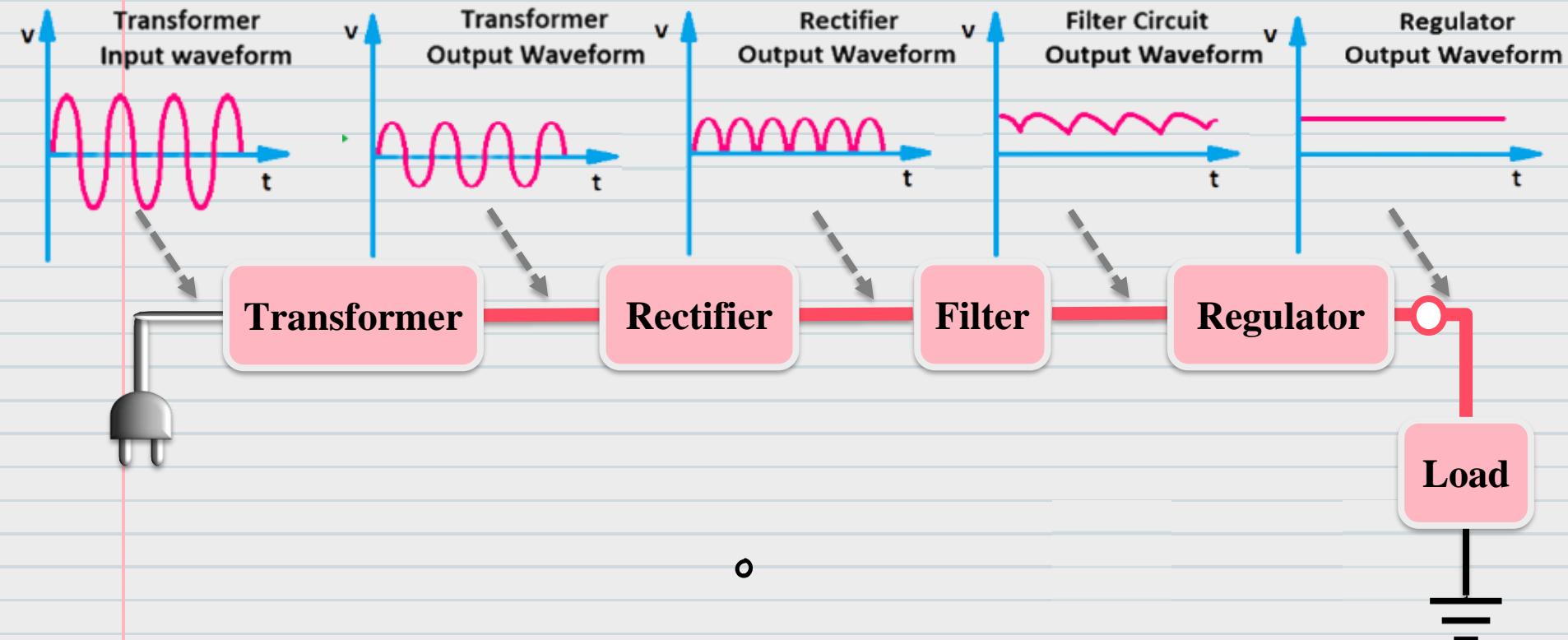

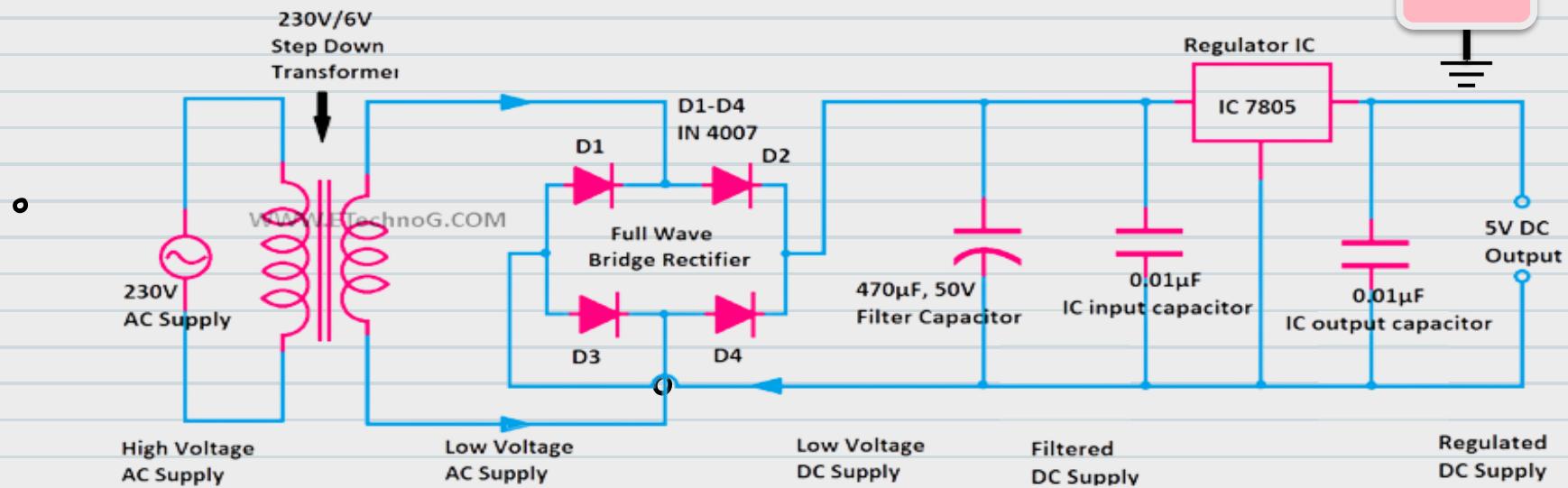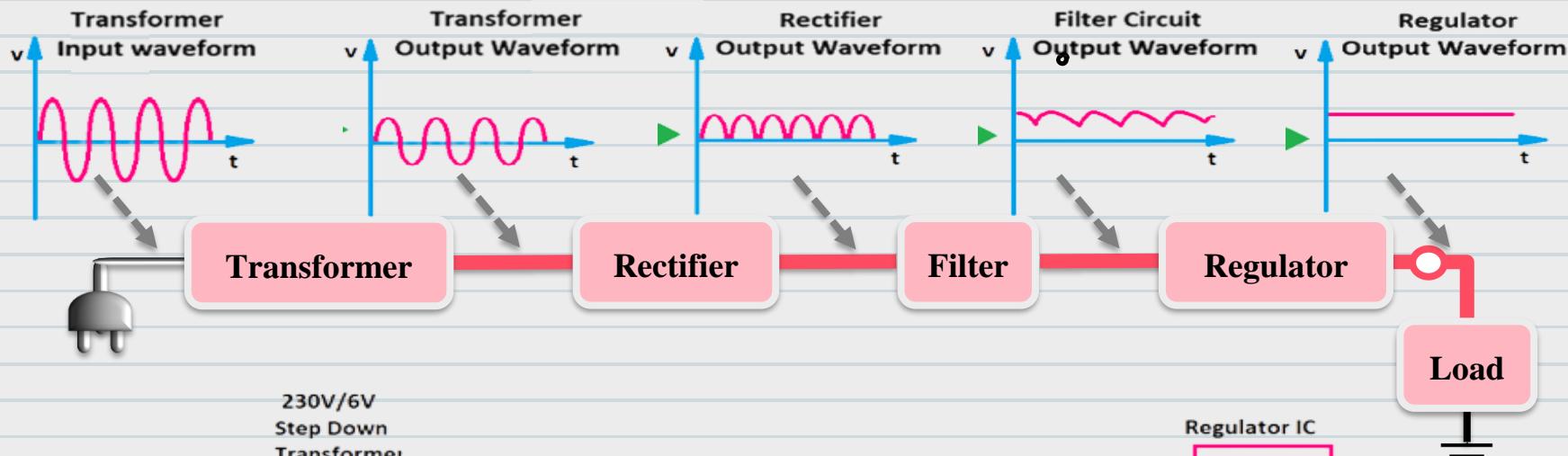

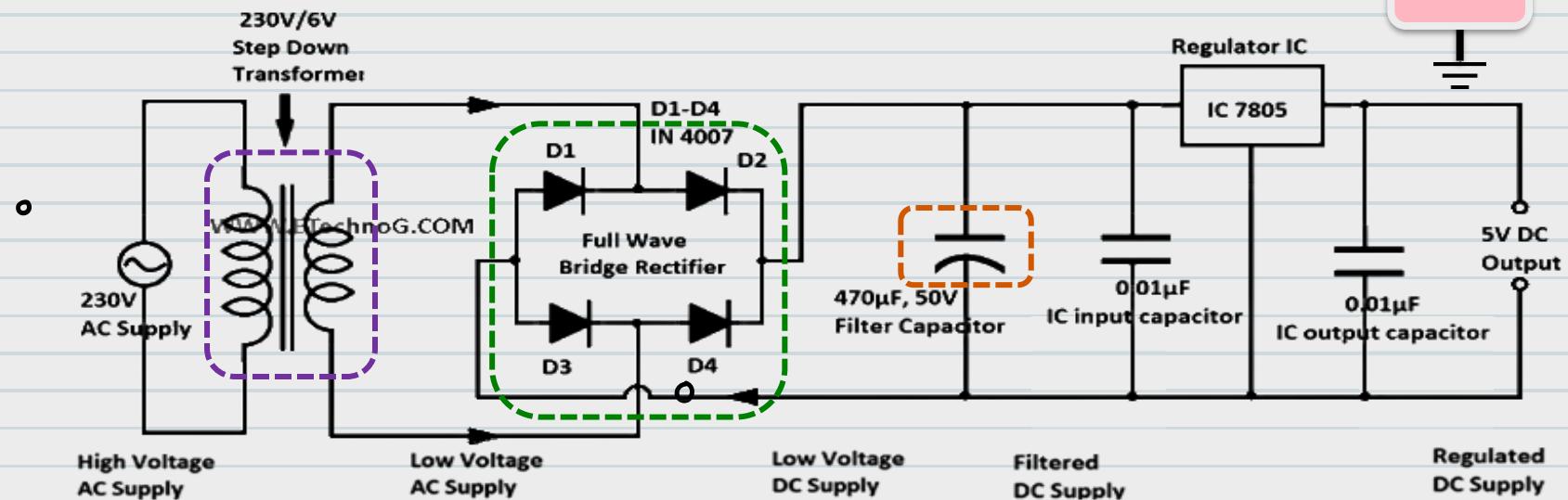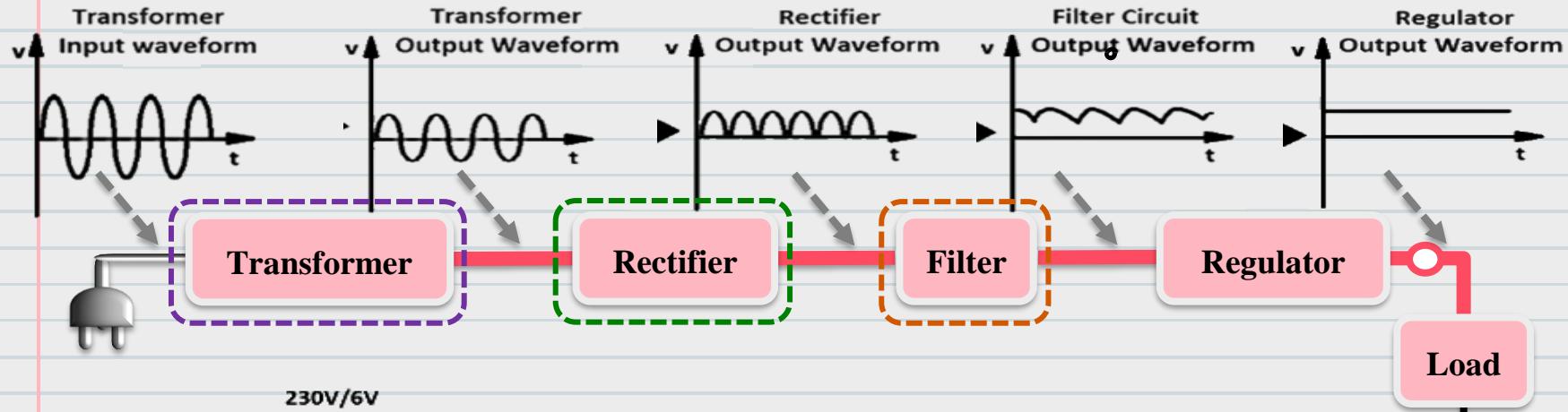

# Regulation

The last and most important block of the regulated power supply.

Ensures a steady constant voltage supply through all operational conditions.


(Maintain/ regulate/ stabilize output voltage during the variations in loads.)

Voltage fluctuations damage to electrical machinery.

Disturbances such as power sags and surges affect sensitive electronics devices.

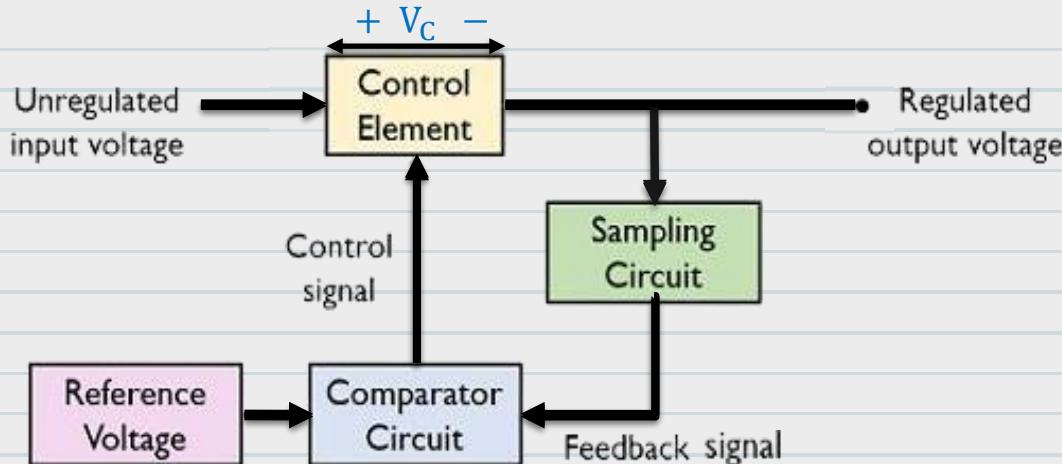The regulator circuit uses different types of regulating components and devices such as a Series inductor, Zener Diode, IC 78XX series, IC 317, etc.





The unregulated dc voltage is the input to the circuit.

**Control element** controls the amount of input voltage that is going to the output side.

**Sampling circuit** provides the necessary feedback signal.

**Comparator circuit** compares the feedback signal with the reference voltage to generate the appropriate control signal.


Thus depending upon the value of control signal, the voltage  $V_c$ , across the control element is adjusted in order to maintain the output voltage constant.

**Used for both fixed as well as variable load conditions.**

Two types of Regulation:


1. Line Regulation
2. Load Regulation

# 1. Line Regulation

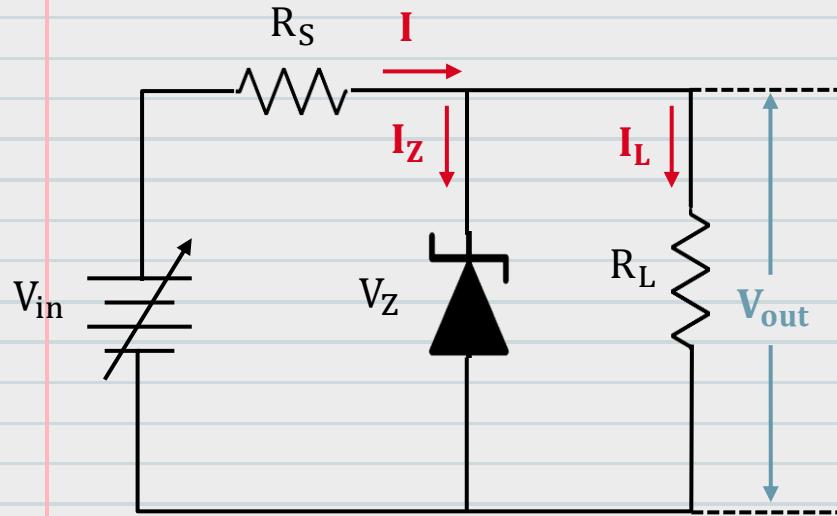

$$V_0 = V_Z = \text{Constant}$$

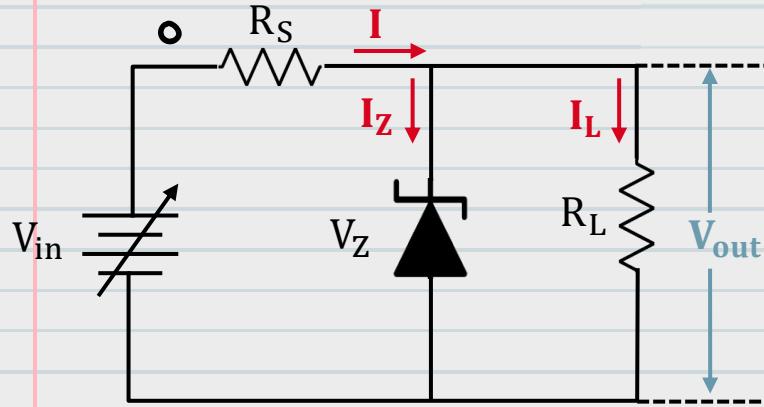- Series resistance,  $R_S$  and load resistance,  $R_L$  are fixed.  
Input voltage,  $\underline{V_{in}}$  is changing.  
Output voltage,  $V_{out}$  remains the same as long as the input voltage is maintained above a ***minimum value***.



Considering the voltage across the  $R_S$ ,


$$V_{RS} = I R_S \quad \textcircled{1}$$

- $V_{RS} = [V_{in}] - [V_{out}] \rightarrow [V_{in}] \propto \{V_{RS}\}$

$$\textcircled{1} \rightarrow \{V_{RS}\} = I [R_S] \rightarrow \{V_{RS}\} \propto \{I\}$$

$$\{V_{in}\} \propto \{V_{RS}\} \propto \{I\} \rightarrow \boxed{\{V_{in}\} \propto \{I\}}$$

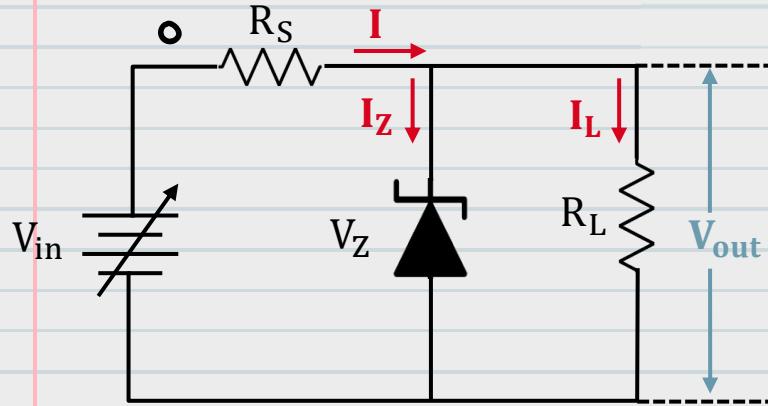**$V_{in}$ : Varying  $\rightarrow I$  : Varying**




Considering the output voltage  $V_{out}$ ,

$$V_{out} = I_L R_L \quad \textcircled{2}$$

- $[V_{out}] = I_L [R_L] \rightarrow [V_{out}] = [I_L][R_L]$

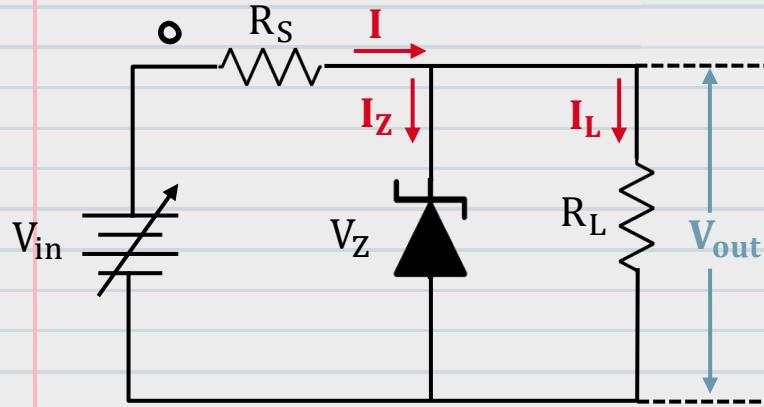**$R_L$ : Fixed  $\rightarrow I_L$ : Constant**



Considering the current  $I$ ,

$$I = I_Z + I_L \quad \text{--- (3)}$$

- $I = I_Z + [ I_L ] \rightarrow I \propto I_Z$


According to (1),

$V_{in}$ : Varying  $\rightarrow I$  : Varying;  $\{V_{in}\} \propto \{I\}$

According to (3),

when,  $I$ : Varying  $\rightarrow I_Z$ : Varying;  $\{I\} \propto \{I_Z\}$

## Limitation of the $I_Z$ :

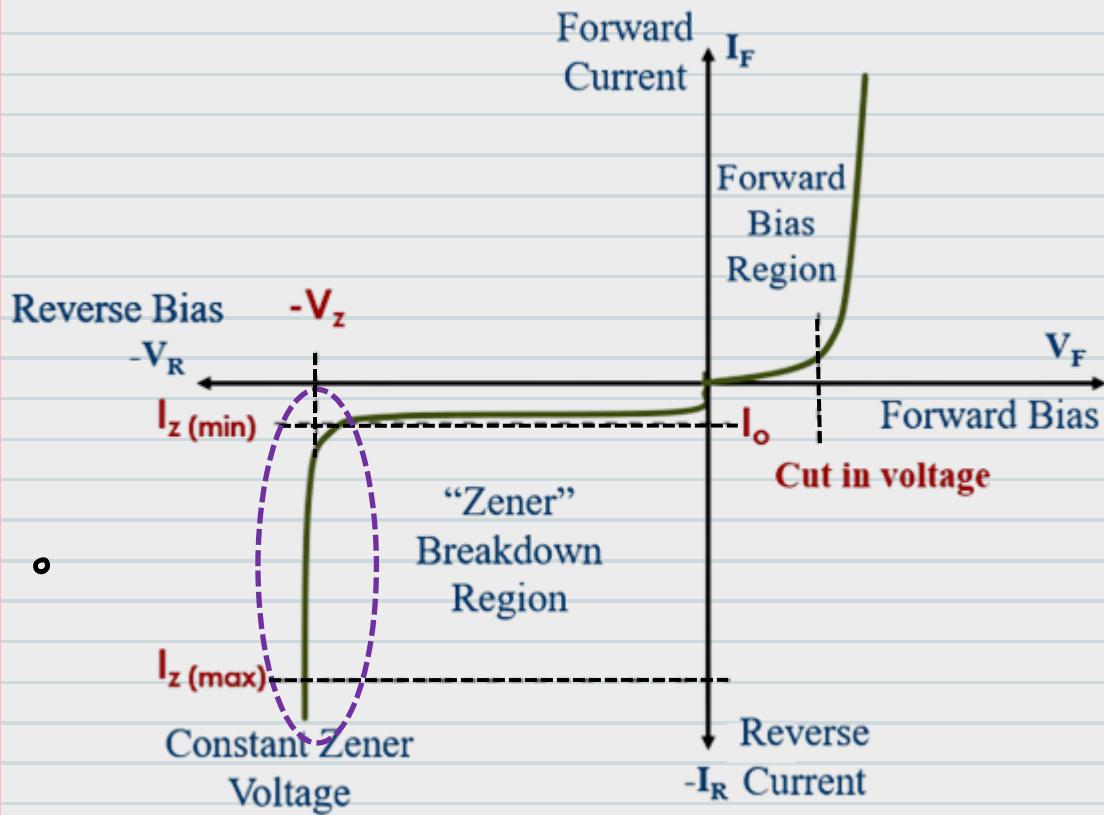


∴ If  $I_Z$  vary within the minimum and maximum current for the Zener diode; then  $V_Z$  can be kept constant.

$$I_{Z\min} < I_Z < I_{Z\max}$$




$$[ V_Z ]$$

## 2. Load Regulation

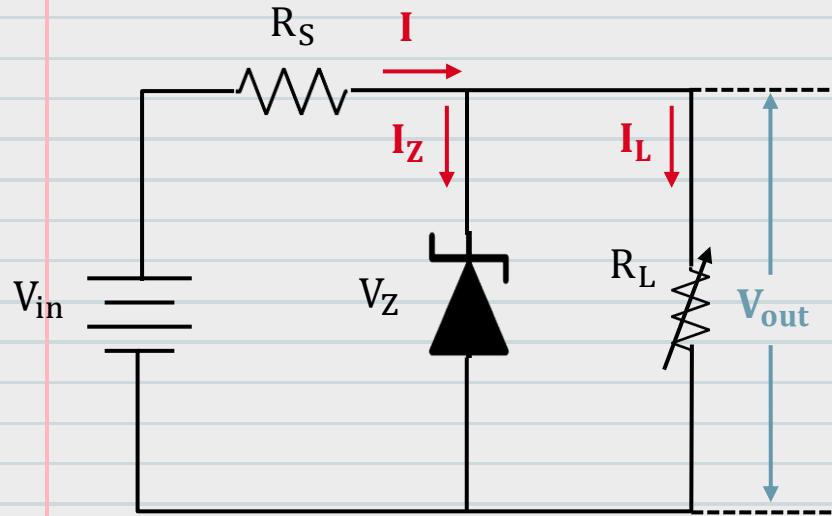


$$V_0 = V_Z = \text{Constant}$$

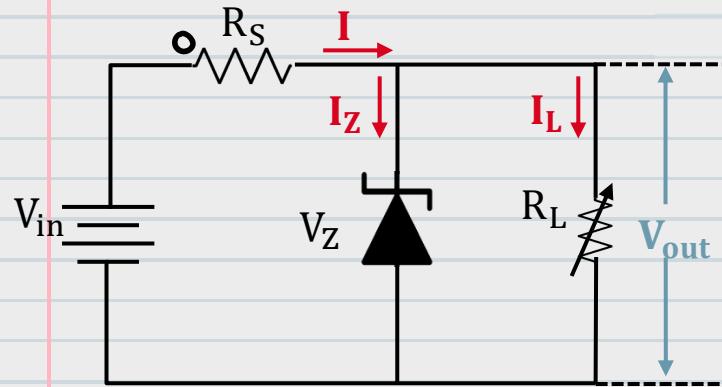- Series resistance,  $R_S$  and Input voltage,  $V_{in}$  are fixed.  
Load resistance,  $R_L$  is changing.  
Output voltage,  $V_{out}$  remains the same as long as the input voltage is maintained above a **minimum value**.



$V_0 = V_Z = \text{Constant}$

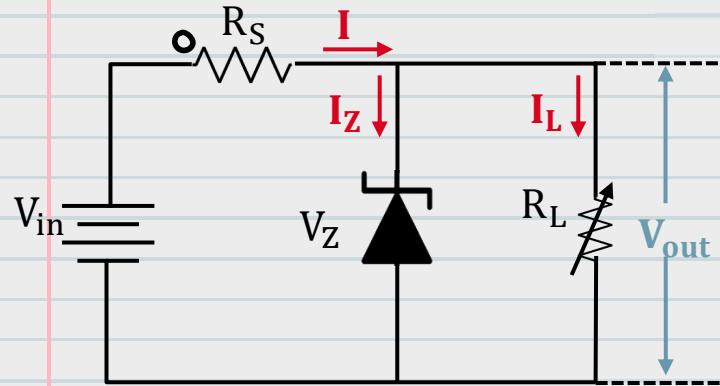$V_{in}$ : Fixed  $\rightarrow I$  : Fixed



$V_0 = V_Z = \text{Constant}$


$V_{\text{in}}: \text{Fixed} \rightarrow I: \text{Fixed}$

Considering the output voltage  $V_{\text{out}}$ ,

$$V_{\text{out}} = I_L R_L \quad \textcircled{2}$$

- $[V_{\text{out}}] = I_L \{R_L\} \rightarrow \{R_L\} \alpha \{I_L\}$

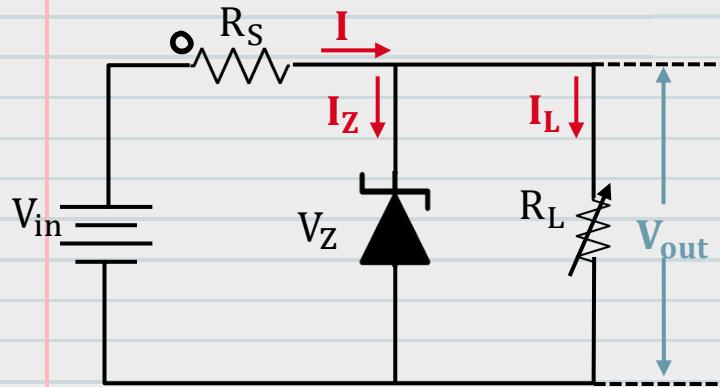$R_L: \text{Varying} \rightarrow I_L: \text{Varying}$



- $V_0 = V_Z = \text{Constant}$

$V_{in}$ : Fixed  $\rightarrow I$ : Fixed

$R_L$ : Varying  $\rightarrow I_L$ : Varying

$I_L$ : Varying  $\rightarrow I_Z$ : Varying


Considering the current  $I$ ,

$$I = I_Z + I_L \quad \text{--- (3)}$$

- $[I] = I_Z + \{I_L\} \rightarrow \{I_L\} \propto \{I_Z\}$

when,

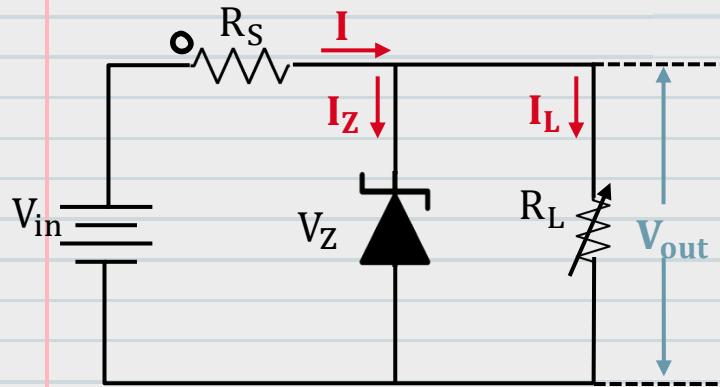$I_L$ : Varying  $\rightarrow I_Z$ : Varying



- $V_0 = V_Z = \text{Constant}$
- $V_{in}: \text{Fixed} \rightarrow I : \text{Fixed}$
- $R_L: \text{Varying} \rightarrow I_L: \text{Varying}$
- $I_L: \text{Varying} \rightarrow I_Z: \text{Varying}$

Same as before, to keep  $V_Z$  constant;

- $I_{Zmin} < I_Z < I_{Zmax}$

↓

$[ V_Z ]$

# Line Regulation vs Load Regulation.

## Line regulation

The ability of the power supply to maintain its specified output voltage over **changes in the input line voltage**.

Expressed as percent of change in the output voltage relative to the change in the input line voltage.

## Load regulation

The ability of the power supply to maintain its specified output voltage given **changes in the load**. (Power is regulated)

- This does not mean the **tolerance** applies when there are sudden changes in load, it means over the permissible load range the regulation can change by this amount.

*Both values apply to the output. This means the worst case value you need to use is both of the line and load tolerance percentages added together.*

# Line Regulation

Can express as;

$$\text{Line Regulation (in %)} = \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} \times 100\%$$

$$\text{Line Regulation (in \% / V)} = \frac{\Delta V_{\text{out}}/V_{\text{out}}}{\Delta V_{\text{in}}} \times 100\%$$

- 

For ideal power supply,

**Line Regulation = 0 %**

### **Example 01:**

**The input of a certain regulator increases by 3.5 V. As a result, the output voltage increases by 0.042 V. The nominal output is 20 V. Determine the line regulation.**

o

## Example 01:

The input of a certain regulator increases by 3.5 V. As a result, the output voltage increases by 0.042 V. The nominal output is 20 V. Determine the line regulation.


$$\begin{aligned} \text{Line Regulation (in \%)} &= \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} \times 100\% = \frac{0.042 \text{ V}}{3.5 \text{ V}} \times 100\% \\ &= \underline{\underline{1.2 \%}} \end{aligned}$$

$$\begin{aligned} \bullet \text{Line Regulation (in \% / V)} &= \frac{\Delta V_{\text{out}}/V_{\text{out}}}{\Delta V_{\text{in}}} \times 100\% = \frac{0.042 \text{ V}/20 \text{ V}}{3.5 \text{ V}} \times 100\% \\ &= \underline{\underline{0.06 \% / \text{V}}} \end{aligned}$$

# Load Regulation

For ideal power supply,


**Line Regulation = 0 %**

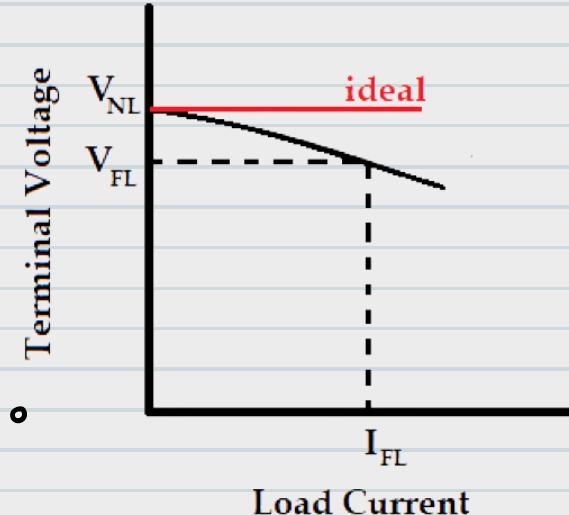

$$\text{Load Regulation (in \%)} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

$V_{NL}$  – No-load output voltage (open circuit)

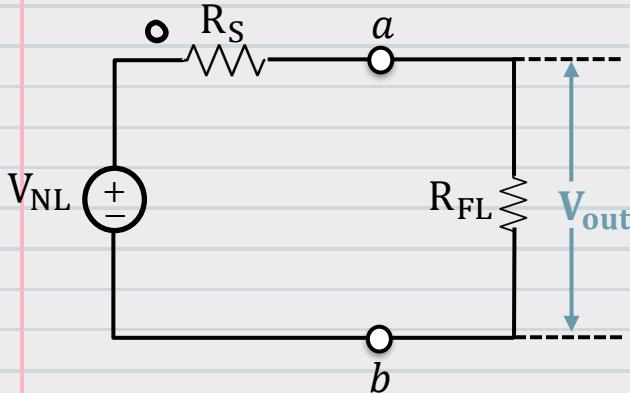$V_{FL}$  – Full-load output voltage (maximum current)



$$V_O = V_{FL} = \frac{R_{FL}}{(R_{FL} + R_S)} V_{NL} \quad \textcircled{1}$$

Load Regulation,

$$\text{Load Regulation (in \%)} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

From, **1**

$$= \frac{V_{NL} - \left[ \frac{R_{FL}}{(R_{FL} + R_S)} V_{NL} \right]}{\left[ \frac{R_{FL}}{(R_{FL} + R_S)} V_{NL} \right]} \times 100\%$$

$$= \frac{R_S}{R_{FL}} \times 100\%$$

***Load Regulation (in %) =  $\frac{R_S}{R_{FL}} \times 100\%$***

# Voltage Regulators

•

Two types of Voltage Regulators:

1. Linear Voltage Regulators
2. Switching Voltage Regulators

•

# 1. Linear Voltage Regulators


•

Similar to Voltage Divider.

The resistance of the linear voltage regulator changes with the load and gives a constant voltage output.

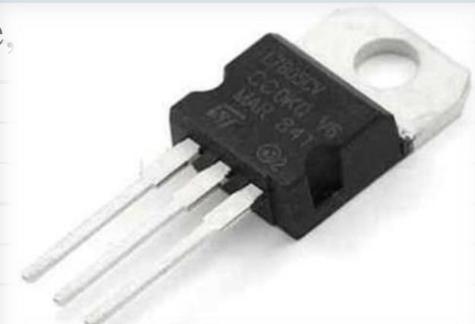Example: LM7805



- **LM78XX:** Voltage regulators that output positive voltage,  
“XX” = voltage output.
- **LM79XX:** Voltage regulators that output negative voltage,  
“XX” = voltage output.




# $\mu$ A7800 SERIES POSITIVE-VOLTAGE REGULATORS

SLVS056J – MAY 1976 – REVISED MAY 2003


## schematic

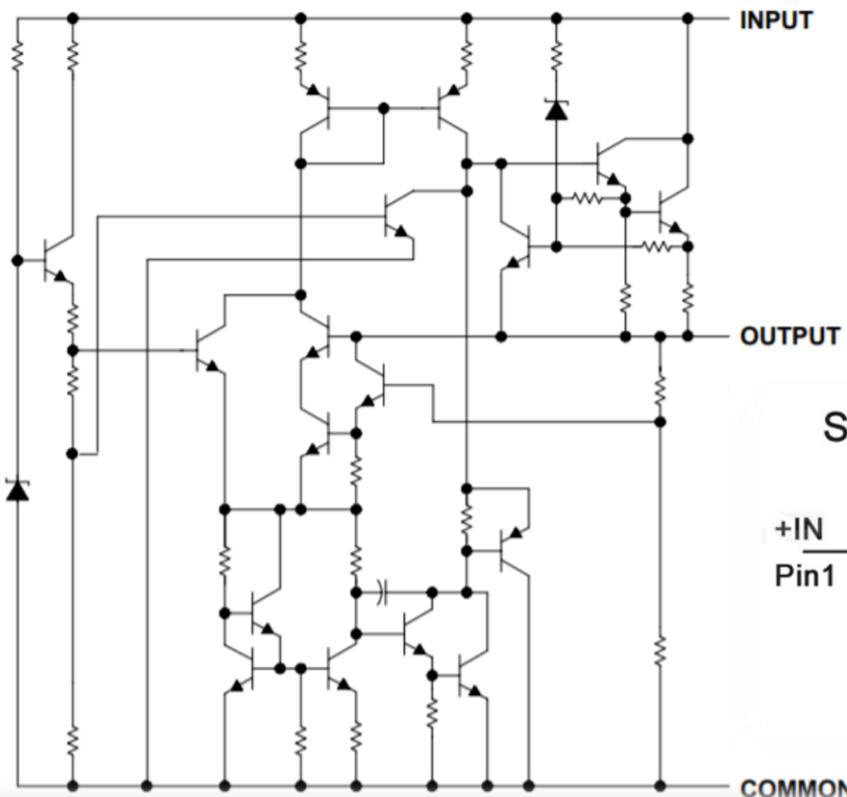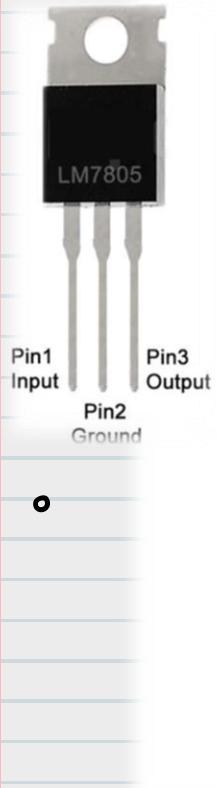

## Symbol In Diagram

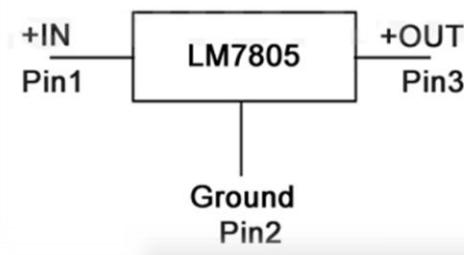

# 1. Linear Voltage Regulators

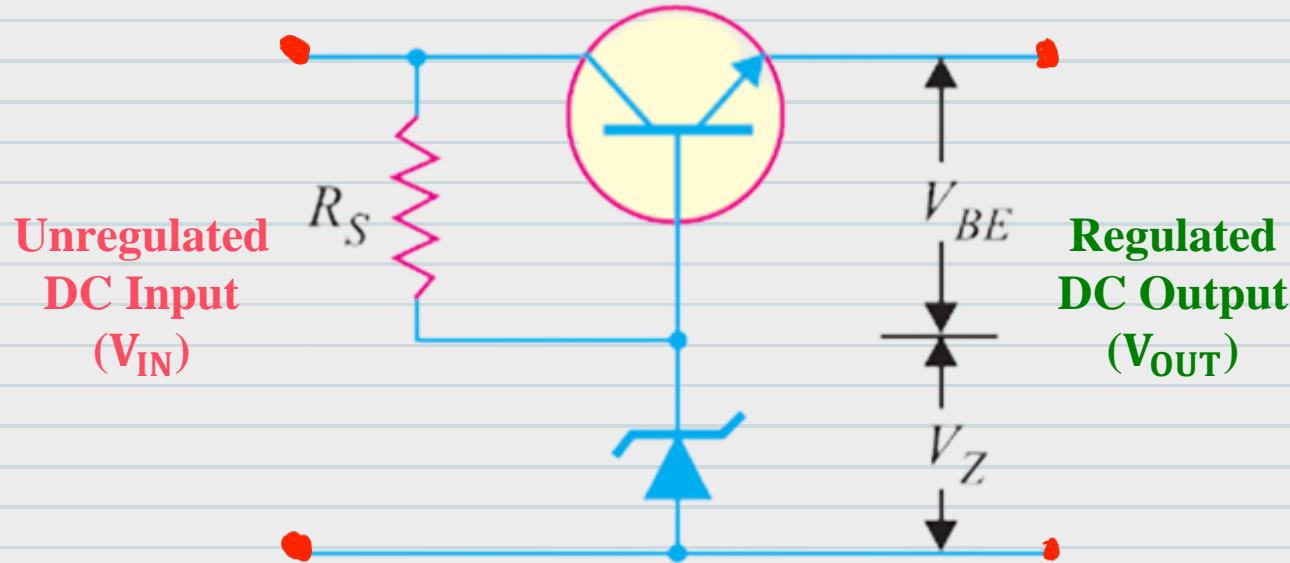


# 1. Linear Voltage Regulators

Two types of Linear Voltage Regulators:

- a. Series Voltage Regulator
- b. Shunt Voltage Regulator (i. e. Parallel by pass)



## a. Series Voltage Regulators

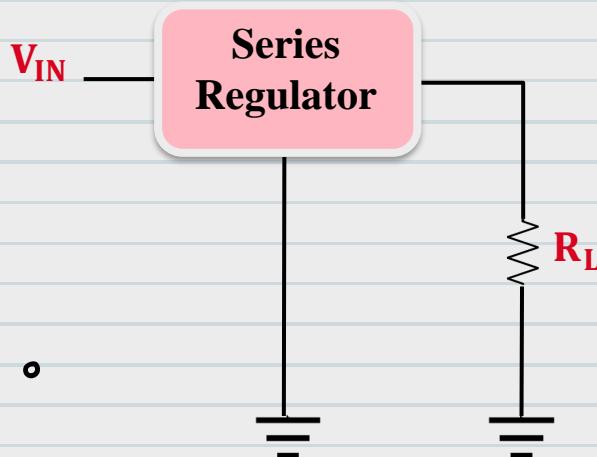

Connected in series with the load.

Does not have an effective voltage regulation at high load currents.

Suitable for heavy loads.


In the series voltage regulator,

Therefore, it is ***high current, low voltage*** device.

Has good efficiency for higher load currents.

## b. Shunt Voltage Regulators

•

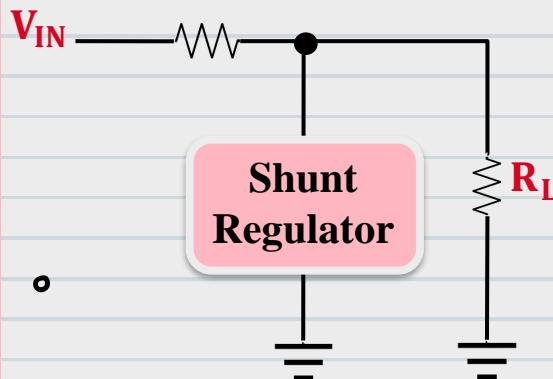

Connected in parallel/shunt with the load.

Has good voltage regulation even at high load currents.

Suitable for light loads.

In the shunt voltage regulator,

Therefore, it is a ***high voltage, low current*** device.

Has good efficiency for low load current.

<b>BASIS OF COMPARISON</b>	<b>SERIES VOLTAGE REGULATOR</b>	<b>SHUNT VOLTAGE REGULATOR</b>
Connection	Series voltage regulator is connected in series with the load.	Shunt voltage regulator is connected in parallel/shunt with the load.
High Load Currents	Series voltage regulator does not have an effective voltage regulation at high load currents.	Shunt voltage regulator has good voltage regulation even at high load currents.
Suitability	The regulator is suitable for heavy loads.	The regulator is suitable for light loads.
Output DC	In the series voltage regulator, the output DC voltage is not constant.	In the shunt voltage regulator, the output DC voltage is constant.
Control Element	In the series voltage, the control element has to carry the load current. Therefore, it is high current low voltage device.	In the shunt voltage, the control element has to bear the load voltage across it. Therefore, it is a high voltage low current device.
Efficiency	Series voltage regulator has good efficiency for higher load currents.	Shunt voltage regulator has good efficiency for low load current.

## Linear Voltage Regulators:

- **Advantages:**

- Cheap

- Fast response time

- Lower electromagnetic Interference and noise

- Good for constant output voltage for low power applications

- **Disadvantages:**

- Low efficiency

- High heat → need heat sink and space

- Output < input

# Switching Regulator Circuit

•

*Rapidly switches a series device on/off.*

Switch's duty cycle sets the amount of charge transferred to the load.

*Controlled by a feedback mechanism similar to that of a linear regulator.*


Series element is either fully conducting or fully switched off → efficient.

Efficient transfer of power to the load (transistor is not always conducting).


*Voltage is passed in pulses, then smoothed and filtered.*

•

# Switching Regulator Circuit

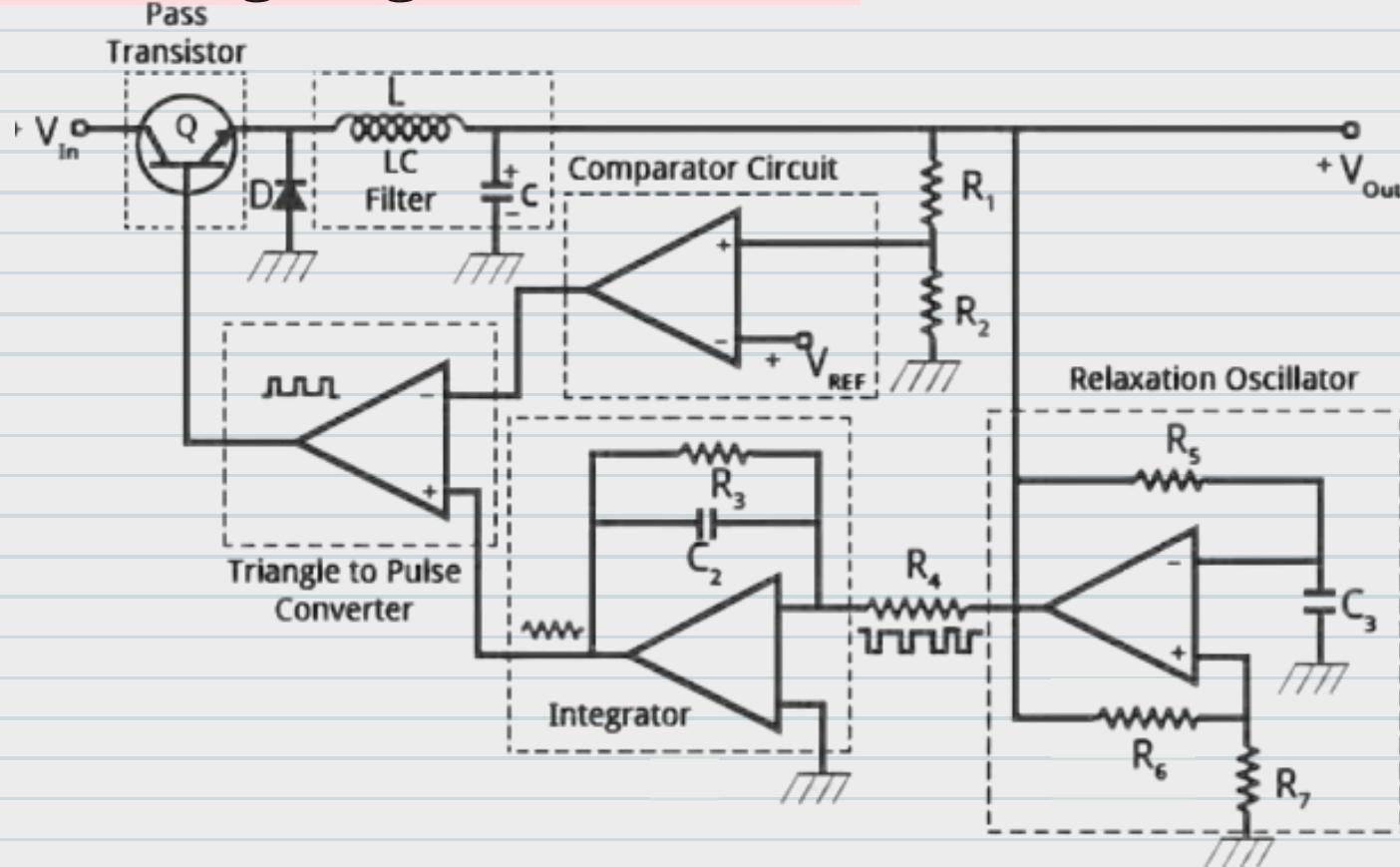

# Switching Regulator Configurations.

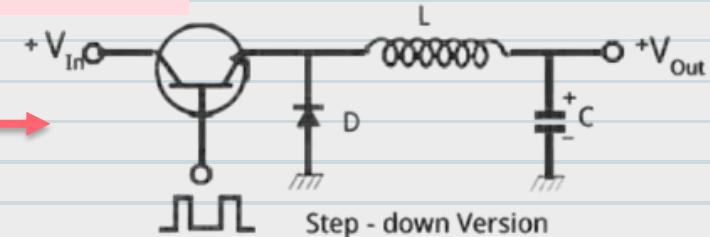


Step - down Version


1. Step Down

2. Step Up

3. Inverter

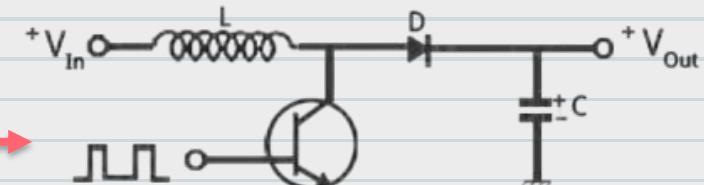

Step - up Version

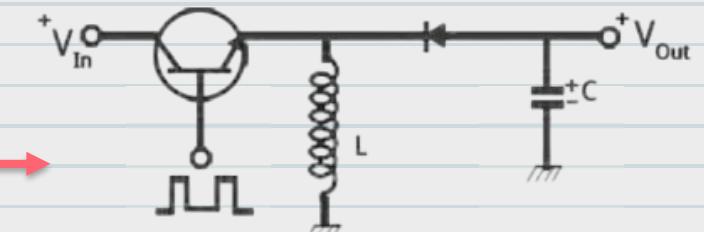

Polarity Inverting Configuration

# Switching Regulators

◦

**Good for high current applications (since less power is dissipated).**

**Voltage regulation is achieved by the on and off action, limiting the amount of current flow based on the varying line and load conditions.**

◦

# Switching Regulator Circuit

•

## Advantages:

Power conversion efficiency is high (even 90% possible).

Heat sinks not needed.

Useful when input/output voltages are very different.


## Disadvantages:

- Expensive.
- High electromagnetic interference and noise.
- Complex circuits.




**THANK YOU!**
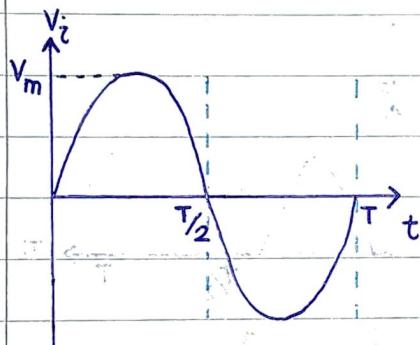
## Half - wave Rectification



The process of removing one - half the input signal to establish a dc level is called half wave rectification




$$V_i = V_m \sin \omega t$$

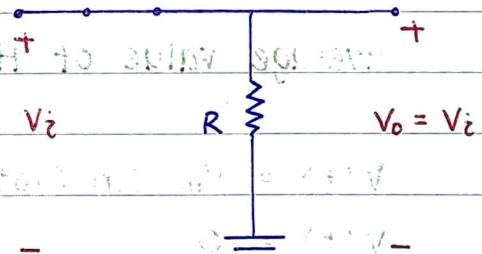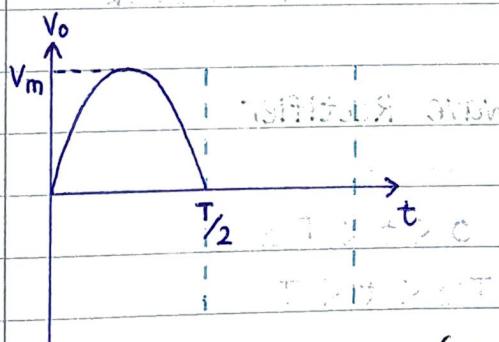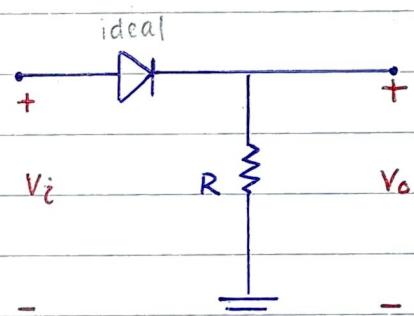

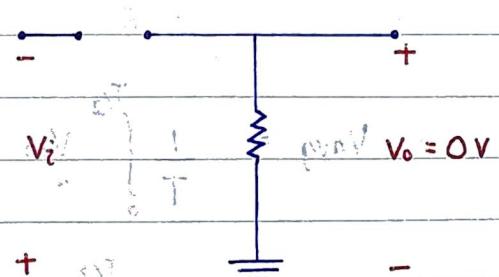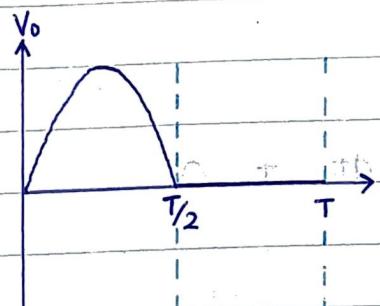Conduction Region ( $0 \rightarrow T/2$ )



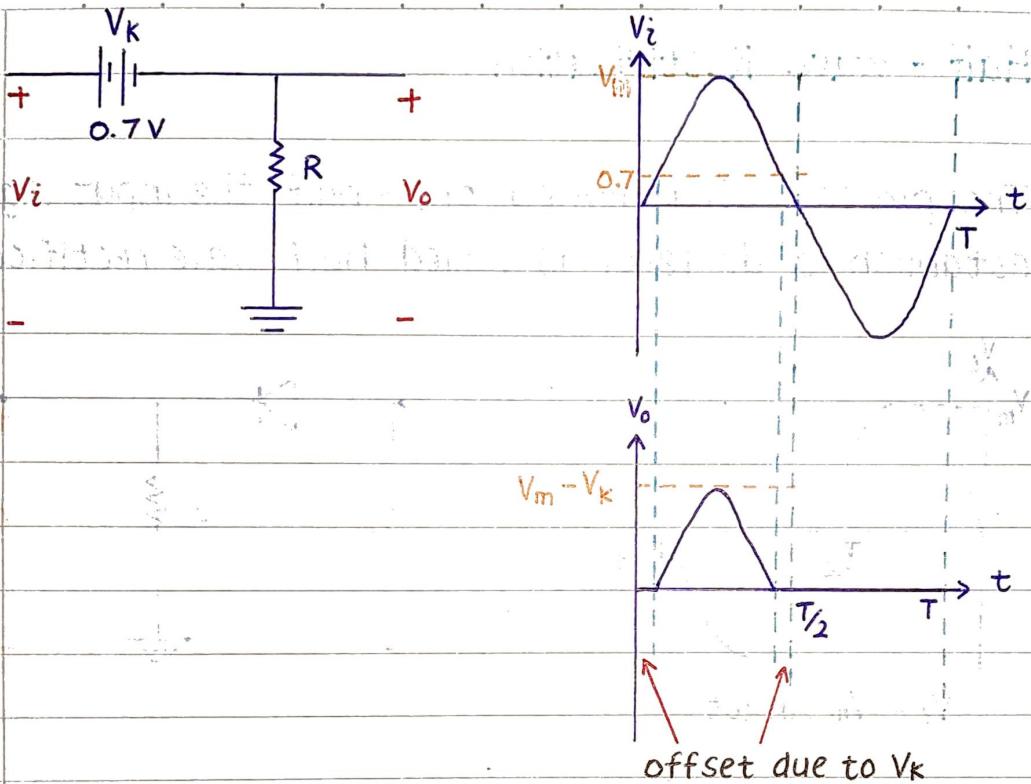Non - conduction Region ( $T/2 \rightarrow T$ )



### Average value of Half-wave Rectifier

$$V(t) = V_m \sin(\omega t) ; 0 < t < T/2$$

$$V(t) = 0 ; T/2 < t < T$$

$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

$$V_{avg} = \frac{1}{T} \int_0^{T/2} V_m \sin(\omega t) dt + 0$$

$$V_{avg} = \frac{V_m}{T} \int_0^{T/2} \sin(\omega t) dt$$

$$V_{avg} = \frac{V_m}{T} \left[ -\cos \omega t \right]_0^{T/2}$$

$\omega = \frac{2\pi}{T}$

$$= \frac{V_m}{T \times \frac{2\pi}{T}} \left[ -\cos \left( \frac{2\pi}{T} \times t \right) \right]_0^{T/2}$$

$$= \frac{V_m}{2\pi} \left[ -\cos \pi - (-\cos 0) \right]$$

$$= \frac{V_m}{2\pi} [-(-1) - (-1)]$$

$$V_{avg} = \frac{V_m}{\pi}$$

Bridging Application

### RMS value of Half-wave Rectifier

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$V_{rms}^2 = \frac{1}{T} \int_0^{T/2} V_m^2 \sin^2(\omega t) dt$$

$$\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$


$$= \frac{V_m^2}{T} \int_0^{T/2} \frac{1 - \cos(2\omega t)}{2} dt$$


$$\begin{aligned}
 V_{rms}^2 &= \frac{V_m^2}{2T} \left[ t - \frac{\sin(2\omega t)}{2\omega} \right]_0^{T/2} \\
 &= \frac{V_m^2}{2T} \left[ \frac{T}{2} - \frac{\sin(4\pi/T \times T/2)}{2\omega} - 0 + \frac{\sin(0)}{2\omega} \right] \\
 &= \frac{V_m^2}{4}
 \end{aligned}$$

$V_{rms} = \frac{V_m}{2}$


## Full-wave Rectification

### Bridge Network

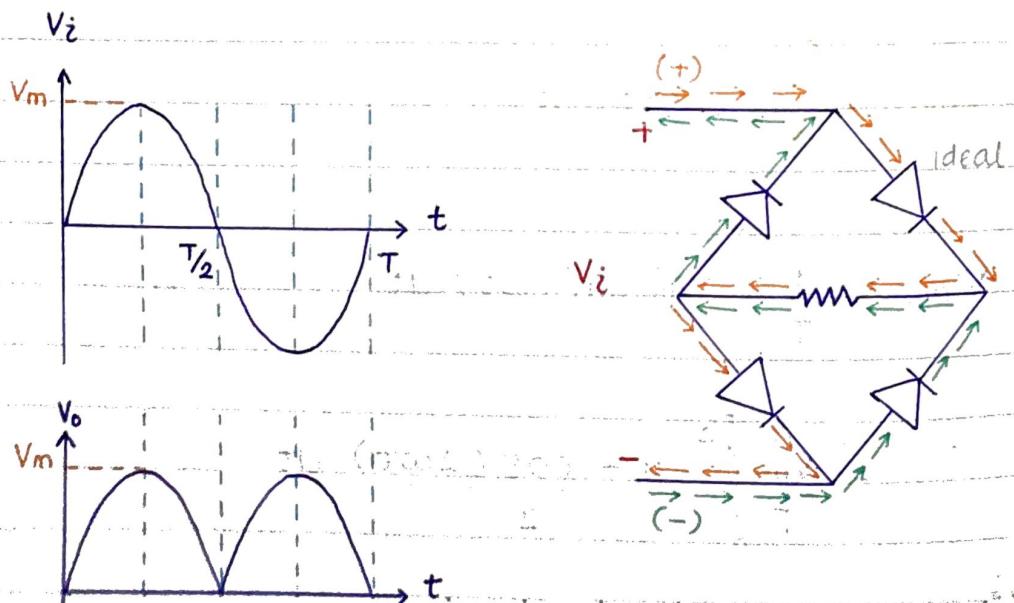

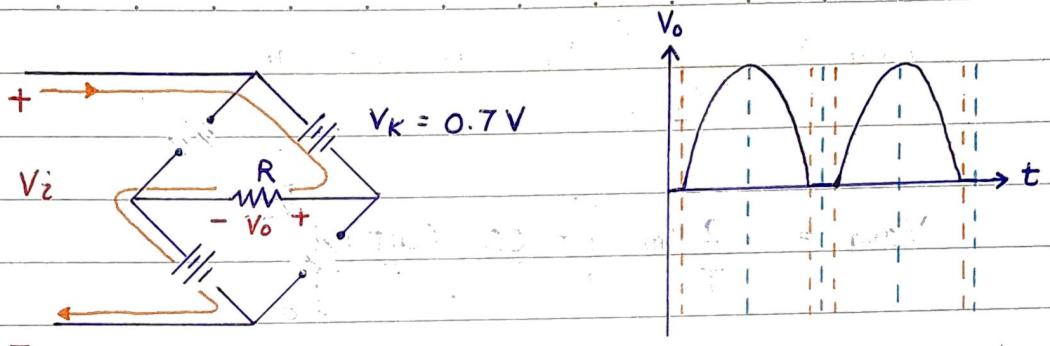

## Center - Tapped Transformer

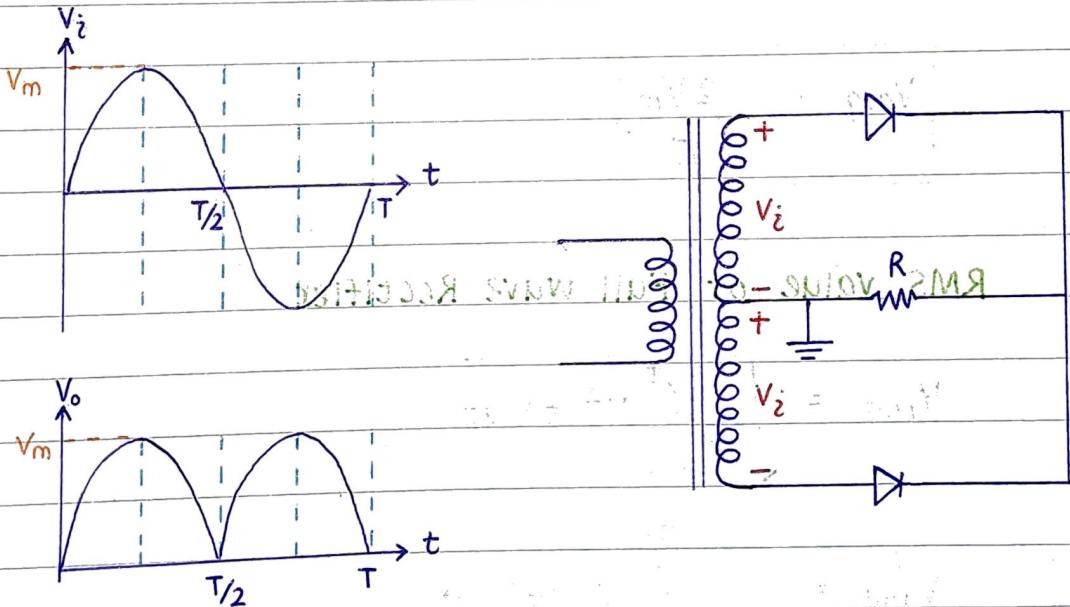

## Average value of Full wave Rectifier

$$V(t) = V_m \sin(\omega t); \quad 0 < t < T/2$$

$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

$$V_{avg} = \frac{1}{T/2} \int_0^{T/2} V_m \sin(\omega t) dt \quad \omega = \frac{2\pi}{T}$$

$$V_{avg} = \frac{2 V_m}{T} \left[ -\frac{\cos(\omega t)}{\omega} \right]_0^{T/2}$$

$$= \frac{V_m}{\pi} (-(-1) + 1) \text{ bagus T - rasa C}$$

$$V_{avg} = \frac{2 V_m}{\pi}$$

### RMS value of Full wave Rectifier

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$V_{rms}^2 = \frac{1}{T/2} \int_0^{T/2} V^2(t) dt$$

$$V_{rms}^2 = \frac{1}{T} \int_{T/2}^T V_m^2 \sin^2(\omega t) dt \quad \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$= \frac{2 V_m^2}{T} \int_0^{T/2} \left[ \frac{1 - \cos(2\omega t)}{2} \right] dt = Q \cdot V$$





$$V_{rms}^2 = \frac{V_m^2}{T} \left[ \frac{T}{2} - \frac{\sin(2\omega t)}{2\omega} + \frac{\sin(0)}{2\omega} \right]$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Parameters	Half-wave Rectifier	Center tapped full wave Rectifier	Full wave Bridge Rectifier
Peak inverse voltage	$V_m$	$2V_m$	$V_m$
Output frequency	$f$	$2f$	$2f$
Average DC value	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2V_m}{\pi}$
RMS value	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$

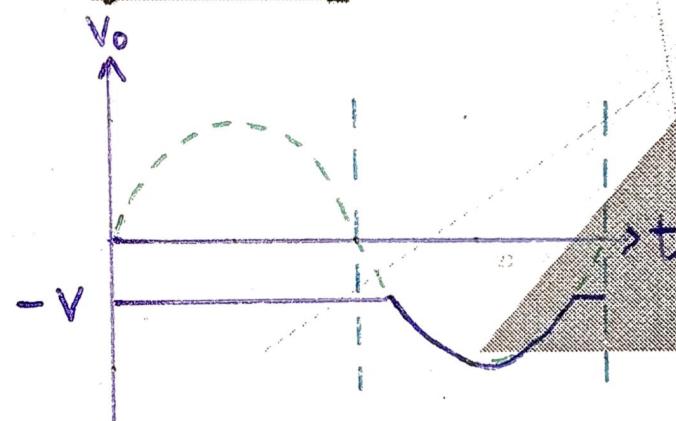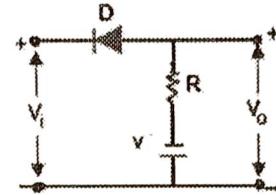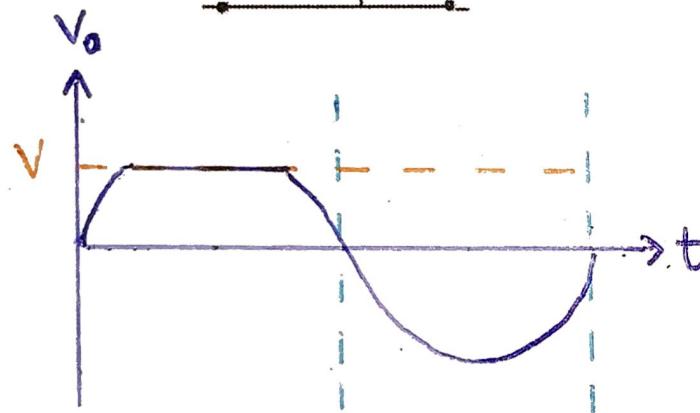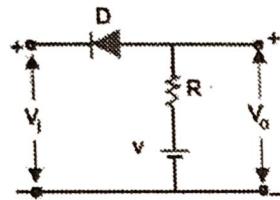
# Series-positive Clipper With Bias

- The clipping takes place during the positive cycle only when the input voltage is greater than the battery voltage (i.e.  $V_i > V$ ). The clipping level can be shifted up or down by varying the bias voltage ( $V$ )



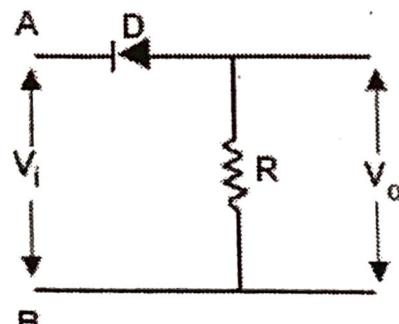
# Series positive Clipper



- In a series positive clipper, a diode is connected in series with the output







(a) Positive Clipper

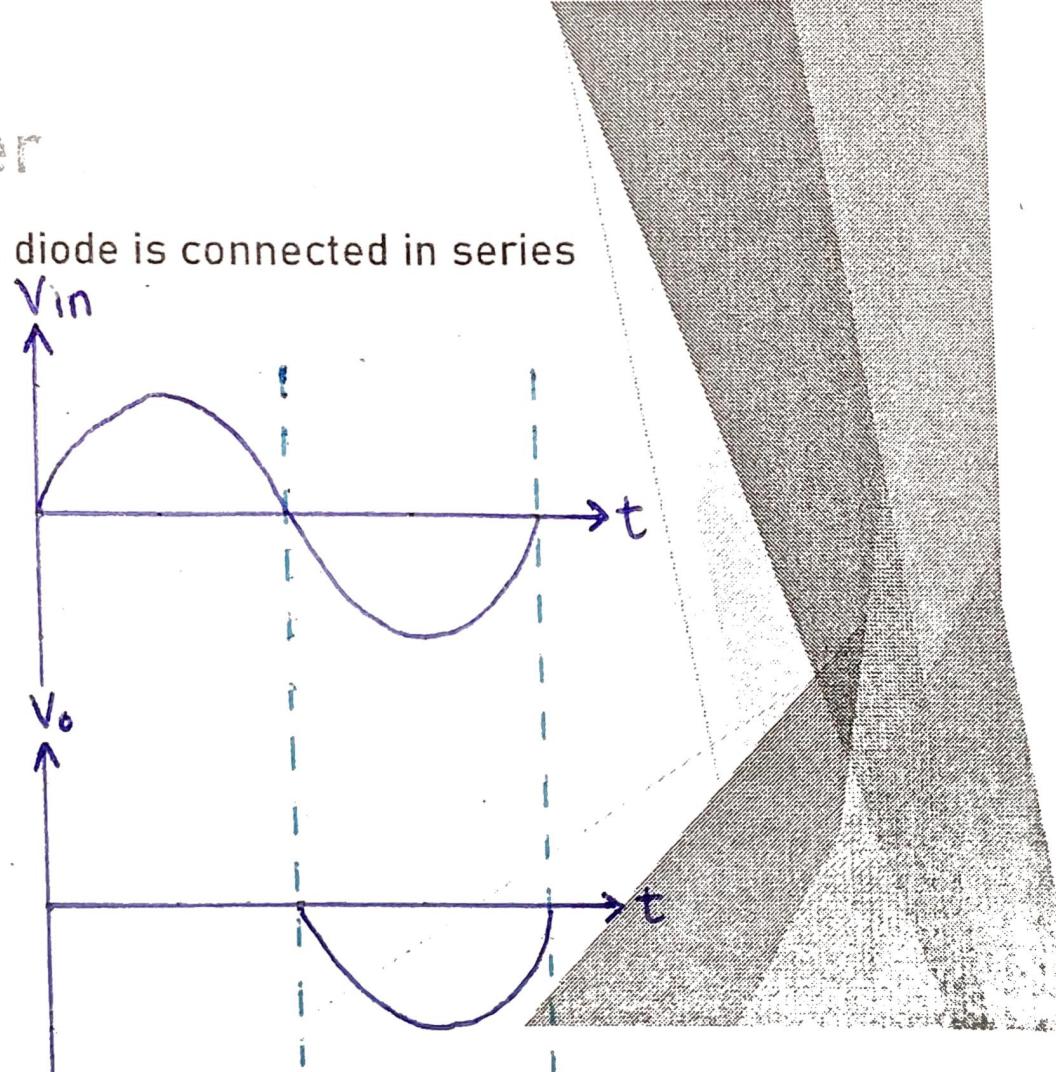





# Series Negative Clipper

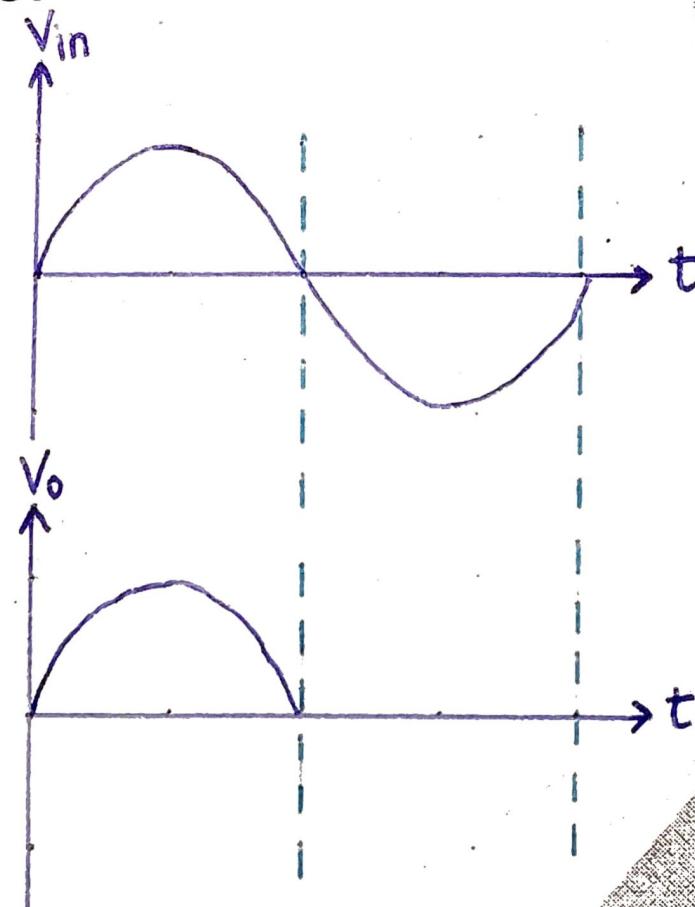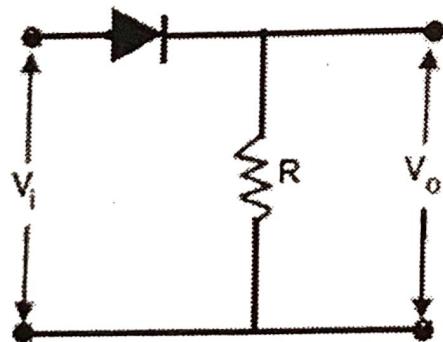

# Series-negative Clipper With Bias

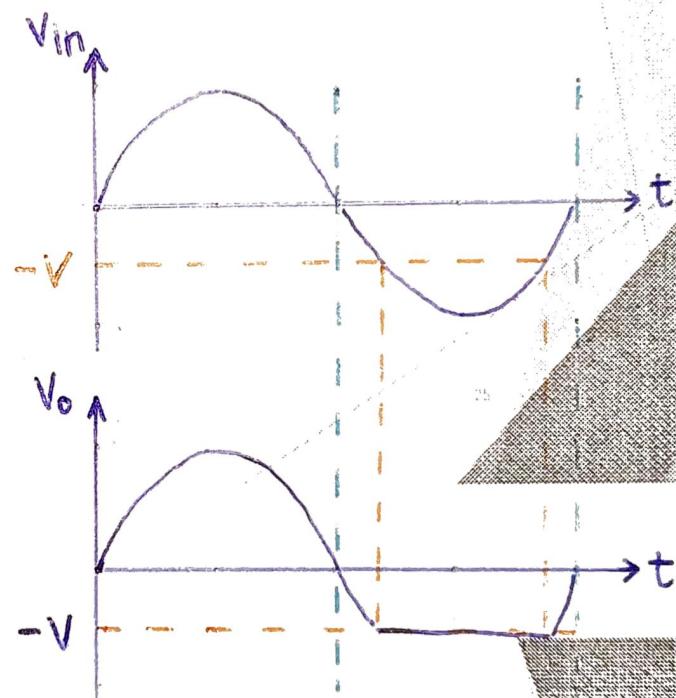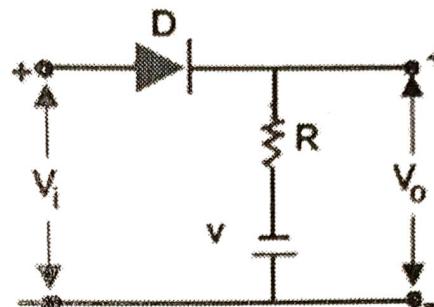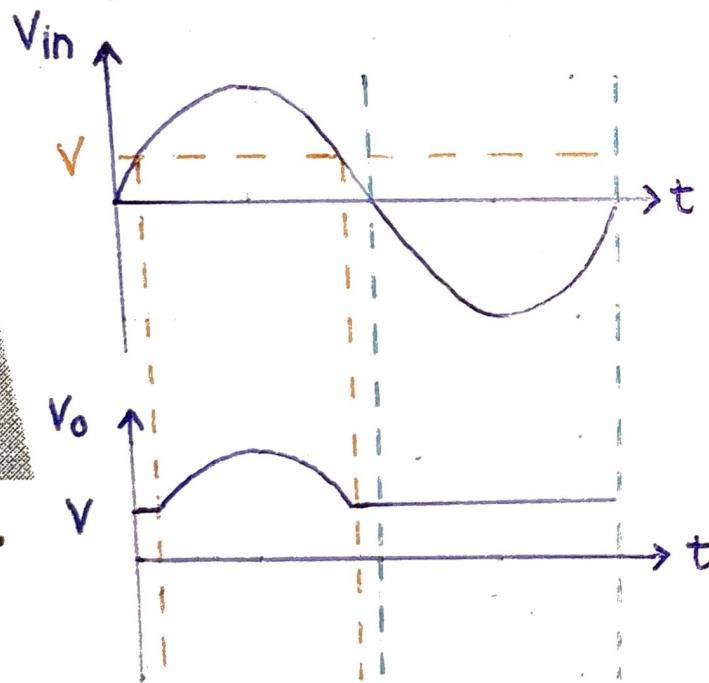
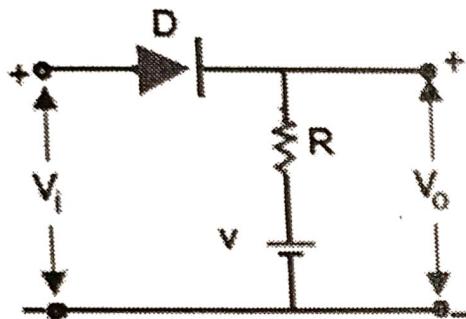

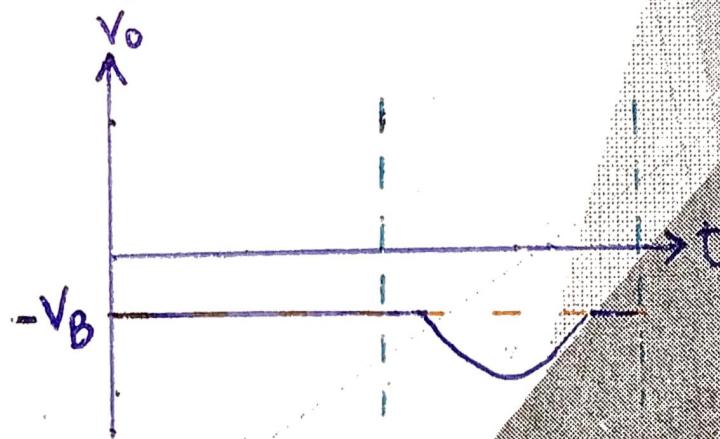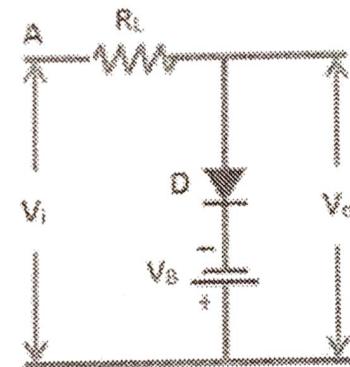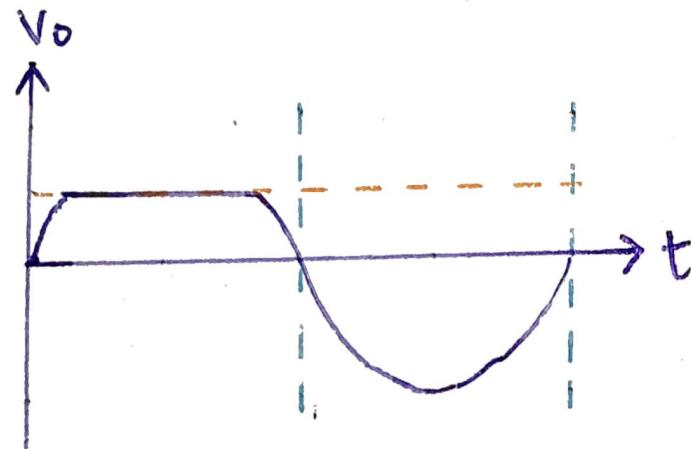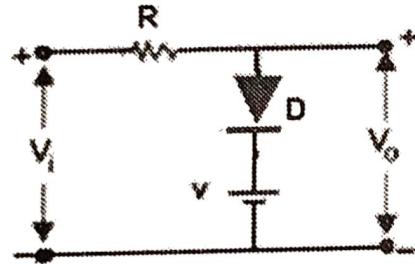
# Shunt Or Parallel Positive Clipper With Bias




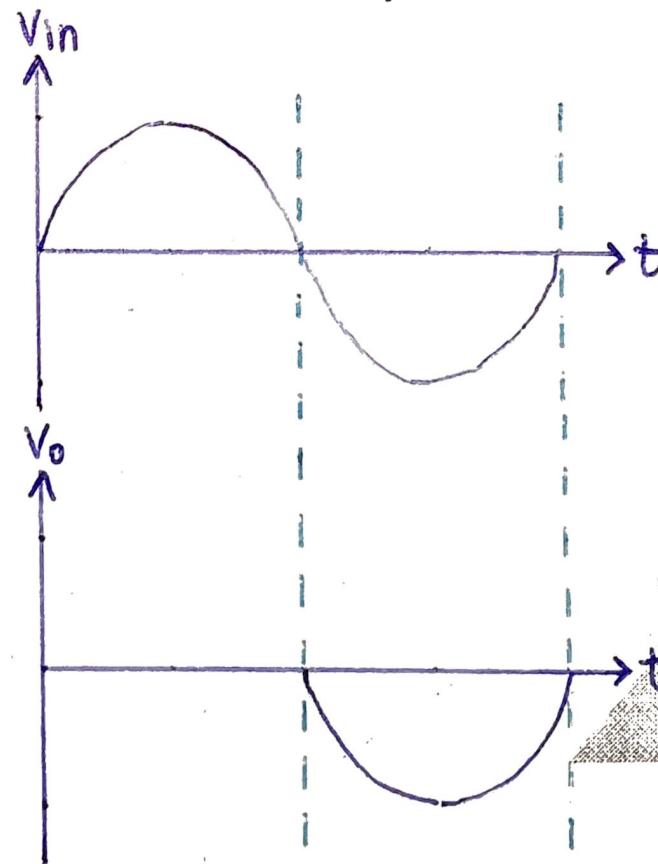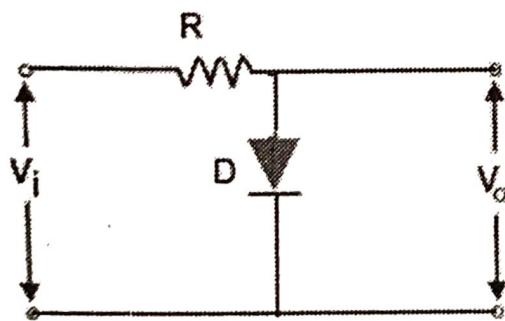
# Shunt Or Parallel Positive Clipper





In shunt clipper, the diode is connected in parallel with the output load.





# Shunt Or Parallel Negative Clipper

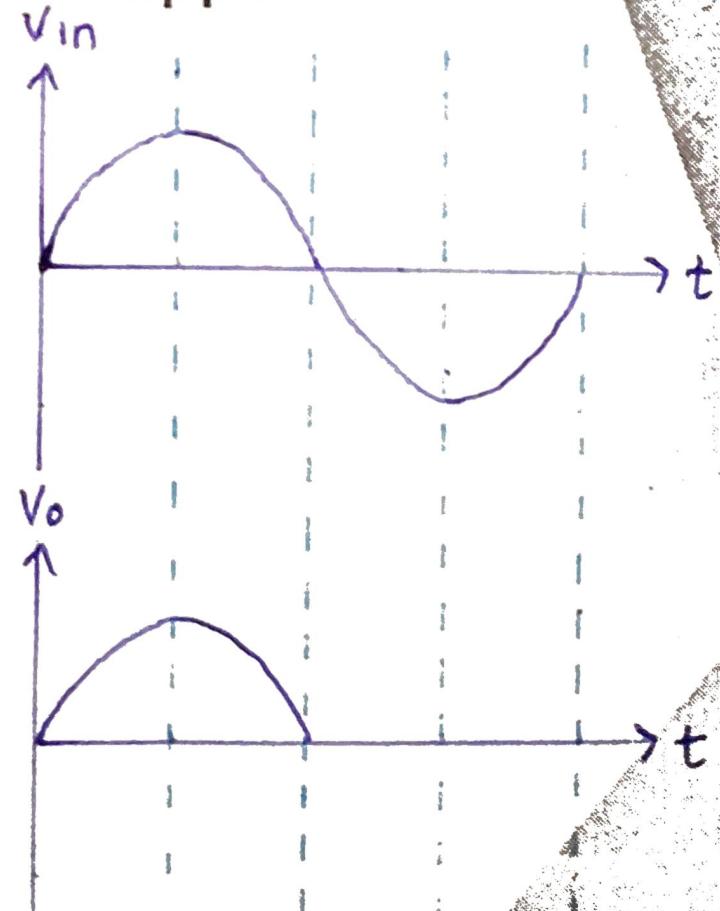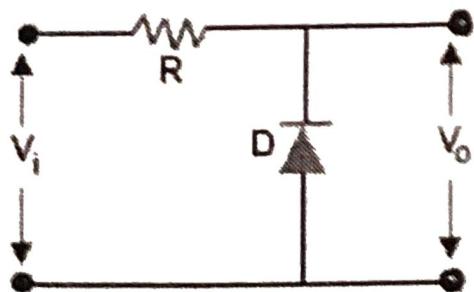
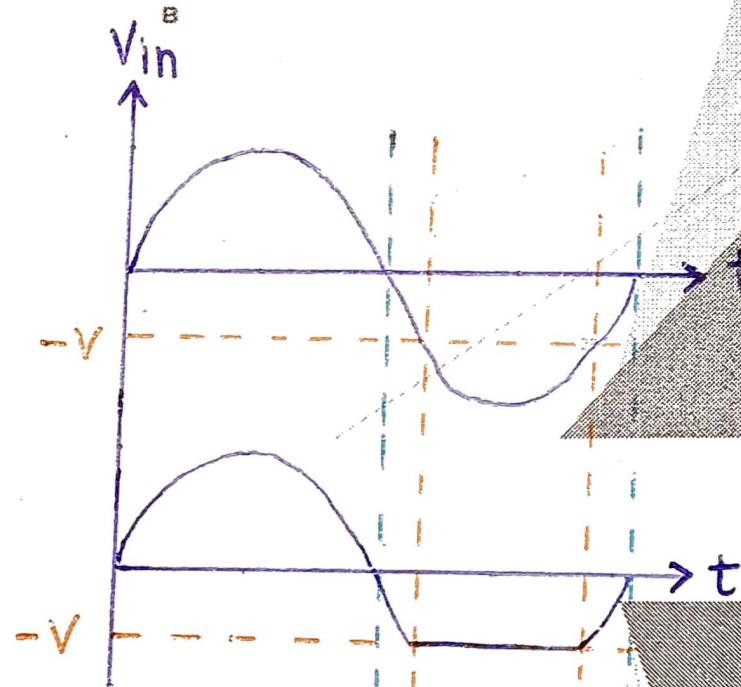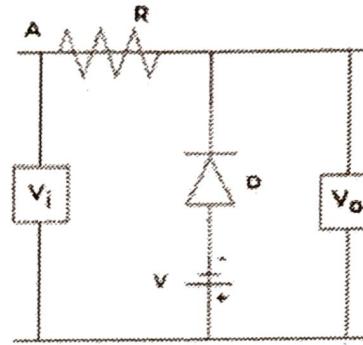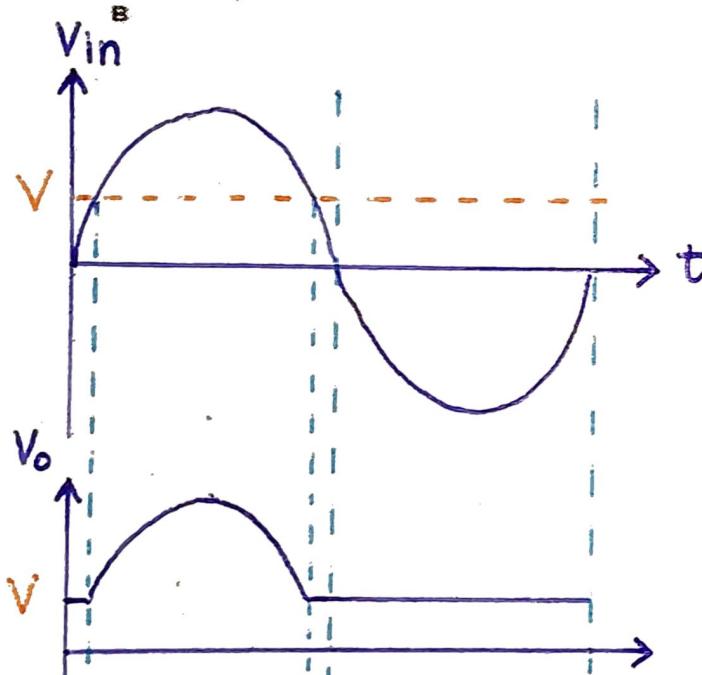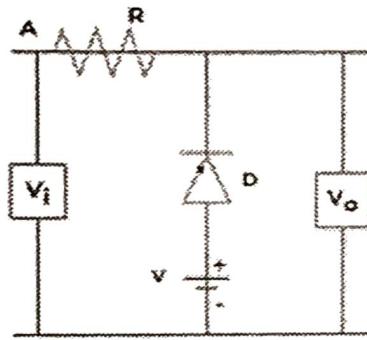
# Shunt Or Parallel Negative Clipper With Bias




# Dual (Combination) Diode Clipper

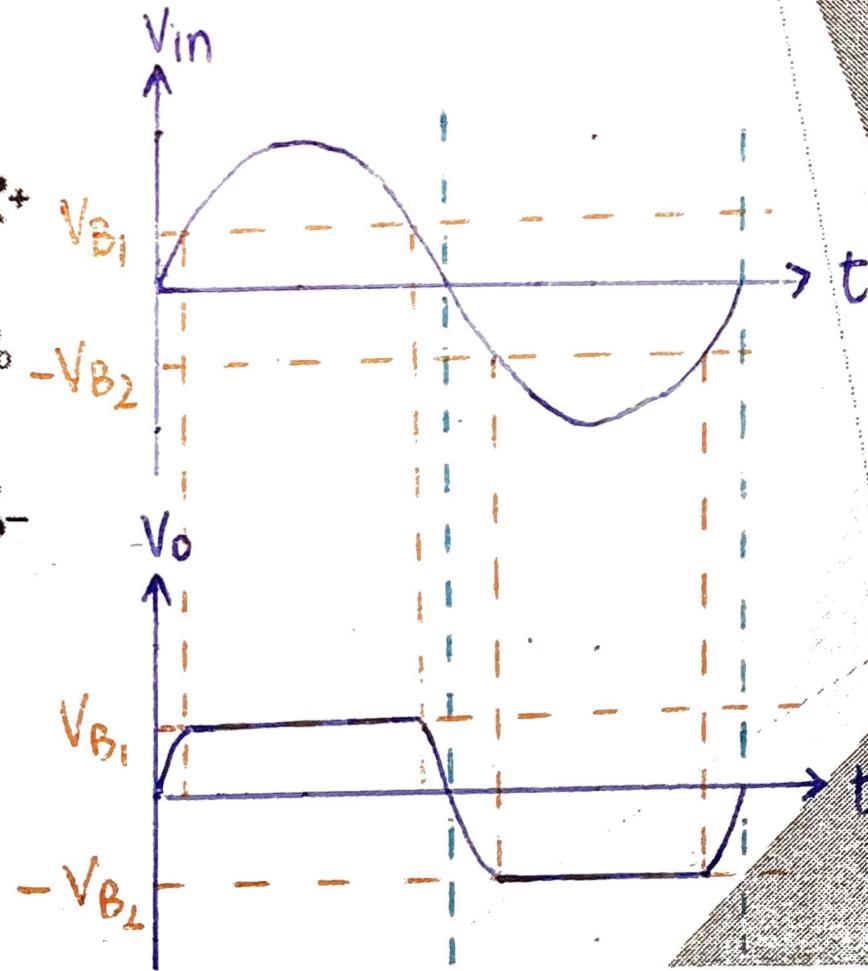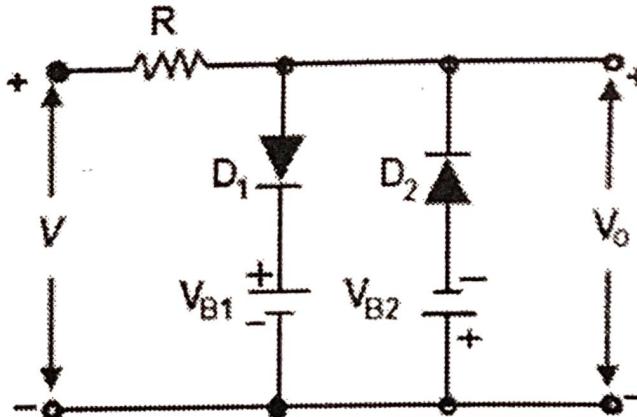

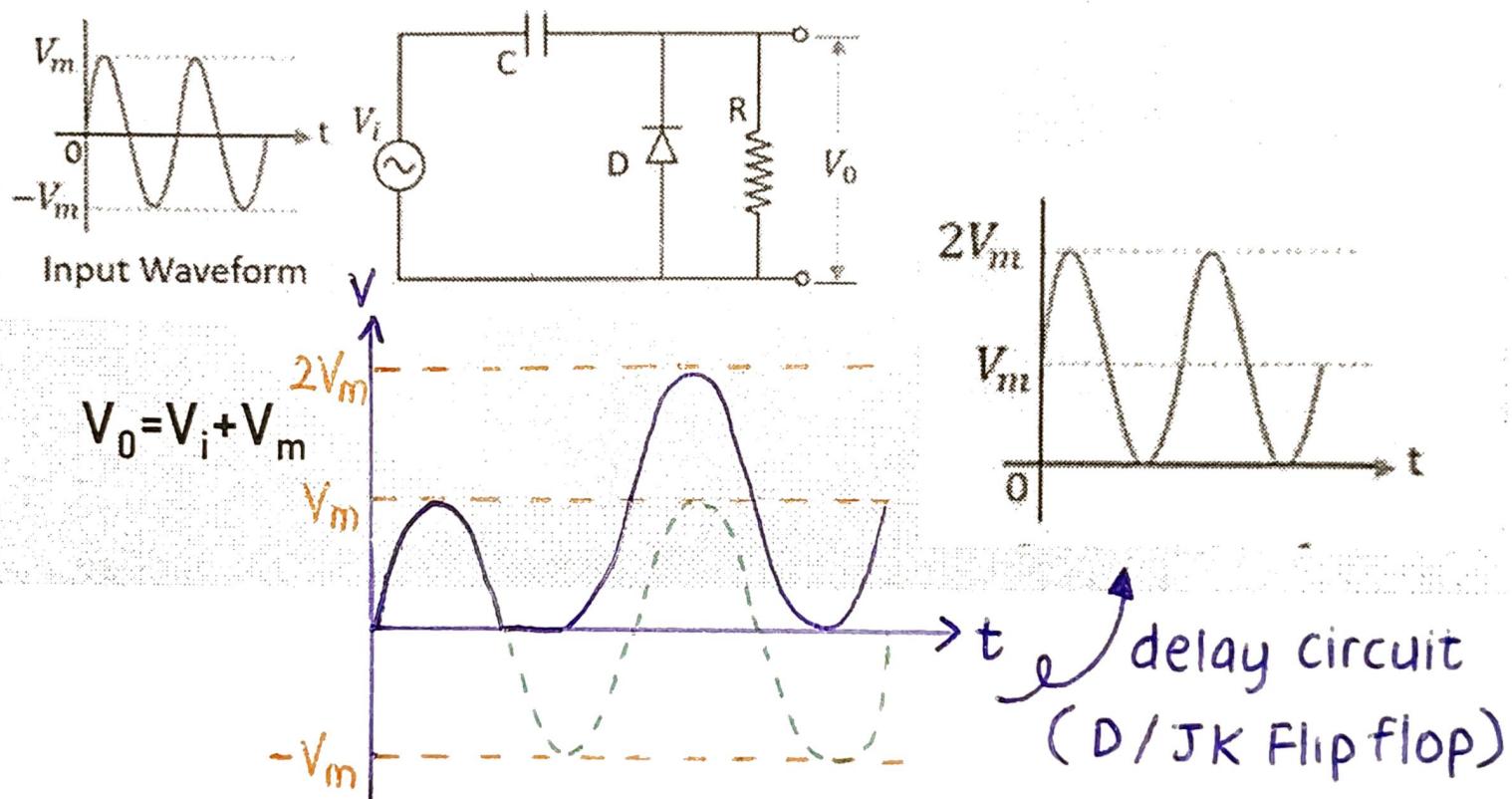
# 1. Positive Clamper Circuit

- A Clamping circuit restores the DC level. When a negative peak of the signal is raised above to the zero level, then the signal is said to be positively clamped.





### 3. Positive Clamper with Negative $V_r$

7

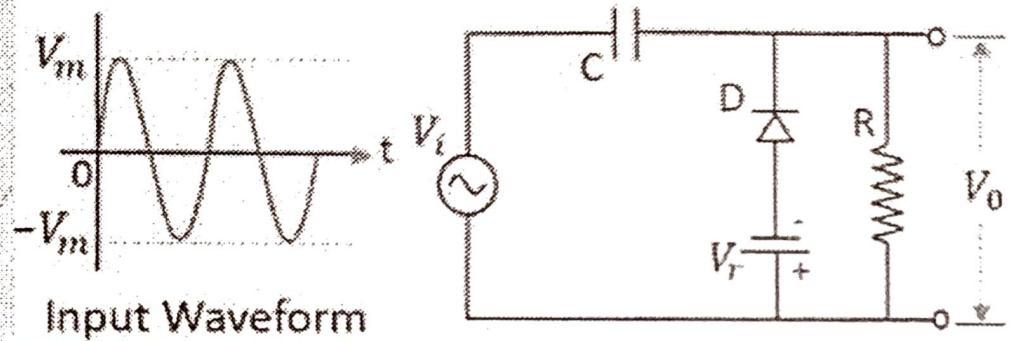




Input Waveform

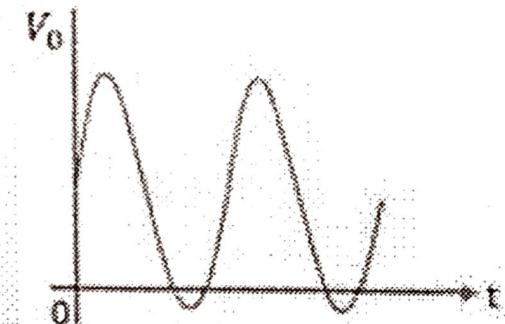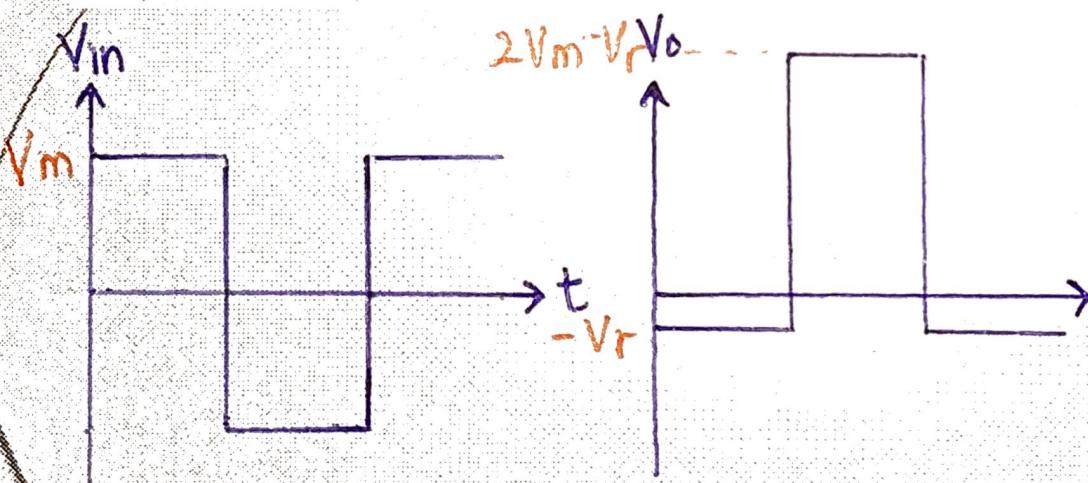
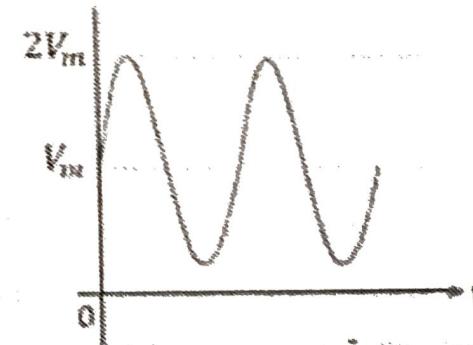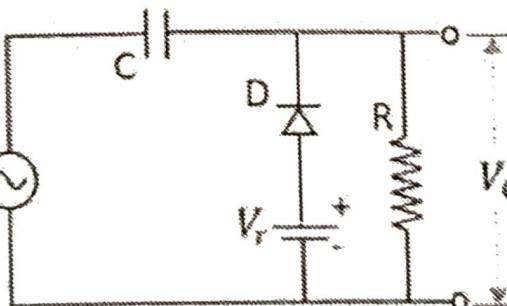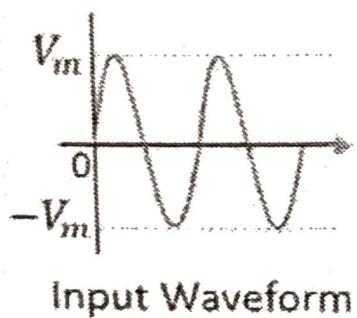
## 2. Positive Clamper with Positive $V_r$

6


- When a Positive clamper circuit is provided with a positive reference voltage and biased accordingly, the circuit incorporates this voltage into its output, elevating the clamped level in the process.


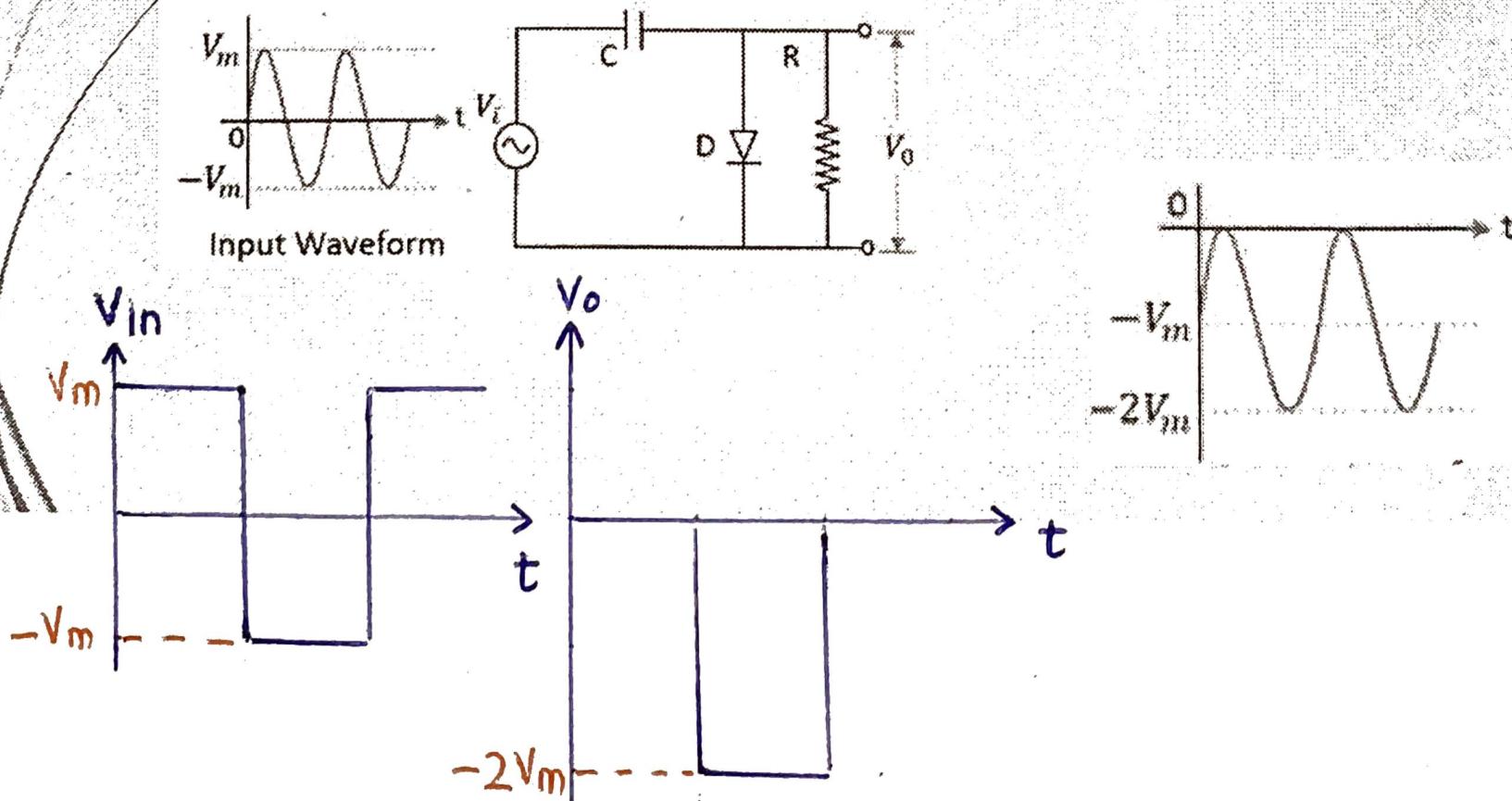
## 4. Negative Clamper


8

► A Negative Clamper circuit is one that consists of a diode, a resistor, and a capacitor and that shifts the output signal to the negative portion of the input signal.



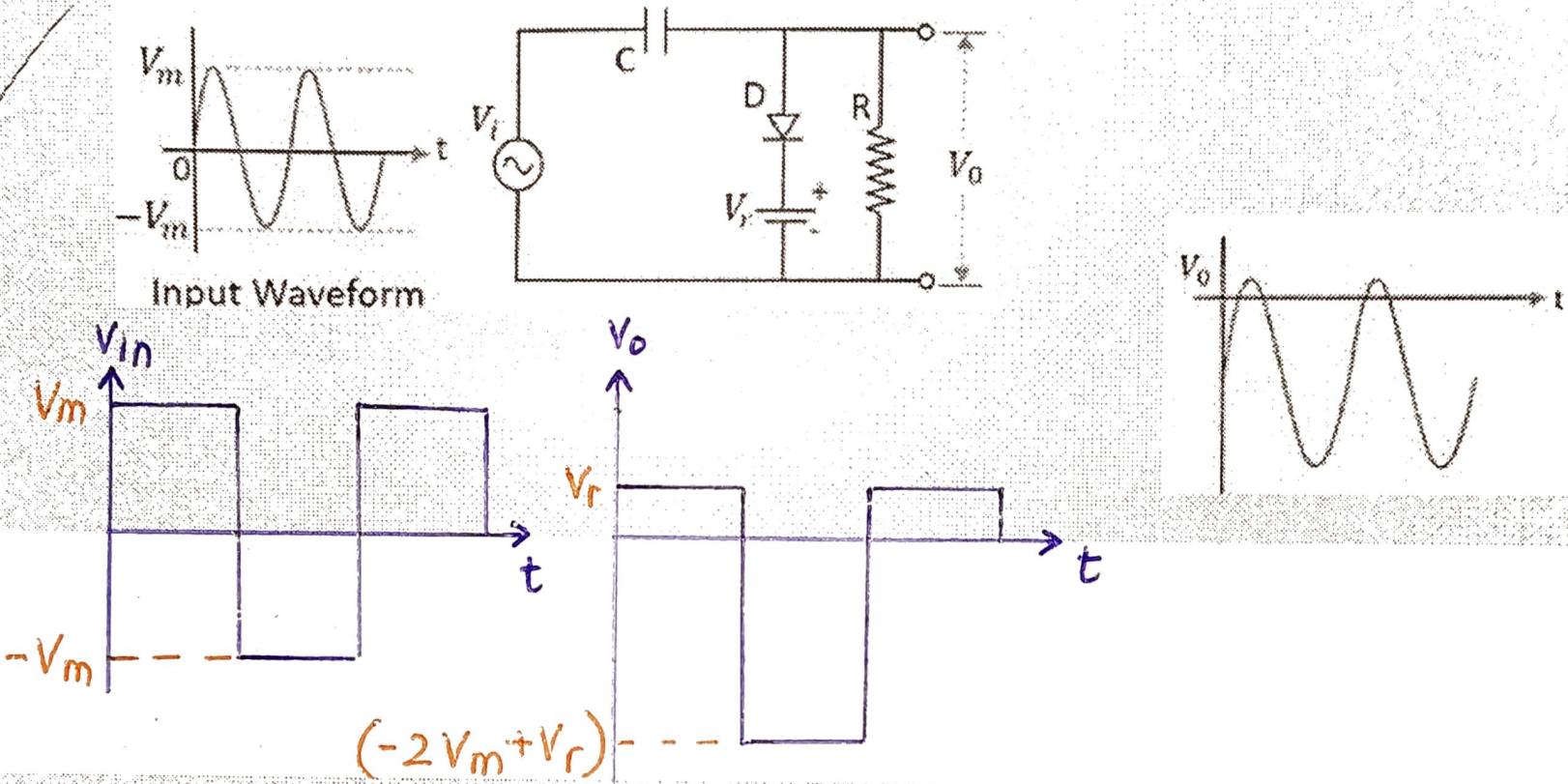
## 5. Negative clamper with positive $V_r$

- A Negative clamper circuit if biased with some positive reference voltage, that voltage will be added to the output to raise the clamped level.



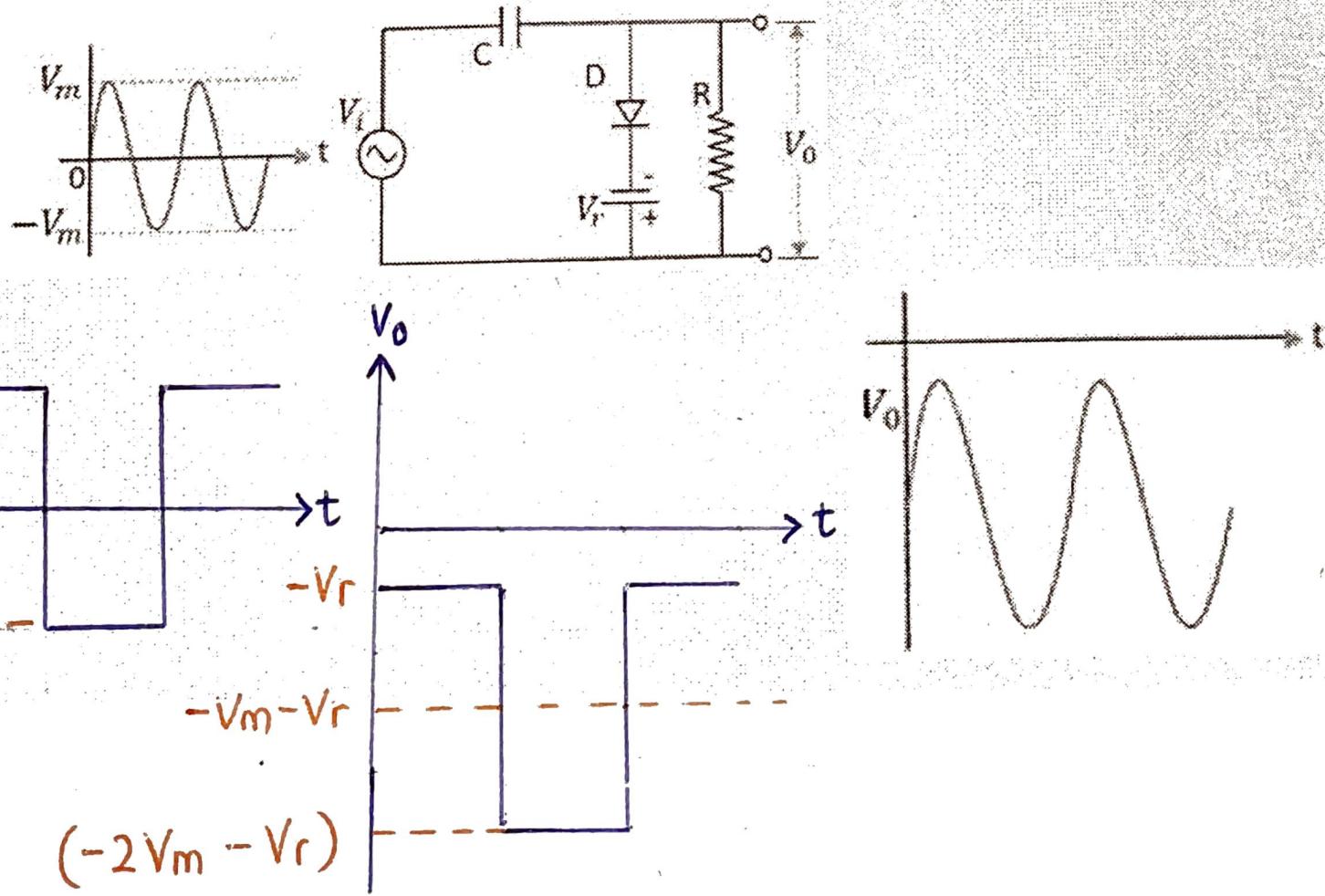
## 6. Negative Clamper with Negative $V_r$



## Ripple factor

### Ripple factor of Half wave rectifier

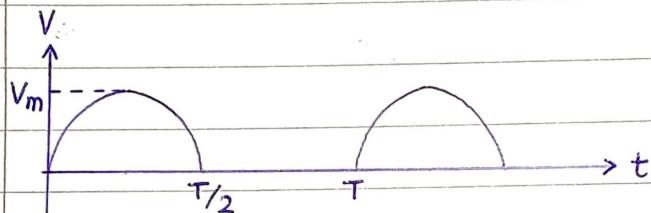

$$\text{Ripple Factor } (r) = \frac{V_{rrms}}{V_{dc}} = 1.21$$

$$V_{rms}^2 = V_{rrms}^2 + V_{dc}^2$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$V_{rms} = \sqrt{V_{rrms}^2 + V_{dc}^2}$$

$$V_{rms} = \frac{V_m}{2}$$


$$V_{rrms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$= \sqrt{\frac{V_m^2}{4} - \frac{V_m^2}{\pi^2}}$$

$$V_{rrms} = V_m \sqrt{\frac{1}{4} - \frac{1}{\pi^2}} = 0.386 V_m$$

$$r = \frac{V_{rrms}}{V_{dc}} = \frac{0.386 V_m}{V_m / \pi} = 1.211$$

## Ripple factor of Full wave rectifier

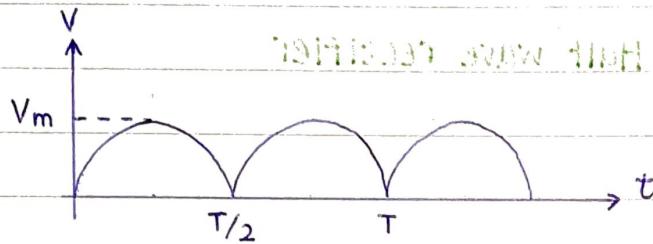

$$\text{Ripple factor (r)} = \frac{V_{rrms}}{V_{dc}} = 0.483$$

$$V_{rrms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

$$= \sqrt{\frac{V_m^2}{2} - \frac{4V_m^2}{\pi^2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$= V_m \sqrt{\frac{1}{2} - \frac{4}{\pi^2}}$$

$$V_{rrms} \approx 0.308 V_m$$

$$r_{avg} = \frac{V_{rrms}}{V_{dc}}$$



$$V_{dc}$$

$$= 0.308 V_m$$

$$= \frac{2V_m}{\pi}$$

$$= 0.483$$

## Half wave rectifier with RC filter

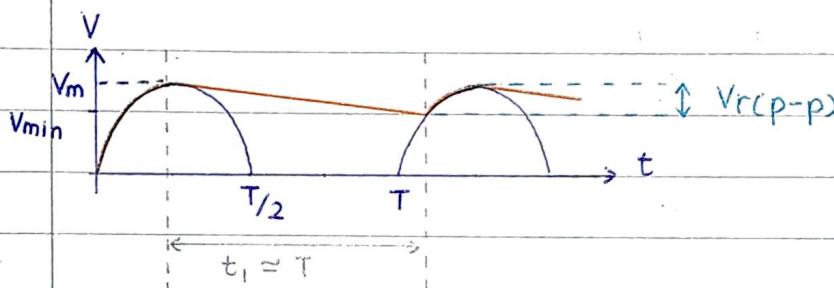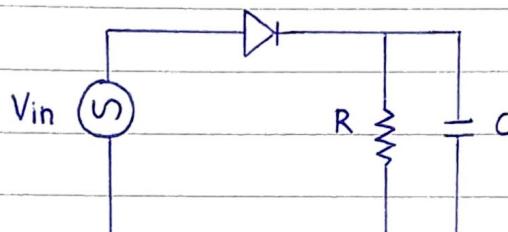

Voltage across the capacitor during discharging

$$V_c(t) = V_m e^{-t/RC}$$

$$\begin{aligned} V_{\min} &= V_m e^{-T/RC} \\ &= V_m \left(1 - \frac{T}{RC}\right) \quad (RC \gg T) \end{aligned}$$

$$V_{\max} = V_m$$

$$V_{rc(p-p)} = V_{\max} - V_{\min}$$




$$V_{rc(p-p)} = V_m - V_m + V_m \frac{T}{RC}$$

$$V_{rc(p-p)} = \frac{V_m T}{RC} = \frac{V_m}{fRC}$$

$$V_{dc} = V_m \cdot \frac{V_{r(p-p)}}{2}$$

$$\therefore V_{r(p-p)} = \frac{V_{dc}}{R_f C} \quad \text{and} \quad I_{dc} = \frac{V_{dc}}{R}$$

$$V_{r(p-p)} = \frac{I_{dc}}{f_c}$$

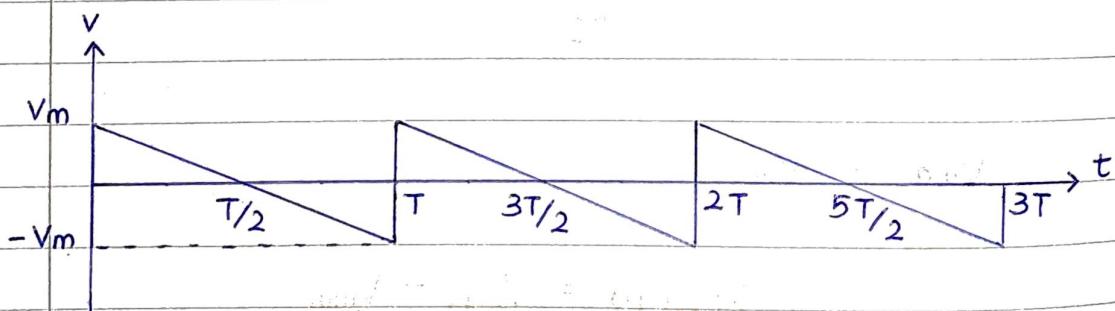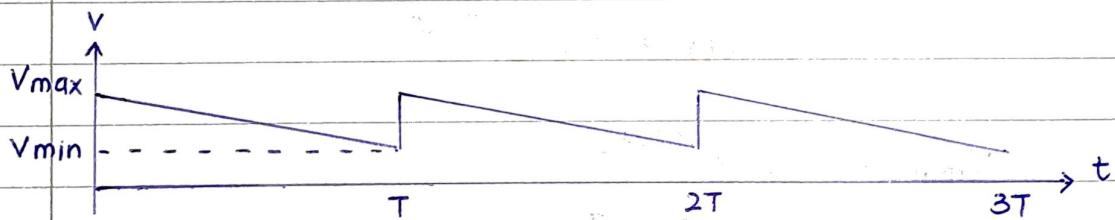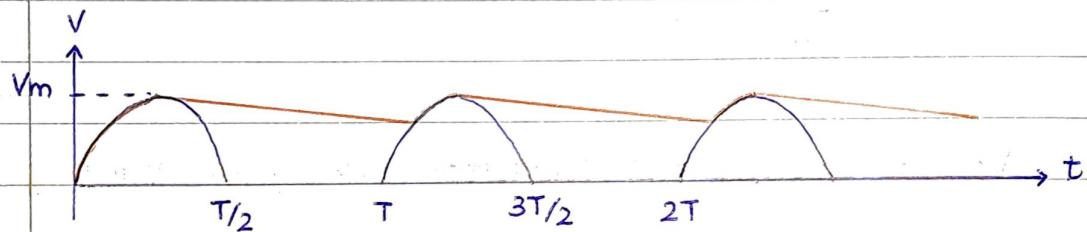

$$V(t) = V_m - \frac{2V_m}{T} \times t, \quad 0 < t < T$$

mV  
32tT mV  
32

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$V^2_{rms} = \frac{1}{T/2} \int_0^{T/2} V^2(t) dt$$

$$= \frac{2}{T} \int_0^{T/2} \left( V_m - \frac{2V_m \times t}{T} \right)^2 dt$$

$$= \frac{2V_m^2}{T} \int_0^{T/2} \left[ 1 - \frac{4t}{T} + \frac{4t^2}{T^2} \right] dt$$

$$= \frac{2V_m^2}{T} \left[ t - \frac{2t^2}{T} + \frac{4t^3}{3T^2} \right]_0^{T/2}$$

$$= \frac{2V_m^2}{T} \left[ \frac{T}{2} - \frac{T}{2} + \frac{T}{6} \right]$$

$$V_{rms} = \frac{V_m}{\sqrt{3}}$$

$$V_{rms} = \frac{V_m}{\sqrt{3}}$$

$$\rightarrow V_{rms} = \frac{2V_m}{2\sqrt{3}}$$

$$V_{rms} = \frac{V_r(p-p)}{2\sqrt{3}}$$

DATE

$$r = \frac{V_{rrms}}{V_{dc}}$$

$$= \frac{V_{r(p-p)}}{2\sqrt{3}}$$

$$V_m = \frac{V_{r(p-p)}}{2}$$


$$= \left( \frac{V_m}{2\sqrt{3}RfC} \right) \quad (RC \ggg T)$$

$$V_m = \frac{V_m}{2fRC} \rightarrow 0$$

$$2fRC$$

$$r = \frac{1}{2\sqrt{3}RfC}$$

### Full wave rectifier with RC filter

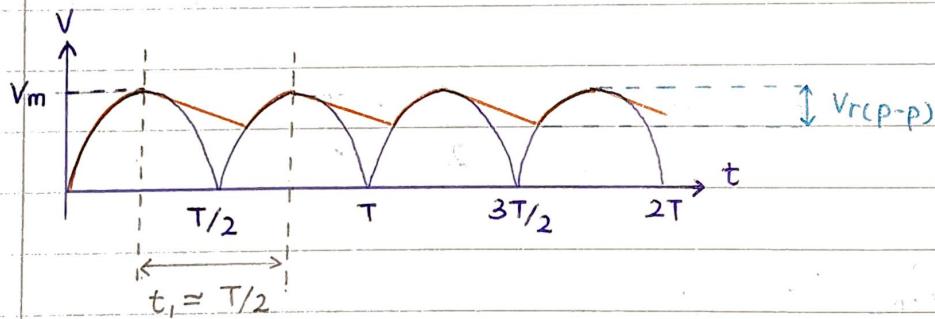

$$V_c(t) = V_m e^{-t/RC}$$

$$V_{min} = V_m e^{-T/2RC}$$

$$V_{min} = V_m \left( 1 - \frac{1}{2RC} \right)$$



$$V_{max} = V_m$$

$$V_{r(p-p)} = V_{max} - V_{min}$$

$$= V_m - V_m + \frac{V_m T}{2RC}$$

$$V_{r(p-p)} = \frac{V_m}{2fRC}$$

$$V_{r(p-p)} = \frac{I_{dc}}{2fC}$$

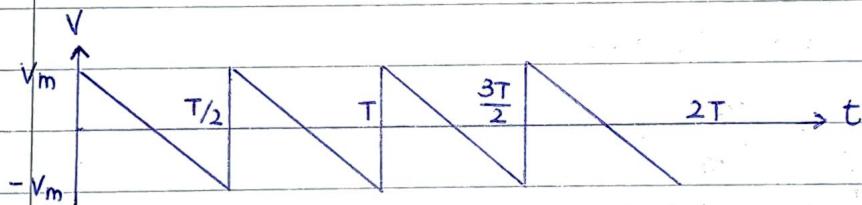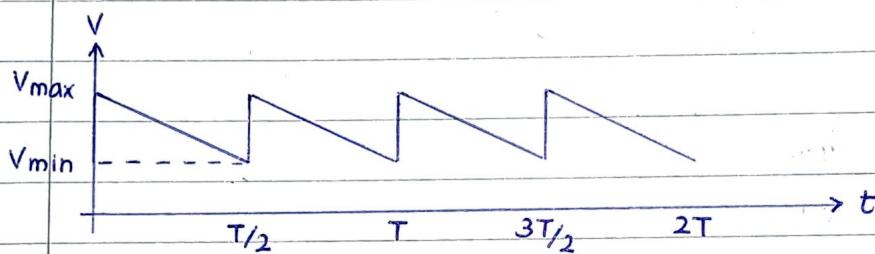

$$V(t) = V_m - \frac{4V_m t}{T} \quad 0 < t < T/2$$

$$V_{rms}^2 = \frac{1}{T/4} \int_0^{T/4} V^2(t) dt$$

$$= \frac{4}{T} \int_0^{T/4} \left( V_m - \frac{4V_m t}{T} \right)^2 dt$$

$$= \frac{4}{T} \int_0^{T/4} V_m^2 \left( 1 - \frac{8t}{T} + \frac{16t^2}{T^2} \right) dt$$

$$V^2_{rms} = \frac{4V_m^2}{T} \left[ \frac{T}{4} - \frac{4}{T} \left( \frac{T}{4} \right)^2 + \frac{16}{3T^2} \left( \frac{T}{4} \right)^3 \right]$$

$$= \frac{4V_m^2}{4} \left[ 1 - 1 + \frac{1}{3} \right]$$

$$V_{rms} = \frac{V_m}{\sqrt{3}} = \frac{V_r(p-p)}{2\sqrt{3}}$$

$$r = V_{rms}$$

$$= \frac{V_r(p-p)}{2\sqrt{3}}$$

$$V_m - \frac{V_r(p-p)}{2}$$

$$= \left( \frac{V_m}{2\sqrt{3}fRC} \right)$$

$$\left( \frac{V_m - \frac{V_m}{2}}{2fRC} \right)^0$$

$$r = \frac{1}{4\sqrt{3}fRC}$$